



DEPARTMENT OF ELECTRICAL & ELECTRONICS ENGINEERING

END OF SEMESTER EXAMINATION -ACADEMIC YEAR 2020-2021

TRIMESTER I

GROUP: Y2 EPE

MODULE: EPE2165—ANALOG ELECTRONICS

DATE: 14/09/2021

TIME: 2 hours

MAX POINTS = 50 POINTS

INSTRUCTIONS

- You have 2 hours to complete the exam. Be a smart test taker: if you get stuck on one problem go on to the next.
- This exam paper comprises 3 pages, excluding the title page. Please check that you have received all of them.
- This exam paper contains 3 questions. Answer only 2 questions as follows
 - QUESTION # 1 is COMPULSORY
 - Chose ONE (1) question from questions 2 and 3
 - If a candidate answers more than two questions, at the sole discretion of the grader, only two questions will be graded.
- Keep your answers short and to the point. Longer is not necessarily better as the number of written words is NOT a grading criterion and, in some case, longer answers may even make your answer abstruse.
- Write legibly. If the grader cannot read it, you will not get credit for it.
- Write all your answers in the answer booklet provided
- Do not forget to write your Registration Number
- No written materials allowed.
- Do not write any answers on this questions paper

1. (a) (5 points) **Figure 1** depicts an amplifier composed of a cascade of three stages. The amplifier is fed by a signal source with a source resistance of $100\text{ k}\Omega$ and delivers its output into a load resistance of $100\ \Omega$. The first stage has a relatively high input resistance and a modest gain factor of 10. The second stage has a higher gain factor of 100 but a lower input resistance. Finally, the last, or output, stage has unity gain but a low output resistance. Calculate the overall gain of the amplifier. Express your answer in dB.

 


FIGURE 1. Three-stage amplifier

Solution:

- The fraction of the source signal that appears at the the input terminal is given by **Equation (1)**

$$\frac{v_{i1}}{v_s} = \frac{1\text{ M}\Omega}{1\text{ M}\Omega + 100\text{ k}\Omega} = 0.909\text{ V/V} \quad (1)$$

- The voltage gain of the first stage is calculated by considering the input resistance of the second stage (**Equation (2)**)

$$A_{v1} \equiv \frac{v_{i2}}{v_{i1}} = 10 \frac{10\text{ k}\Omega}{100\text{ k}\Omega + 1\text{ k}\Omega} = 9.9\text{ V/V} \quad (2)$$

- In the same manners, the voltage gain of the second stage is given by **Equation (3)**

$$A_{v1} \equiv \frac{v_{i3}}{v_{i2}} = 100 \frac{10\text{ k}\Omega}{10\text{ k}\Omega + 1\text{ k}\Omega} = 90.9\text{ V/V} \quad (3)$$

- The voltage gain of the output stage is given **Equation (4)**

$$A_{v1} \equiv \frac{v_L}{v_{i3}} = \frac{100\ \Omega}{100\ \Omega + 10\ \Omega} = 0.909\text{ V/V} \quad (4)$$

- The overall gain is the product of the three gains (**Equation (5)**)

$$\begin{aligned} A_v &= \text{frac} v_L v_{i1} = A_{v1} A_{v2} A_{v3} = 818\text{ V/V} = 818\text{ V/V} \\ &= 20 \log(818) = 58.25\text{ dB} \end{aligned} \quad (5)$$

- (b) **Figure 2** represents a portion of battery-charger circuit for a battery with a voltage V_B . The sine-wave input $v_S = 12\text{V}(rms)$, while the battery voltage varies from 12 V to 14 V from the discharged to fully charged states. The charging-source resistance $R_S = 10\ \Omega$. Assuming that D is an ideal diode, and $R_C = 50\ \Omega$ is a current-controlling resistor established by the designer:


 


FIGURE 2. Battery-charger circuit

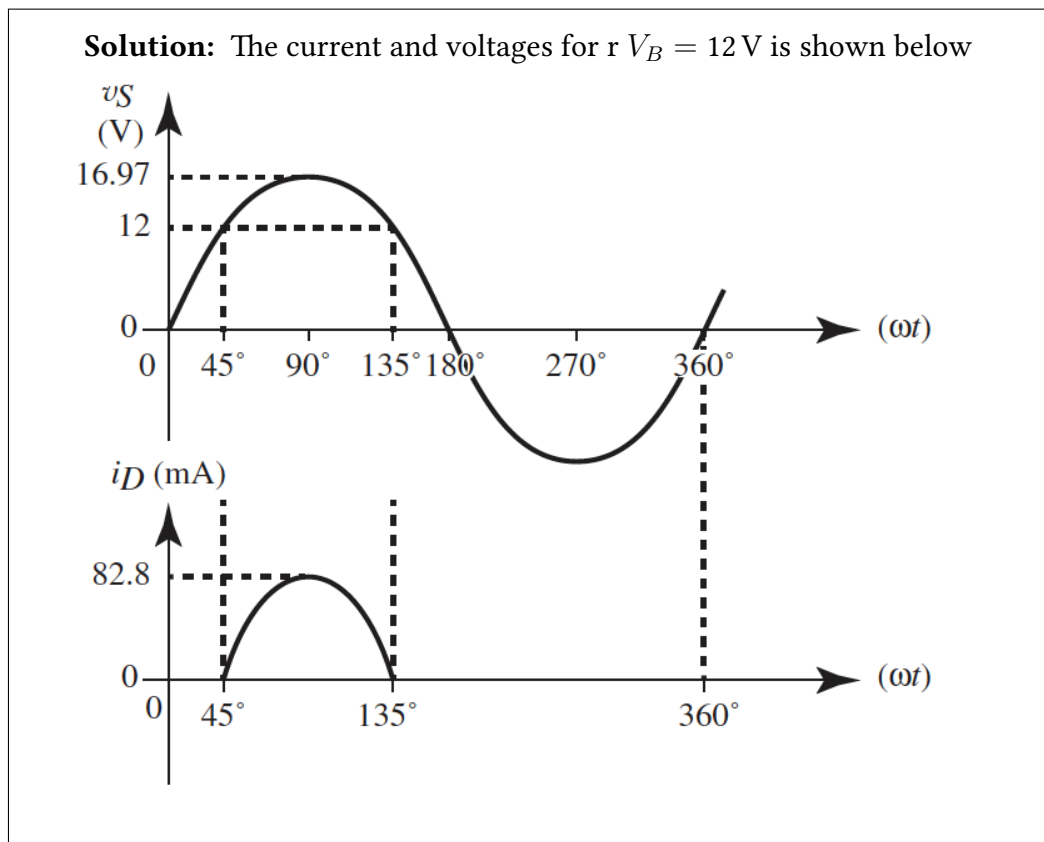- i. (5 points) Sketch and label the voltage waveforms of the voltage accros the diode and the current through the diode for $V_B = 12\text{ V}$.



Note: To receive the full marks, the student should show:

- Clear units
- Clear labels and their values
- That the peak is at 90 degrees

ii. (5 points) What is the peak diode current?

Solution: For a battery voltage V_B and an ideal diode, the diode current is

$$i_D = \frac{v_s - V_B}{R_S + R_C} = \frac{V_S' \sin(\omega t) - V_B}{10 \Omega + 50 \Omega} \quad (6)$$

where $V_S' = \sqrt{2} \times 12V = 16.97V$. Thus, for $V_B = 12V$, the current is given in Equation (7)

$$i_D = \frac{16.97 \sin(\omega t) - 12V}{60 \Omega} \quad (7)$$

Equation (7) shows that the peak current would be Equation (8)

$$i_{Dmax} = \frac{16.97V - 12V}{60 \Omega} = 82.8 \text{ mA} \quad (8)$$

(c) An NMOS transistor is fabricated in a $0.13 \mu\text{m}$ CMOS process (i.e., $L_{min} = 0.13 \mu\text{m}$) with $L = 1.5L_{min}$, $W = 1.3 \mu\text{m}$. The process technology is specified to have an oxide layer $t_{ox} = 2.7 \text{ nm}$, $\mu_n = 400 \text{ cm}^2 \text{ V}^{-1} \text{ s}$ and $V_{tn} = 0.4V$

i. (6 points) Find the oxide capacitance, C_{ox} , the process transconductance, k_n' , and the MOSFET transconductance parameter, k_n . The permittivity of the silicon dioxide, $\epsilon_{ox} = 3.45 \times 10^{-11} \text{ F} \cdot \text{m}^{-1}$

Solution:

$$L = 1.5L_{min} = 1.5 \times 0.13 = 0.195 \mu\text{m} \quad (9)$$

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = 1.28 \times 10^{-2} \text{ F/m}^2 \quad (10)$$

$$k_n' = \mu_n C_{ox} = 512 \times 10^{-6} \text{ A/V}^2 \quad (11)$$

$$k_n = k_n' \frac{W}{L} = 3413 \mu\text{A V}^{-2} \quad (12)$$

- ii. (6 points) Find the overdrive voltage V_{OV} and the minimum value of V_{DS} required to operate the transistor in saturation at a current $I_D = 100\ \mu\text{A}$. What gate-to-source voltage is required?

Solution: When the MOSFET operates in saturation, the current is given by

$$I_D = \frac{1}{2}k_n V_{OV}^2 \quad (13)$$

Thus,

$$V_{OV} = \sqrt{\frac{I_D}{\frac{1}{2}k_n}} = 0.24\text{V} \quad (14)$$

As V_{GS} is reduced, r_{DS} increases, becoming infinite when the channel disappears, which occurs as V_{OV} reaches zero or, correspondingly,

$$V_{GS} = V_{tn} = 0.4\text{V} \quad (15)$$

- (d) (6 points) For the NMOS transistor in **Figure 3**, determine the values of R_D and R_S so that the transistor operates at $i_D = 0.4\text{mA}$ and $V_D = +0.5\text{V}$. The NMOS transistor has $V_t = 0.7\text{V}$, $\mu_n C_{ox} = 100\ \mu\text{A}/\text{V}^2$, $L = 1\ \mu\text{m}$, and $W = 32\ \mu\text{m}$. Neglect the channel-length modulation effect (i.e., $\lambda = 0$).

 


FIGURE 3. NMOS transistor

 


FIGURE 4. Common-emitter BJT circuit

Solution:

- For a V_D voltage, we have

$$R_D = \frac{V_{DD} - V_D}{I_D} = \frac{2.5 - 0.5}{0.4} = 5\text{ k}\Omega \quad (16)$$

- To calculate R_S we need to know the voltage at the source terminal.

– Since $V_D = 0.5 > V_G$, the transistor is in the saturation mode. Thus,

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{OV}^2 \quad (17)$$

The overdrive voltage is thus given by

$$V_{OV} = \sqrt{\frac{I_D}{\frac{1}{2} \mu_n C_{ox} \frac{W}{L}}} = 0.5V \quad (18)$$

– It is now possible to calculate V_{GS}

$$V_{GS} = V_t + V_{OV} = 0.7V + 0.5V = 1.2V \quad (19)$$

– The source resistor is thus given by

$$R_S = \frac{V_G - V_S - V_{SS}}{I_D} = \frac{0 - 1.2 - (-2.5)}{0.4} = 3.25 \text{ k}\Omega \quad (20)$$

(e) For the common-emitter circuit in **Figure 4**,

- (5 points) Calculate the base current, collector current, emitter currents, the V_{CE} voltage and the transistor power dissipation. Assume $\beta = 200$ and $V_{BE(on)} = 0.7V$

Solution:

- The base current is found as

$$\begin{aligned} I_B &= \frac{V_{BB} - V_{BE(on)}}{R_B} \\ &= \frac{4V - 0.7V}{220k} \\ &= 15 \mu A \end{aligned} \quad (21)$$

- The collector current is

$$I_C = \beta I_B = 200 \times 15 \mu A = 3mA \quad (22)$$

- The emitter current is

$$I_E = (1 + \beta) I_B = 3.02mA \quad (23)$$

- The collector-emitter voltage is

$$V_{CE} = V_{CC} - I_C R_C = 4V \tag{24}$$

- The power dissipated is

$$\begin{aligned} P_T &= I_B V_{BE(on)} + I_C V_{CE} \\ &= 0.015 \times 0.7 + 3 \times 4 \\ &= 12mW \end{aligned} \tag{25}$$

ii. (2 points) What is the mode of operation for the BJT in **Figure 4**? Briefly explain your answer.

Solution: Since $V_{BB} > V_{BE(on)}$ and $V_{CE} > V_{BE(on)}$, the transistor is biased in the forward-active mode.

2. The NMOS transistor in the circuit in **Figure 5** has $V_{tn} = 0.5V$, $k'_n = 400 \mu A V^{-2}$, $W/L = 10$ and $\lambda = 0$

 


FIGURE 5

 


FIGURE 6

(a) (2 points) Find the the transistor's operating mode when $V_D = +0.5V$

Solution: When $V_D = +0.5V$, then the transistor will be in the saturation mode since $V_D > V_G$

- (b) (4 points) Find the required values of R_S and R_D to obtain $i_D = 180 \mu A$ and $V_D = +0.5V$. Also, find the voltage V_S that results

Solution:

- As shown in the previous solution, for $V_D = 0.5V$, the transistor will be in the saturation mode. Hence,

$$I_D = \frac{1}{2} k'_n \left(\frac{W}{L} \right) V_{OV}^2 \quad (26)$$

- Solving Equation (26) given the required value of V_{OV}

$$180 = \frac{1}{2} \times 400 \times 10 V_{OV}^2 \Rightarrow V_{OV} = 0.3V \quad (27)$$

- V_{GS} is calculated as shown in Equation (28)

$$V_{GS} = V_{tm} + V_{OV} = 0.5 + 0.3 = 0.8V \quad (28)$$

- Consequently,

$$V_S = V_G - V_{GS} = 0 - 0.8 = -0.8V \quad (29)$$

- And the required value for R_S is given as

$$\begin{aligned} R_S &= \frac{V_S - (-V_S)}{I_D} \\ &= \frac{-0.8 - (-1)}{180 \mu A} \\ &= 1.11 \text{ k}\Omega \end{aligned} \quad (30)$$

- The value of the R_D resistor is given as

$$R_D = \frac{V_{DD} - V_D}{I_D} = \frac{1V - 0.5V}{0.18mA} = 2.78 \text{ k}\Omega \quad (31)$$

- (c) (4 points) What is the largest value to which R_D can be increased while the transistor remains in the saturation mode?

Solution:

- As R_D is increased, V_D decreases (Equation (32))

$$\begin{aligned} V_D &= 1 - I_D R_D \\ &= C \\ &= D \end{aligned} \quad (32)$$

- Eventually, V_D falls below V_G by V_{tn} at which point the transistor leaves the saturation region and enters the triode region. This occurs at

$$V_D = V_G - V_{tn} = -0.5V \quad (33)$$

- The corresponding value of R_D is given by

$$-0.5 = V - 0.18R_D \Rightarrow R_D = 8.3\text{ k}\Omega \quad (34)$$

3. The BJT in Figure 6 has $\beta = 100$, $V_{CESat} = 0.3V$ and $V_{B(on)} = 0.7V$. Find V_E , V_C and I_B and the transistor's mode of operation:

- (a) (3 points) When $V_B = 0V$

Solution: In this case, the transistor is in cut-off mode. Thus,

- $i_B = 0$
- $V_E = V_B = 0$
- $V_C = 10V$

- (b) (3 points) When $V_B = 3V$

Solution: In this case, the transistor is in the active mode

- $V_E = V_B - V_{on} = 3 - 0.7 = 2.3V$
- $I_E = \frac{V_E}{2k} = \frac{2.3}{2k} = 1.15mA$
- $I_C = \alpha I_E = 0.99 \times 1.15 = 1.14mA$
- $I_B = I_E - I_C = 0.01mA$
- $V_C = 10V - I_C R_C = 4.3V$

- (c) (4 points) When $V_B = 5V$



Solution: If we apply the same approach as in (b) above (and assume that the transistor is in active mode), we would notice that $I_C < 0$, which is not possible. Thus, the transistor must be in active mode. In this case:

- $V_E = 4.3V$
- $I_E = 4.3/2 = 2.15mA$
- $V_C = V_E + V_{CESat} = 4.3 + 0.3V = 4.6V$
- $I_C = \frac{10V-4.6V}{5} = 1.08mA$
- $I_B = I_E - I_C = 1.07mA$