



---

DEPARTMENT OF ELECTRICAL & ELECTRONICS ENGINEERING

---

**END OF SEMESTER EXAMINATION -ACADEMIC YEAR 2020-2021**

**TRIMESTER I**

**GROUP: Y2 EPE**

**MODULE: EPE2165—ANALOG ELECTRONICS**

**DATE: 14/09/2021**

**TIME: 2 hours**


**MAX POINTS = 50 POINTS**

---

**INSTRUCTIONS**


- You have 2 hours to complete the exam. Be a smart test taker: if you get stuck on one problem go on to the next.
- This exam paper comprises 3 pages, excluding the title page. Please check that you have received all of them.
- This exam paper contains 3 questions. Answer only 2 questions as follows
  - QUESTION # 1 is COMPULSORY
  - Chose ONE (1) question from questions 2 and 3
  - If a candidate answers more than two questions, at the sole discretion of the grader, only two questions will be graded.
- Keep your answers short and to the point. Longer is not necessarily better as the number of written words is NOT a grading criterion and, in some case, longer answers may even make your answer abstruse.
- Write legibly. If the grader cannot read it, you will not get credit for it.
- Write all your answers in the answer booklet provided
- Do not forget to write your Registration Number
- No written materials allowed.
- Do not write any answers on this questions paper

1. (a) (5 points) **Figure 1** depicts an amplifier composed of a cascade of three stages. The amplifier is fed by a signal source with a source resistance of  $100\text{ k}\Omega$  and delivers its output into a load resistance of  $100\ \Omega$ . The first stage has a relatively high input resistance and a modest gain factor of 10. The second stage has a higher gain factor of 100 but a lower input resistance. Finally, the last, or output, stage has unity gain but a low output resistance. Calculate the overall gain of the amplifier. Express your answer in dB.

 

**FIGURE 1.** Three-stage amplifier


- (b) **Figure 2** represents a portion of battery-charger circuit for a battery with a voltage  $V_B$ . The sine-wave input  $v_S = 12\text{ V}(rms)$ , while the battery voltage varies from  $12\text{ V}$  to  $14\text{ V}$  from the discharged to fully charged states. The charging-source resistance  $R_S = 10\ \Omega$ . Assuming that  $D$  is an ideal diode, and  $R_C = 50\ \Omega$  is a current-controlling resistor established by the designer:

 


**FIGURE 2.** Battery-charger circuit

- i. (5 points) Sketch and label the voltage waveforms of the voltage across the diode and the current through the diode for  $V_B = 12\text{ V}$ .
  - ii. (5 points) What is the peak diode current?
- (c) An NMOS transistor is fabricated in a  $0.13\ \mu\text{m}$  CMOS process (i.e.,  $L_{min} = 0.13\ \mu\text{m}$ ) with  $L = 1.5L_{min}$ ,  $W = 1.3\ \mu\text{m}$ . The process technology is specified to have an oxide layer  $t_{ox} = 2.7\text{ nm}$ ,  $\mu_n = 400\text{ cm}^2\text{ V}^{-1}\text{ s}$  and  $V_{tn} = 0.4\text{ V}$

- i. (6 points) Find the oxide capacitance,  $C_{ox}$ , the process transconductance,  $k'_n$ , and the MOSFET transconductance parameter,  $k_n$ . The permittivity of the silicon dioxide,  $\epsilon_{ox} = 3.45 \times 10^{-11} F \cdot m^{-1}$
  - ii. (6 points) Find the overdrive voltage  $V_{OV}$  and the minimum value of  $V_{DS}$  required to operate the transistor in saturation at a current  $I_D = 100 \mu A$ . What gate-to-source voltage is required?
- (d) (6 points) For the NMOS transistor in **Figure 3**, determine the values of  $R_D$  and  $R_S$  so that the transistor operates at  $i_D = 0.4 mA$  and  $V_D = +0.5V$ . The NMOS transistor has  $V_t = 0.7V$ ,  $\mu_n C_{ox} = 100 \mu A/V^2$ ,  $L = 1 \mu m$ , and  $W = 32 \mu m$ . Neglect the channel-length modulation effect (i.e.,  $\lambda = 0$ ).

 

**FIGURE 3.** NMOS transistor

 

**FIGURE 4.** Common-emitter BJT circuit

- (e) For the common-emitter circuit in **Figure 4**,
    - i. (5 points) Calculate the base current, collector current, emitter currents, the  $V_{CE}$  voltage and the transistor power dissipation. Assume  $\beta = 200$  and  $V_{BE(on)} = 0.7V$
    - ii. (2 points) What is the mode of operation for the BJT in **Figure 4**? Briefly explain your answer.
2. The NMOS transistor in the circuit in **Figure 5** has  $V_{tn} = 0.5V$ ,  $k'_n = 400 \mu A V^{-2}$ ,  $W/L = 10$  and  $\lambda = 0$
- (a) (2 points) Find the the transistor's operating mode when  $V_D = +0.5V$
  - (b) (4 points) Find the required values of  $R_S$  and  $R_D$  to obtain  $i_D = 180 \mu A$  and  $V_D = +0.5V$ . Also, find the voltage  $V_S$  that results
  - (c) (4 points) What is the largest value to which  $R_D$  can be increased while the transistor remains in the saturation mode?

 


FIGURE 5

 


FIGURE 6

3. The BJT in **Figure 6** has  $\beta = 100$ ,  $V_{CEsat} = 0.3V$  and  $V_{B(on)} = 0.7V$ . Find  $V_E$ ,  $V_C$  and  $I_B$  and the transistor's mode of operation:
- (3 points) When  $V_B = 0V$
  - (3 points) When  $V_B = 3V$
  - (4 points) When  $V_B = 5V$