



UNIVERSITY OF RWANDA
COLLEGE OF SCIENCE & TECHNOLOGY
SCHOOL OF ENGINEERING
DEPARTMENT OF ELECTRICAL & ELECTRONICS ENGINEERING

DR. KIZITO NKURIKIYEYEU

EPE 2165—ANALOG ELECTRONICS

HOMEWORK #1—Signals and amplifiers

Question:	1	2	3	4	5	6	Total
Points:	10	10	20	20	15	25	100
Score:							

Issued on:

May 18, 2022

Due on:

May 26, 2022

- Ohm's law relates V , I , and R for a resistor. For each of the situations following, find the missing item:
 - (2½ points) $R = 1\text{ k}\Omega$, $V = 5\text{ V}$
 - (2½ points) $V = 5\text{ V}$, $I = 1\text{ mA}$
 - (2½ points) $R = 10\text{ k}\Omega$, $I = 0.1\text{ mA}$
 - (2½ points) $R = 100\ \Omega$, $V = 1\text{ V}$
- FIG 1 (a) shows a two-resistor voltage divider. Its function is to generate a voltage V_o (smaller than the power-supply voltage V_{DD}) at its output node X. The circuit looking back at node X is equivalent to that shown in FIG 1 (b). Observe that this is the Thevenin equivalent of the voltage-divider circuit.

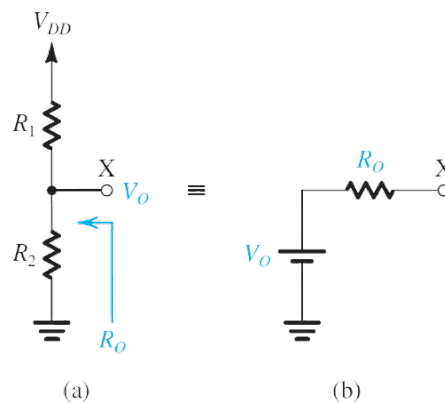


FIGURE 1. Two-resistor voltage divider.

- (5 points) Find expressions for V_o for $V_{DD} = 5\text{ V}$, $R_1 = R_2 = 1\text{ k}$
 - (5 points) Find expressions for R_o for $V_{DD} = 5\text{ V}$, $R_1 = R_2 = 1\text{ k}$
- (20 points) An amplifier has the following RMS¹ characteristics: $v_I = 100\text{ mV}$, $i_I = 100\ \mu\text{A}$, $v_o = 10\text{ V}$, $R_L = 100\ \Omega$. Find its the voltage, current, and power gains (A_v , A_i , and A_p , respectively) both as ratios and in dB
 - Suppose you are part of team that needs to design a voltage amplifier which will be driven from a signal source v_s with an amplitude of $v_s = 5\text{ mV}$ peak amplitude and a source resistance of $R_s = 10\text{ k}\Omega$. Assuming that the amplifier must supply a peak output of $v_o = 2\text{ V}$ across a $R_L = 1\text{ k}\Omega$ load ...
 - (5 points) What is the required voltage gain from the source to the load?
 - (5 points) If the peak current available from the source is $0.1\ \mu\text{A}$, what is the smallest input resistance allowed?

¹ Remember the root-mean-square (RMS) value of a voltage V_o is equal to $V_{RMS} = \frac{V_o}{\sqrt{2}}$



UNIVERSITY OF RWANDA

- (c) (5 points) For the design with the value of R_i obtained in question (b) above, find the overall current gain and power gain.
- (d) (5 points) If the amplifier power supply limits the peak value of the output open-circuit voltage to 3 V, what is the largest output resistance allowed?
5. A spectrum analyzer is used to measure a square a square-wave signal. The spectrum analyzer is a frequency-selective voltmeter and show its spectrum to contain adjacent components (spectrallines) at 98 kHz and 126 kHz of amplitudes 63 mV and 49 mV, respectively.
- (a) (5 points) For this signal, what would direct measurement of the fundamental show its frequency and amplitude to be?
- (b) (5 points) What is the RMS value of the fundamental?
- (c) (5 points) What are the peak-to-peak amplitude and period of the originating square wave?
6. An amplifier operating from $\pm 3V$ supplies provides a 2.2V peak sine wave across a $100\ \Omega$ load when provided with a 0.2 V peak input from which 1.0mA peak is drawn. The average current in each supply is measured to be 20 mA.
- (a) (5 points) Find the voltage gain of the amplifier
- (b) (5 points) Find the current gain of the amplifier
- (c) (5 points) Find the power gain of the amplifier and express it in decibels
- (d) (10 points) Find the supply power, amplifier dissipation, and amplifier efficiency.