



UNIVERSITY OF RWANDA
COLLEGE OF SCIENCE & TECHNOLOGY
SCHOOL OF ENGINEERING
DEPARTMENT OF ELECTRICAL & ELECTRONICS ENGINEERING

DR. KIZITO NKURIKIYEYEU

EPE 2165—ANALOG ELECTRONICS

HOMEWORK #3—MOSFETs

Question:	1	2	3	4	5	6	Total
Points:	20	10	20	10	20	20	100
Score:							

Issued on:
Due on:

June 29, 2022
July 7, 2022

- An NMOS transistor that is operated with a small v_{DS} is found to exhibit a resistance r_{DS} . By what factor will r_{DS} change in each of the following situations?
 - (5 points) v_{OV} is doubled.
 - (5 points) The device is replaced with another fabricated in the same technology but with double the width.
 - (5 points) The device is replaced with another fabricated in the same technology but with both the width and length doubled.
 - (5 points) The device is replaced with another fabricated in a more advanced technology for which the oxide thickness is halved and similarly for W and L (assume n remains unchanged)."
- (10 points) For a particular IC-fabrication process, the transconductance parameter $k' = 400 \mu A V^{-2}$ and $V_t = 0.5V$. In an application in which $v_{GS} = v_{DS} = V_{supply} = 1.8V$, a drain current of 2 mA is required of a device of minimum length of 0.18 μm . What value of channel width must the design use?
- (a) (10 points) For the circuit shown in **Figure 1a**, assuming that $\lambda = 0$, show that

$$V = V_t + \sqrt{\frac{2I}{k'_n W/L}} \tag{1}$$

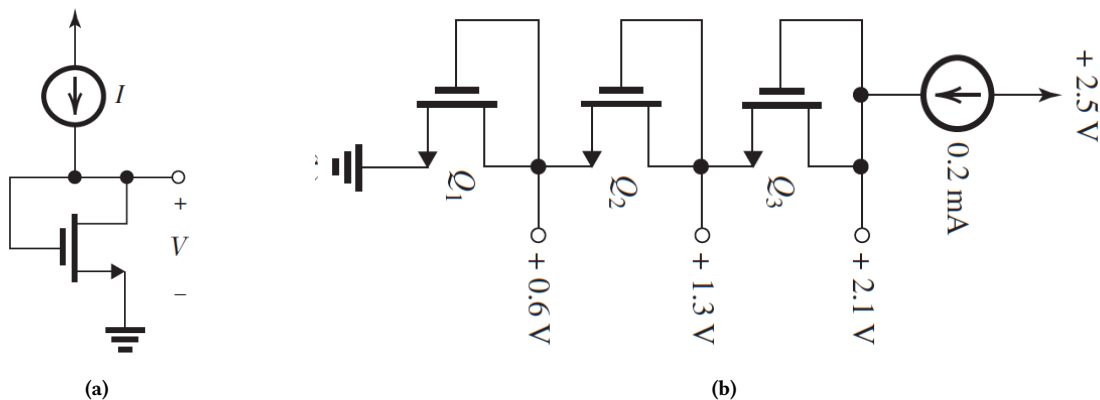


FIGURE 1

- (10 points) The MOSFETs **Figure 1b** have $V_t = 0.4V$, $k'_n = 0.4mA/V^2$ and $\lambda = 0$. Find ration W/L of each transistors (Q_1, Q_2 and Q_3) that are required to obtain the reference voltages ($V_1 = +0.6V, V_2 = +1.3V$ and $V_3 = 2.1V$) shown on the circuit.
- (10 points) **Figure 2a** has a drain current of 0.1 mA and a drain voltage of $V_D = 0.2V$. The MOSFET has $V_t = 0.2V, \mu_n C_{ox} = 400 \mu A V^{-2}, L = 0.5 \mu m$, and $W = 4 \mu m$. What is the the required values for R_S and R_D ? Assume $\lambda = 0$

5. The MOSFET in the circuit of **Figure 2b** has $V_t = 1V$ and $k_n = 2mA/V^2$, and the Early effect can be neglected.

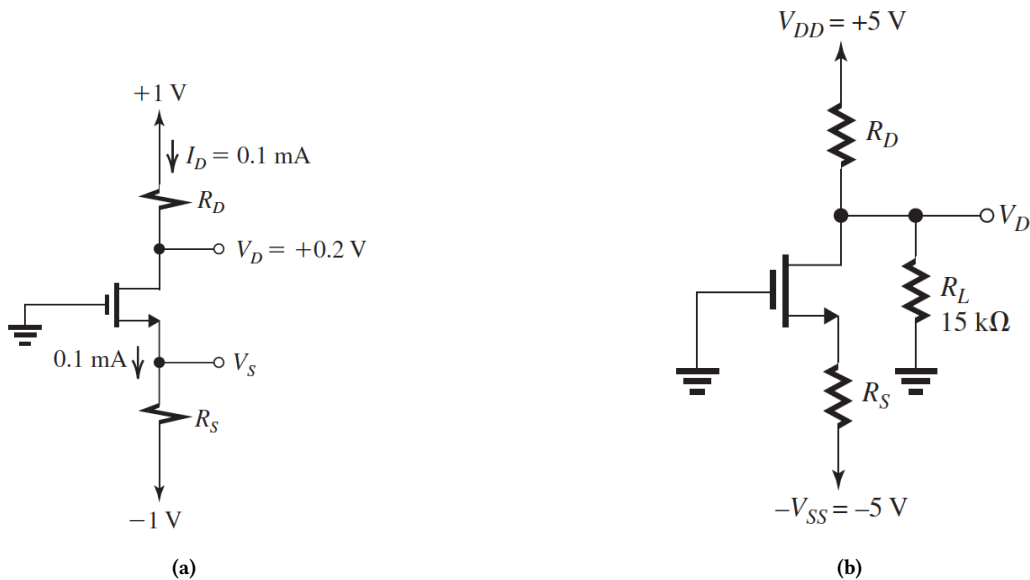


FIGURE 2

- (a) (10 points) Find the values of R_S and R_D that result in the MOSFET operating with an overdrive voltage of $0.5V$ and a drain voltage of $1.5V$. What is the resulting I_D value?
- (b) (5 points) If R_L is reduced from $15\text{ k}\Omega$, what does V_D become?
- (c) If R_L is disconnected, what does V_D become?
- (d) (5 points) With R_L disconnected, what is the largest R_D that can be used while the MOSFET is remaining in saturation?

6. The transistors in the circuit of **Figure 3** have $k_n = k_p = 2mA/V^2$ and $V_{tn} = -V_{tp} = 0.4V$. Find v_O for each of the following cases:

- (a) (5 points) $v_I = 0V$
 (b) (5 points) $v_I = 1V$
 (c) (5 points) $v_I = -1V$
 (d) (5 points) $v_I = -2V$

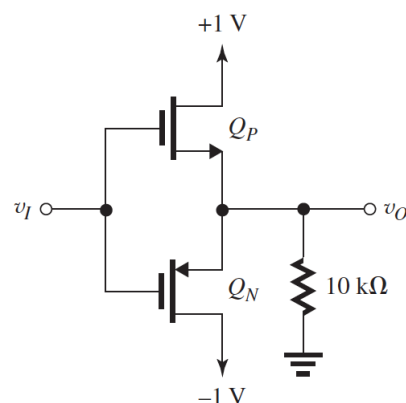


FIGURE 3