

<https://qirio.com/epe2165/>


## Circuit models for an amplifier

Kizito NKURIKIYEYEU,

Ph.D.

### Why circuit models?


- A **conceptual model** is a representation of a system and is used to communicate a set of concepts<sup>1</sup>
- **model** is the description of component's terminal behavior and ignores internal operation and components design (Fig. 1)

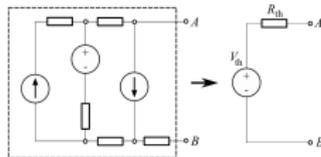

**FIG 1. Thevenin model of a circuit**<sup>2</sup>  
Any black box containing resistances only and voltage and current sources can be replaced by a Thévenin equivalent circuit consisting of an equivalent voltage source in series connection with an equivalent resistance.
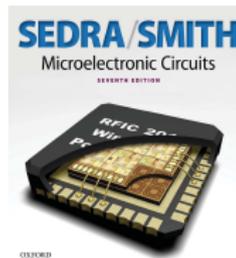
## Readings

- **Section 1.5 (pages 23-32)**
- **Example 1.3 on page 25**
- **Table 1.1. on page 28**
- **Section 1.5.5 on page 29**



- <sup>1</sup>Readings are based on Sedra & Smith (2014), Microelectronic Circuits 7th edition.
- <sup>2</sup>Bold reading section are mandatory. Other sections are suggested but not required readings


Kizito NKURIKIYEYEU, Ph.D.

Circuit models for an amplifier

May 16, 2022 1 / 6

### Voltage amplifier model


- Voltage-controlled with source  $v_s$  with a gain  $A_{vo}$ , an input resistance  $R_i$  and an output resistance  $R_o$
- Using the voltage-divider rule,  $v_o$  is represented by **Equation (1)**

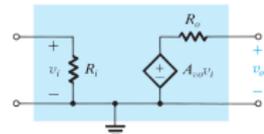

**FIG 2.** Circuit model for the voltage amplifier

$$v_o = V_{vo} v_i \frac{R_L}{R_L + R_o} \quad (1)$$

- Thus, the voltage gain can be expressed by **Equation (2)**

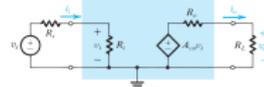

**FIG 3.** Voltage amplifier with input signal source

## Important remarks

- From Equation (2), the optimum gain is achieved when the output resistance  $R_o$  should be **much smaller** than the load resistance  $R_L$ .
- when designing an amplifier circuit in which  $R_L$  is known to vary over a certain range,  $R_o$  should be **much smaller than the lowest value of  $R_L$** .
- An ideal voltage amplifier is one with  $R_o = 0$ .
- Equation (2) shows that when  $R_L = \infty$ , then  $A_v = A_{vo}$ . Thus  $A_{vo}$  is the voltage gain of the unloaded amplifier, or the **open-circuit voltage gain**.
- When specifying the voltage gain of an amplifier, one must also specify the value of load resistance  $R_L$  at which this gain is measured or calculated.
- If a load resistance is not specified, it is normally assumed that the given voltage gain is the open-circuit gain  $A_{vo}$ .

## Important remarks

- The input resistance  $R_i$  reduces the actual value of the source signal  $v_s$  that reaches the input terminals of the amplifier (Equation (3))

$$v_i = v_s \frac{R_i}{R_i + R_s} \quad (3)$$

- Equation (3) shows that in order not to lose a much of the input signal in coupling the signal source to the amplifier input, the input resistance  $R_i$  must be much greater than the resistance of the signal source  $R_s$ , i.e.,  $R_i \gg R_s$
- When designing an amplifier circuit in which the source resistance vary over a certain range,  $R_i$  should be **much greater than the largest value of  $R_s$** .
- An ideal voltage amplifier is one with  $R_i = \infty$ . In this ideal case both the current gain and power gain become infinite
- The overall voltage gain ( $A = v_o/v_s$ ) is obtained by

## Cascaded amplifiers

- Real amplifiers are not ideal and they do not have infinite input impedance or zero output impedance.
- Cascading of amplifiers is used to solve this (Fig. 4).
  - First amplifier**—high  $R_i$ , medium  $R_o$
  - Last amplifier**—medium  $R_i$ , low  $R_o$
  - Aggregate**—high  $R_i$ , low  $R_o$

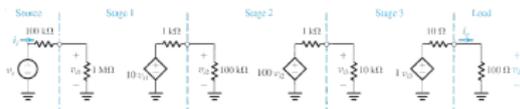


FIG 4. Three-stage amplifier

The first stage has a large input resistance ( $R_i = 1\text{M}\Omega$ ). The second stage achieves the required voltage gain. The final stage functions as a buffer amplifier, providing a relatively large input resistance and a low output resistance, much lower than  $R_L$ . It is this stage that enables connecting the amplifier to the 100  $\Omega$  load.

# The end