

Rectifier Circuits

Kizito NKURIKIYEYU,
Ph.D.

Rectifier Circuits

- The most important applications of diodes is in the design of rectifier circuits
- Rectifiers converts alternating current (AC) to DC current¹

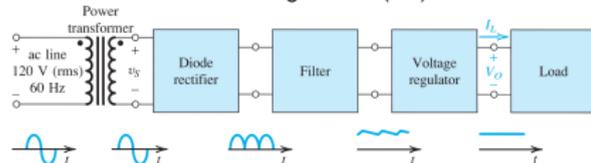


FIG 1. Block diagram of a dc power supply

The power supply is fed from the 120-V (rms) 60-Hz ac line, and it delivers a voltage V_O (usually in the range of 4 V to 20 V) to an electronic circuit represented by the load block. The dc voltage V_O is required to be as constant as possible in spite of variations in the ac line voltage and in the current drawn by the load.

Half-wave rectifier

- A half-wave rectifier utilizes alternate half-cycles of the input sinusoid
- If we use the constant voltage drop diode model in Fig. 2:

$$v_o = \begin{cases} 0, & \text{if } v_s < V_D \\ v_s - V_D & \text{otherwise} \end{cases} \quad (1)$$

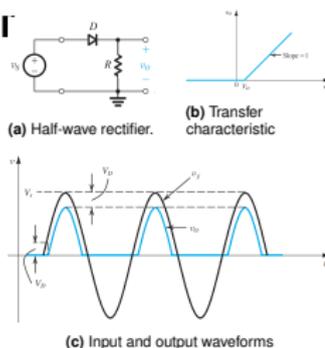


FIG 2. Characteristics of a half-wave rectifier

Half-wave rectifier

In selecting diodes for rectifier design, two important parameters must be specified

- **current-handling capability**—what is maximum forward current diode is expected to conduct?
- **peak inverse voltage (PIV)**—what is maximum reverse voltage it is expected to block without breakdown?
 - When $v_s < 0$, the diode will be cut off and v_o will be zero and PIV is equal to the peak of v_s (Equation (2))

$$PIV = V_s \quad (2)$$

- It is usually prudent, however, to select a diode that has a reverse breakdown voltage at least 50% greater than the expected PIV .

■ Note:

- It is possible to use the diode exponential model in describing rectifier operation; however, this requires too much work
- The rectifier does not work well for small input voltage (e.g.,

¹<https://www.physics-and-radio-electronics.com/electronic-devices-and-circuits/rectifier/halfwaverectifier.html>

Full-wave rectifier

Full-wave rectifier

- The full-wave rectifier utilizes both halves of the input sinusoid.
- The center-tapping of the transformer, allowing "reversal" of certain currents

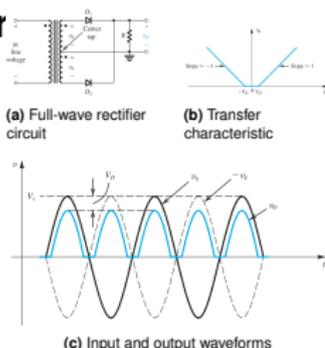


FIG 3. Full-wave rectifier utilizing a transformer with a center-tapped secondary winding

Kizito NKURIKIYEYEU, Ph.D.


Rectifier Circuits

June 22, 2022

4 / 18


Working principle

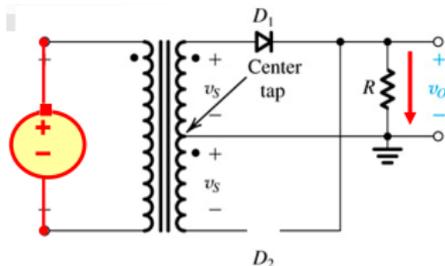When $v_s > 0$, D_1 conducts while D_2 will be reverse biased. The current through D_1 will flow through R and back to the center tap of the secondary.



Working principle

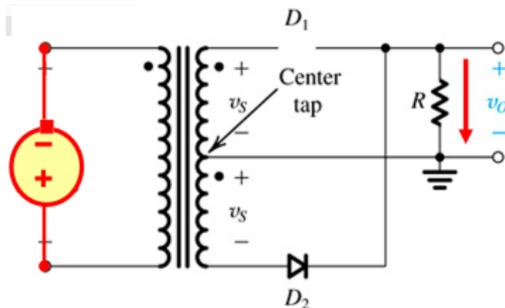When $v_s < 0$, the situation reverses: D_2 conducts while D_1 blocks



¹<https://www.physics-and-radio-electronics.com/electronic-devices-and-circuits/rectifier/fullwaverectifier.html>

Working principle

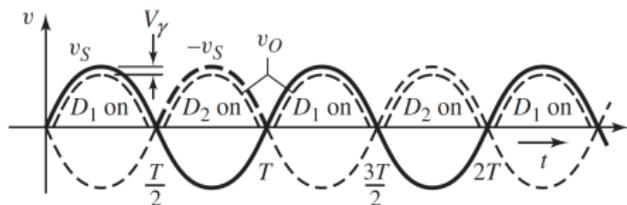


FIG 4. Full-wave rectifier working principle

When $v_s > V_D$, D_1 is on and D_2 is off. The output voltage is then $v_o = v_s - V_D$.
 When $v_s < -V_D$, then for $v_s < -V_D$ or $-v_s > V_D$, D_1 is off and D_2 is on. The output voltage is $v_o = -v_s - V_D$ ¹

Peak inverse voltage

- The direction of current flowing across load never changes (both halves of AC wave are rectified). The full-wave rectifier produces a more “energetic” waveform than half-wave
- During the positive half-cycle:
 - diode D_1 is conducting, and D_2 is cut off. The voltage at the cathode of D_2 is v_o , and that at its anode is $-v_s$.
 - The reverse voltage across D_2 is $v_o + v_s$, and reaches the maximum when v_o is at its peak value of $V_p = V_s - V_D$
 - The peak inverse voltage is approximately twice that for the case of the half-wave rectifier as shown in Equation (3)


$$PIV = 2V_s - V_D \quad (3)$$

¹Adapted from Neamen, D. (2009). Microelectronics Circuit Analysis and Design (4th ed.)


Bridge rectifier

Bridge rectifier

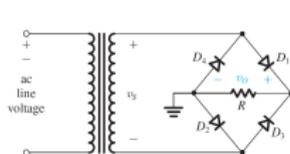- Provides electrical isolation between the input ac powerline and the rectifier output, but does not require a center-tapped secondary winding.
- Uses four diodes, compared to only two in the previous circuit.
- Its Peak inverse voltage $VIP = V_s - 2V_D - V_D = V_s - V_D$ and is about half the value for the full-wave rectifier with a center-tapped transformer.




(a) Bridge rectifier circuit

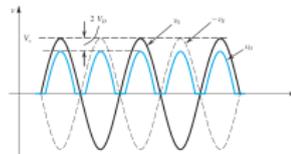

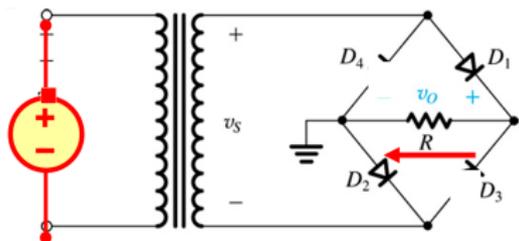(b) input and output waveforms



Working principles

- When the instantaneous source voltage $v_s > 0$, D_1 and D_2 conduct while D_3 and D_4 block
- In this case, the current passes from the source, then to D_1 , then to D_2 and return back to the source.




Working principles

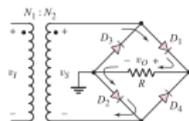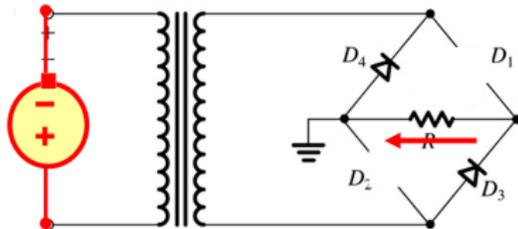
- When instantaneous source voltage is negative D_1 and D_2 block while D_3 and D_4 conduct
- In this case, the current passes from the source, then to D_3 , then to D_4 and return back to the source.



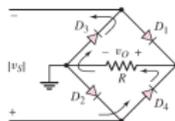(a) Current direction for a positive input cycle



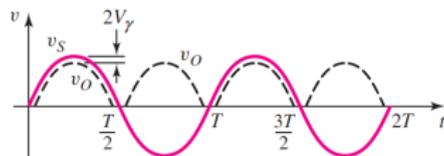(b) Current direction for a negative input cycle




(c) Input and output waveforms


FIG 6. A full-wave bridge rectifier

The Peak Rectifier

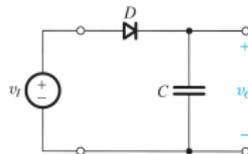- Pulsating nature of rectifier output makes unreliable dc supply.
- As such, a filter capacitor is employed to remove ripple.



(a) diode with a capacitor

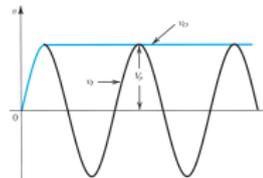

(b) Input and output assuming an ideal diode

FIG 7. A simple circuit used to illustrate the effect of a filter capacitor. Note that the circuit provides a dc voltage equal to the peak of the input sine wave. The circuit is therefore known as a *peak rectifier* or a *peak detector*

The Peak Rectifier

The peak rectifiers works in three steps:

- Step 1: The source voltage is positive, diode is ON—then capacitor charges.
- Step 2: The source voltage is reverse, diode is OFF—then capacitor cannot discharge
- Step 3: The source voltage is positive, diode is ON—then capacitor charges—thus, the capacitor maintains the existing voltage.
- This example is, of course, unrealistic because for any

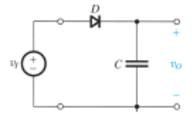


FIG 8. this is figure 1

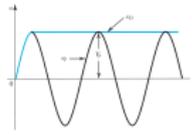


FIG 9. this is figure 2

Peak Rectifier with a load

- Practical situation where a load resistance R is connected across the capacitor C
- In this case, one must consider the discharging of capacitor across load.
- When diode is forward biased and conducting.
- When diode is reversed biased.

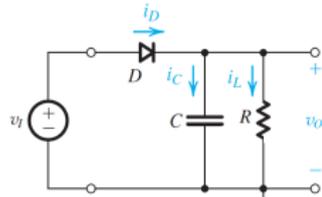


FIG 10. Rectifier with a filter capacitor and a load

$$v_o(t) = v_i(t) - v_D \quad (4)$$

Case 1: —when the diode is forward biased

- The load current i_L is given $i_L = v_o/R$
- The diode current is (Equation (6))

$$i_D = i_C + i_L = C \frac{dv_i}{dt} + i_L \quad (6)$$


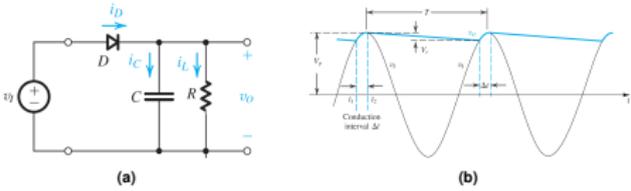


FIG 11. Peak rectifier with $v_i > 0$ for an ideal diode
Fig. 11b shows the steady-state input and output voltage under the

Case 2: —when the diode is reverse biased

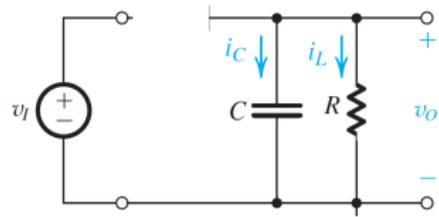- The diode current is $i_D = 0$
- The output voltage v_o is $v_o = Ri_L$
- The load current is $i_L = -i_C$



Full-wave peak rectifier.

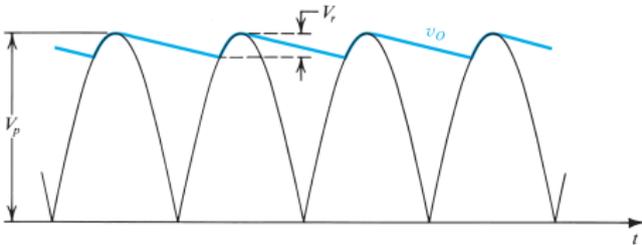


FIG 12. Waveforms in the full-wave peak rectifier.

The end