


<https://qiro.com/epe2165/>

Circuit models for an amplifier

Kizito NKURIKIYEYEU, Ph.D.

Readings

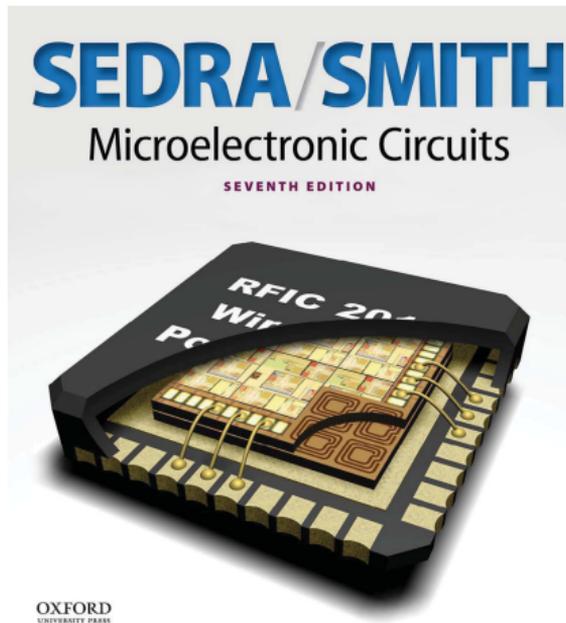- Section 1.5 (pages 23-32)
- Example 1.3 on page 25
- Table 1.1. on page 28
- Section 1.5.5 on page 29



¹ Readings are based on Sedra & Smith (2014), Microelectronic Circuits 7th edition.

² Bold reading section are mandatory. Other sections are suggested but not required readings

Why circuit models?

- A **conceptual model** is a representation of a system and is used to communicate a set of concepts¹
- **model** is the description of component's terminal behavior and ignores internal operation and components design (Fig. 1)

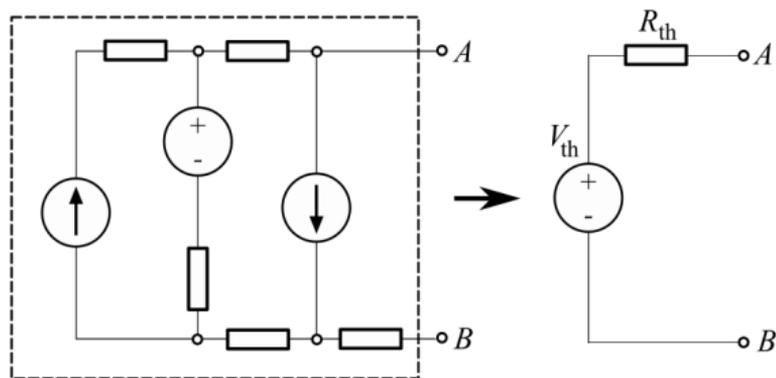


FIG 1. Thevenin model of a circuit²

Any black box containing resistances only and voltage and current sources can be replaced by a Thévenin equivalent circuit consisting of an equivalent voltage source in series connection with an equivalent resistance.

¹https://en.wikipedia.org/wiki/Conceptual_model

²https://en.wikipedia.org/wiki/Th%C3%A9venin%27s_theorem

Voltage amplifier model

- Voltage-controlled with source v_s with a gain A_{vo} , an input resistance R_i and an output resistance R_o
- Using the voltage-divider rule, v_o is represented by Equation (1)

$$v_o = A_{vo} v_i \frac{R_L}{R_L + R_o} \quad (1)$$

- Thus, the voltage gain can be expressed by Equation (2)

$$A_V \equiv \frac{v_o}{v_i} = A_{vo} \frac{R_L}{R_L + R_o} \quad (2)$$

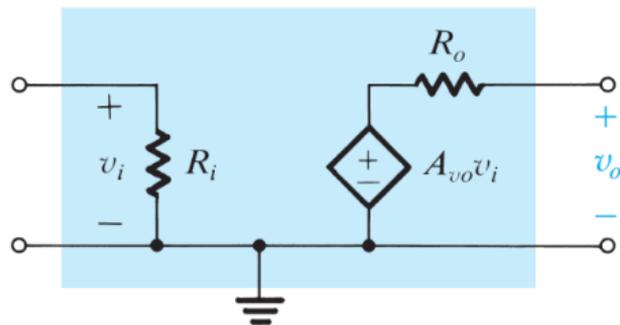


FIG 2. Circuit model for the voltage amplifier

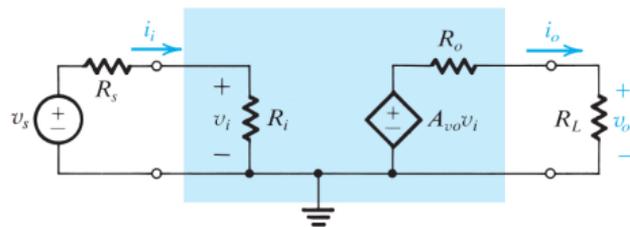


FIG 3. Voltage amplifier with input signal source

Important remarks

- From Equation (2), the optimum gain is achieved when the output resistance R_o should be much smaller than the load resistance R_L .
- when designing an amplifier circuit in which R_L is known to vary over a certain range, R_o should be much smaller than the lowest value of R_L .
- An ideal voltage amplifier is one with $R_o = 0$.
- Equation (2) shows that when $R_L = \infty$, then $A_V = A_{V0}$. Thus A_{V0} is the voltage gain of the unloaded amplifier, or the open-circuit voltage gain.
- When specifying the voltage gain of an amplifier, one must also specify the value of load resistance R_L at which this gain is measured or calculated.
- If a load resistance is not specified, it is normally assumed that the given voltage gain is the open-circuit gain A_{V0} .

Important remarks

- From Equation (2), the optimum gain is achieved when the output resistance R_o should be much smaller than the load resistance R_L .
- when designing an amplifier circuit in which R_L is known to vary over a certain range, R_o should be much smaller than the lowest value of R_L .
- An ideal voltage amplifier is one with $R_o = 0$.
- Equation (2) shows that when $R_L = \infty$, then $A_V = A_{V0}$. Thus A_{V0} is the voltage gain of the unloaded amplifier, or the open-circuit voltage gain.
- When specifying the voltage gain of an amplifier, one must also specify the value of load resistance R_L at which this gain is measured or calculated.
- If a load resistance is not specified, it is normally assumed that the given voltage gain is the open-circuit gain A_{V0} .

Important remarks

- From Equation (2), the optimum gain is achieved when the output resistance R_o should be much smaller than the load resistance R_L .
- when designing an amplifier circuit in which R_L is known to vary over a certain range, R_o should be much smaller than the lowest value of R_L .
- An ideal voltage amplifier is one with $R_o = 0$.
- Equation (2) shows that when $R_L = \infty$, then $A_V = A_{V0}$. Thus A_{V0} is the voltage gain of the unloaded amplifier, or the open-circuit voltage gain.
- When specifying the voltage gain of an amplifier, one must also specify the value of load resistance R_L at which this gain is measured or calculated.
- If a load resistance is not specified, it is normally assumed that the given voltage gain is the open-circuit gain A_{V0} .

Important remarks

- From Equation (2), the optimum gain is achieved when the output resistance R_o should be much smaller than the load resistance R_L .
- when designing an amplifier circuit in which R_L is known to vary over a certain range, R_o should be much smaller than the lowest value of R_L .
- An ideal voltage amplifier is one with $R_o = 0$.
- Equation (2) shows that when $R_L = \infty$, then $A_v = A_{vo}$. Thus A_{vo} is the voltage gain of the unloaded amplifier, or the open-circuit voltage gain.
- When specifying the voltage gain of an amplifier, one must also specify the value of load resistance R_L at which this gain is measured or calculated.
- If a load resistance is not specified, it is normally assumed that the given voltage gain is the open-circuit gain A_{vo} .

Important remarks

- From Equation (2), the optimum gain is achieved when the output resistance R_o should be much smaller than the load resistance R_L .
- when designing an amplifier circuit in which R_L is known to vary over a certain range, R_o should be much smaller than the lowest value of R_L .
- An ideal voltage amplifier is one with $R_o = 0$.
- Equation (2) shows that when $R_L = \infty$, then $A_v = A_{vo}$. Thus A_{vo} is the voltage gain of the unloaded amplifier, or the open-circuit voltage gain.
- When specifying the voltage gain of an amplifier, one must also specify the value of load resistance R_L at which this gain is measured or calculated.
- If a load resistance is not specified, it is normally assumed that the given voltage gain is the open-circuit gain A_{vo} .

Important remarks

- From Equation (2), the optimum gain is achieved when the output resistance R_o should be much smaller than the load resistance R_L .
- when designing an amplifier circuit in which R_L is known to vary over a certain range, R_o should be much smaller than the lowest value of R_L .
- An ideal voltage amplifier is one with $R_o = 0$.
- Equation (2) shows that when $R_L = \infty$, then $A_v = A_{vo}$. Thus A_{vo} is the voltage gain of the unloaded amplifier, or the open-circuit voltage gain.
- When specifying the voltage gain of an amplifier, one must also specify the value of load resistance R_L at which this gain is measured or calculated.
- If a load resistance is not specified, it is normally assumed that the given voltage gain is the open-circuit gain A_{vo} .

Important remarks

- The input resistance R_i reduces the actual value of the source signal v_s that reaches the input terminals of the amplifier (Equation (3))

$$v_i = v_s \frac{R_i}{R_i + R_s} \quad (3)$$

- Equation (3) shows that in order not to lose a much of the input signal in coupling the signal source to the amplifier input, the input resistance R_i must be much greater than the resistance of the signal source R_s , i.e., $R_i \gg R_s$
- When designing an amplifier circuit in which the source resistance vary over a certain range, R_i should be much greater than the largest value of R_s .
- An ideal voltage amplifier is one with $R_i = \infty$. In this ideal case both the current gain and power gain become infinite
- The overall voltage gain ($A = v_o/v_s$) is obtained by combining Equation (2) and Equation (3) as shown in Equation (4)

$$\frac{v_o}{v_s} = A_{V_{v_o}} \frac{R_i}{R_i + R_s} \cdot \frac{R_L}{R_L + R_o} \quad (4)$$

Important remarks

- The input resistance R_i reduces the actual value of the source signal v_s that reaches the input terminals of the amplifier (Equation (3))

$$v_i = v_s \frac{R_i}{R_i + R_s} \quad (3)$$

- Equation (3) shows that in order not to lose a much of the input signal in coupling the signal source to the amplifier input, the input resistance R_i must be much greater than the resistance of the signal source R_s , i.e., $R_i \gg R_s$
- When designing an amplifier circuit in which the source resistance vary over a certain range, R_i should be much greater than the largest value of R_s .
- An ideal voltage amplifier is one with $R_i = \infty$. In this ideal case both the current gain and power gain become infinite
- The overall voltage gain ($A = v_o / v_s$) is obtained by combining Equation (2) and Equation (3) as shown in Equation (4)

$$\frac{v_o}{v_s} = A_{V_{v_o}} \frac{R_i}{R_i + R_s} \cdot \frac{R_L}{R_L + R_o} \quad (4)$$

Important remarks

- The input resistance R_i reduces the actual value of the source signal v_s that reaches the input terminals of the amplifier (Equation (3))

$$v_i = v_s \frac{R_i}{R_i + R_s} \quad (3)$$

- Equation (3) shows that in order not to lose a much of the input signal in coupling the signal source to the amplifier input, the input resistance R_i must be much greater than the resistance of the signal source R_s , i.e., $R_i \gg R_s$
- When designing an amplifier circuit in which the source resistance vary over a certain range, R_i should be much greater than the largest value of R_s .
- An ideal voltage amplifier is one with $R_i = \infty$. In this ideal case both the current gain and power gain become infinite
- The overall voltage gain ($A = v_o / v_s$) is obtained by combining Equation (2) and Equation (3) as shown in Equation (4)

$$\frac{v_o}{v_s} = A_{V_{v_o}} \frac{R_i}{R_i + R_s} \cdot \frac{R_L}{R_L + R_o} \quad (4)$$

Important remarks

- The input resistance R_i reduces the actual value of the source signal v_s that reaches the input terminals of the amplifier (Equation (3))

$$v_i = v_s \frac{R_i}{R_i + R_s} \quad (3)$$

- Equation (3) shows that in order not to lose a much of the input signal in coupling the signal source to the amplifier input, the input resistance R_i must be much greater than the resistance of the signal source R_s , i.e., $R_i \gg R_s$
- When designing an amplifier circuit in which the source resistance vary over a certain range, R_i should be much greater than the largest value of R_s .
- An ideal voltage amplifier is one with $R_i = \infty$. In this ideal case both the current gain and power gain become infinite
- The overall voltage gain ($A = v_o / v_s$) is obtained by combining Equation (2) and Equation (3) as shown in Equation (4)

$$\frac{v_o}{v_s} = A_{V_{v_o}} \frac{R_i}{R_i + R_s} \cdot \frac{R_L}{R_L + R_o} \quad (4)$$

Important remarks

- The input resistance R_i reduces the actual value of the source signal v_s that reaches the input terminals of the amplifier (Equation (3))

$$v_i = v_s \frac{R_i}{R_i + R_s} \quad (3)$$

- Equation (3) shows that in order not to lose a much of the input signal in coupling the signal source to the amplifier input, the input resistance R_i must be much greater than the resistance of the signal source R_s , i.e., $R_i \gg R_s$
- When designing an amplifier circuit in which the source resistance vary over a certain range, R_i should be much greater than the largest value of R_s .
- An ideal voltage amplifier is one with $R_i = \infty$. In this ideal case both the current gain and power gain become infinite
- The overall voltage gain ($A = v_o/v_s$) is obtained by combining Equation (2) and Equation (3) as shown in Equation (4)

$$\frac{v_o}{v_s} = A_{V_{vo}} \frac{R_i}{R_i + R_s} \cdot \frac{R_L}{R_L + R_o} \quad (4)$$

Cascaded amplifiers

- Real amplifiers are not ideal and they do not have infinite input impedance or zero output impedance.
- Cascading of amplifiers is used to solve this (Fig. 4).
 - **First amplifier** —high R_i , medium R_o
 - **Last amplifier** —medium R_i , low R_o
 - **Aggregate** —high R_i , low R_o

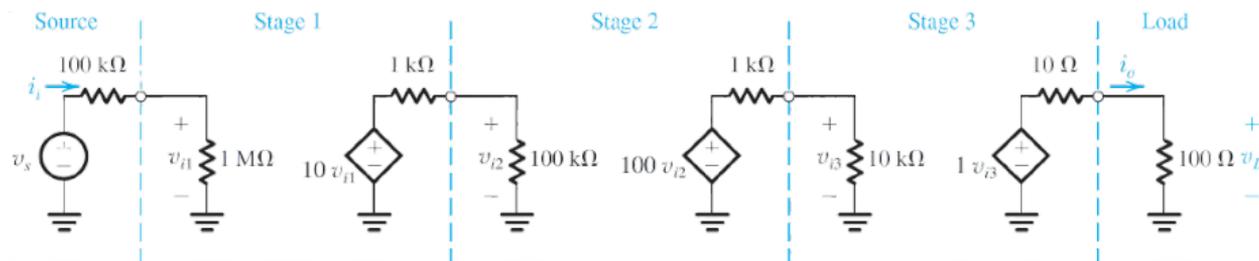


FIG 4. Three-stage amplifier

The first stage has a large input resistance ($R_i = 1\text{M}\Omega$). The second stage achieves the required voltage gain. The final stage functions as a buffer amplifier, providing a relatively large input resistance and a low output resistance, much lower than R_L . It is this stage that enables connecting the amplifier to the 100Ω load.

The end