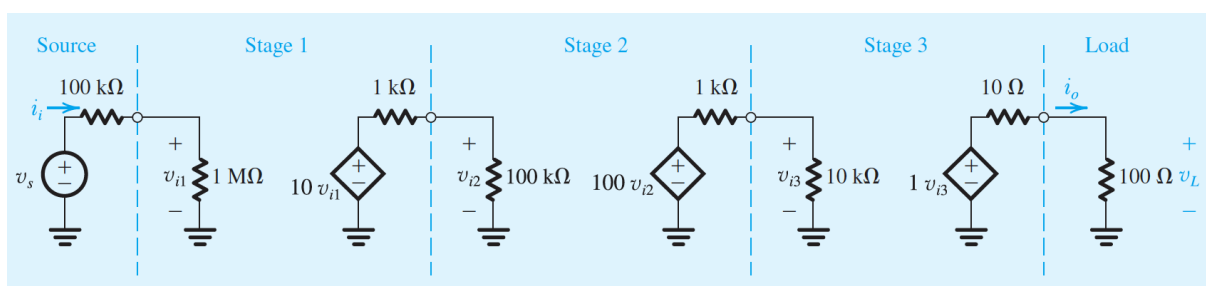


# EPE2165—Analog Electronic Exam #1


14 July, 2022

- (10 points) **Figure 1** depicts an amplifier composed of a cascade of three stages. The amplifier is fed by a signal source with a source resistance of  $100\text{ k}\Omega$  and delivers its output into a load resistance of  $100\ \Omega$ . The first stage has a relatively high input resistance and a modest gain factor of 10. The second stage has a higher gain factor of 100 but a lower input resistance. Finally, the last, or output, stage has unity gain but a low output resistance. Calculate the overall gain of the amplifier. Express your answer in dB.



**FIGURE 1.** Three-stage amplifier

- Consider a half-wave rectifier circuit shown in **Figure 2**. Let  $v_s$  be a sinusoid with 10V

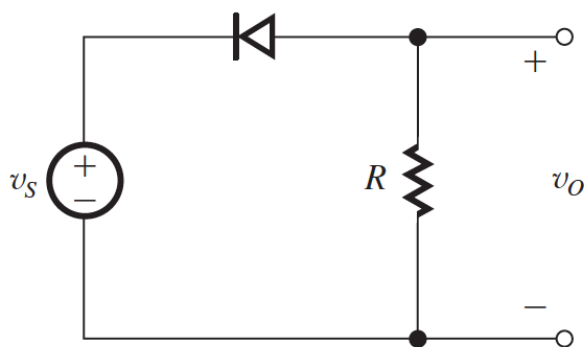

**FIGURE 2**

peak amplitude, and let  $R = 1\text{ k}\Omega$ . Use the constant-voltage-drop diode model with  $V_D = 0.7\text{ V}$  and:

- (5 points) Sketch the transfer characteristic.
- (5 points) Sketch the waveform of  $v_O$ .
- (5 points) Find the peak current in the diode.
- (5 points) Find the PIV of the diode

3. The transistors in the circuit of **Figure 3** have  $k_n = k_p = 2\text{mA/V}^2$  and  $V_{tn} = -V_{tp} = 0.4\text{V}$ . Find  $v_O$  for each of the following cases:

- (a) (5 points)  $v_I = 0\text{V}$
- (b) (5 points)  $v_I = 1\text{V}$
- (c) (5 points)  $v_I = -1\text{V}$
- (d) (5 points)  $v_I = -2\text{V}$

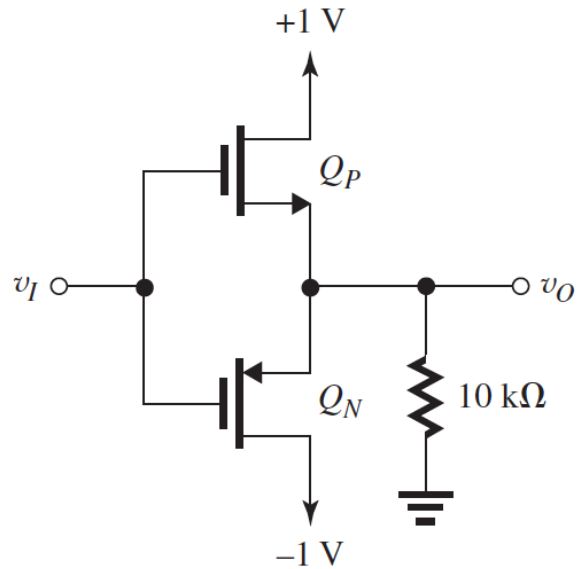


FIGURE 3