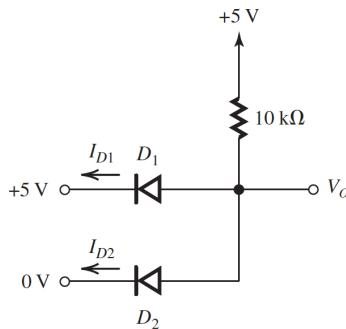


# EPE2165—Exam #1


July 26, 2022

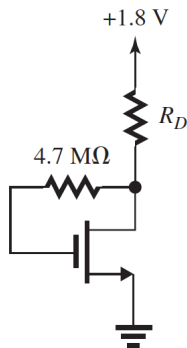1. (15 points) For the circuits shown in **Figure 1**, find the output voltage  $v_o$  and the diode currents  $I_{D1}$  and  $I_{D2}$ . Model a conducting diode as a constant voltage drop of 0.7 V.

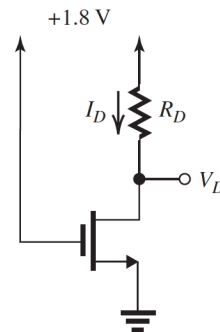


**FIGURE 1**

2. (15 points) The MOSFET in **Figure 2** has  $V_t = 0.4V$ ,  $k'_n = 0.4 \text{ mA V}^{-2}$ ,  $\lambda = 0$  and  $L = 0.4 \mu\text{m}$ . Find the values of  $W$  and  $R_D$  to operate it at  $I_D = 0.2 \text{ mA}$  and  $V_D = 0.6V$



**FIGURE 2**



**FIGURE 3**

3. (20 points) The MOSFET in **Figure 3** has  $V_t = 0.5V$ ,  $k'_n = 0.4 \text{ mA V}^{-2}$ ,  $V_A = 10V$  and  $W/L = 10$ . Find the value of  $R_D$ ,  $I_D$  and the incremental drain-to-source resistance  $R_{DS}$  that results in  $V_D = 0.1V$