



UNIVERSITY OF RWANDA
COLLEGE OF SCIENCE & TECHNOLOGY
SCHOOL OF ENGEERING
DEPARTMENT OF ELECTRICAL & ELECTRONICS ENGINEERING

KIZITO NKURIKIYEYEU, PHD

EPE 2165—ANALOG ELECTRONICS

SOLUTION #—1: DIODE CIRCUITS

July 26, 2022

4.1

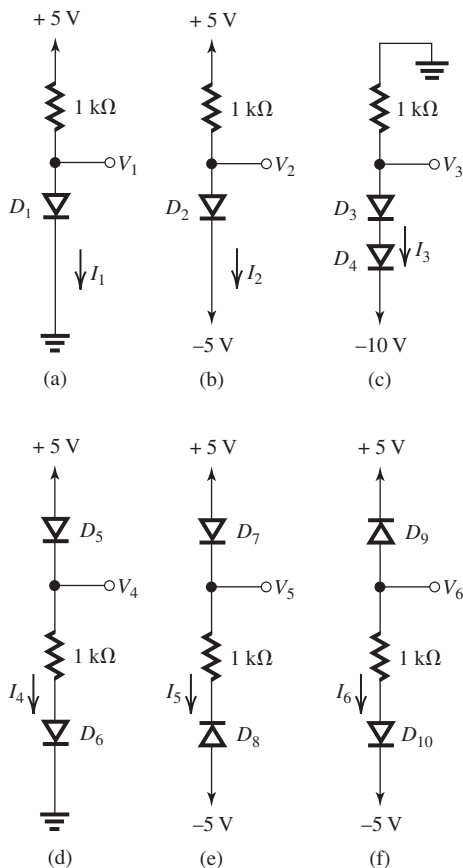


Figure 4.1.1

(a) Since the anode of D_1 is connected to +5 V through the 1-k Ω resistor, and the cathode is connected to ground, D_1 conducts and, being ideal,

has a zero voltage drop, thus

$$V_1 = 0 \text{ V}$$

$$I_1 = \frac{5 - 0}{1 \text{ k}\Omega} = 5 \text{ mA}$$

(b) Here the situation is similar to that in (a) except that the cathode is connected to -5 V. Thus, diode D_2 conducts and, being ideal, exhibits zero voltage drop, thus

$$V_2 = -5 \text{ V}$$

$$I_2 = \frac{5 - (-5)}{1 \text{ k}\Omega} = 10 \text{ mA}$$

(c) Diodes D_3 and D_4 are connected in series in the same direction with the cathode of D_4 connected to -10 V and the anode of D_3 to ground through the 1-k Ω resistance. Thus, D_3 and D_4 will conduct and, being ideal, will have zero voltage drops, resulting in

$$V_3 = -10 \text{ V}$$

$$I_3 = \frac{0 - (-10)}{1 \text{ k}\Omega} = 10 \text{ mA}$$

(d) Diodes D_5 and D_6 are connected in series in the same direction and since the anode of D_5 is connected to +5 V and the cathode of D_6 to ground, the diodes will conduct and exhibit zero voltage drops, resulting in

$$V_4 = +5 \text{ V}$$

$$I_4 = \frac{5}{1 \text{ k}\Omega} = 5 \text{ mA}$$

(e) Here diode D_7 is polarized to conduct while the series diode D_8 is not (its anode is at -5 V and

its cathode is connected through the 1-kΩ resistor and D_7 to +5 V). Thus

$$I_5 = 0$$

However, since D_7 is polarized to conduct, it will conduct a minute current that flows through the meter connected to measure V_5 . The conducting D_7 will exhibit a zero voltage drop and thus

$$V_5 = +5 - 0 = +5 \text{ V}$$

(f) Here D_9 is polarized to not conduct, thus

$$I_6 = 0$$

Diode D_{10} , however, is connected to conduct and it will conduct a very small current that flows through the meter connected to measure V_6 . The resulting voltage across D_{10} will be zero and the voltage across the 1-kΩ resistor will be negligibly small, thus

$$V_6 = -5 \text{ V}$$

4.2

The circuit with all currents and voltages indicated is shown in Fig. 4.2.2 (refer Figure below).

Our analysis proceeded as follows: Diode D_1 , with its anode connected to ground and its cathode connected to -8 V through R_1 , must conduct. Thus, its cathode will be at 0 V , which enables us to determine the current through R_1 as

$$I_{R1} = \frac{0 - (-8)}{R_1} = \frac{8}{1} = 8 \text{ mA}$$

Next, we assume that D_2 will be conducting because its cathode is at 0 V and its anode is connected to $+8 \text{ V}$ through R_2 . Thus, the current in R_2 can now be found as

$$I_{R2} = \frac{8 - 0}{2} = 4 \text{ mA}$$

Now, since I_{R1} (8 mA) is greater than I_{R2} (4 mA), then D_1 and D_2 both conduct. Now, noting that succeeding resistances are progressively larger, assume that D_3 and D_4 also conduct, and then their anode and cathode voltages will all be zero volts. Thus

$$I_{R3} = \frac{0 - (-8)}{4} = 2 \text{ mA}$$

and

$$I_{R4} = \frac{8 - 0}{8} = 1 \text{ mA}$$

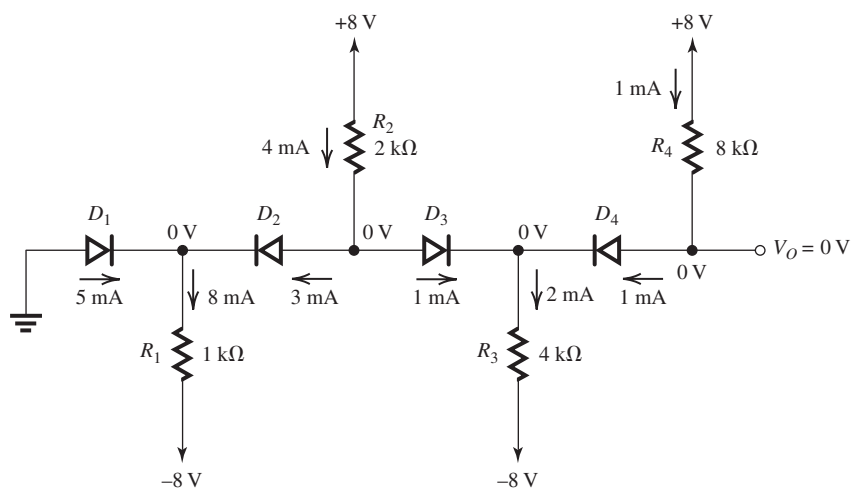


Figure 4.2.2

Thus, overall:

$$\begin{aligned} I_{D4} &= I_{R4} = 1 \text{ mA} \\ I_{D3} &= I_{R3} - I_{D4} = 2 - 1 = 1 \text{ mA} \\ I_{D2} &= I_{R2} - I_{D3} = 4 - 1 = 3 \text{ mA} \\ I_{D1} &= I_{R1} - I_{D2} = 8 - 3 = 5 \text{ mA} \end{aligned}$$

and

$$V_O = 0 \text{ V}$$

4.3

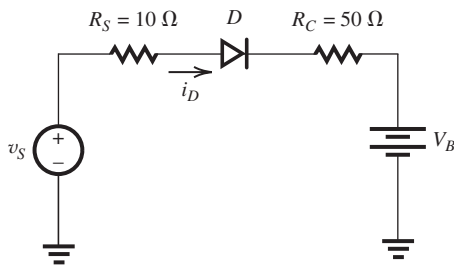


Figure 4.3.1

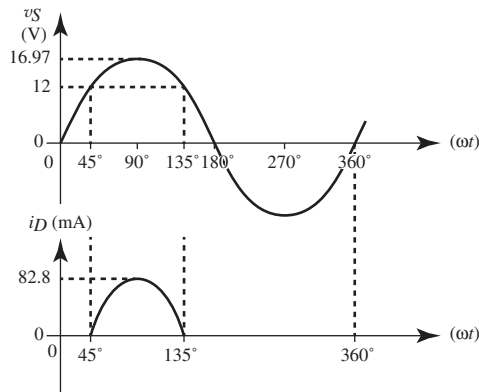


Figure 4.3.2

For a battery voltage V_B and an ideal diode, the diode current is

$$\begin{aligned} i_D &= \frac{v_S - V_B}{R_S + R_C} \\ &= \frac{\hat{V}_S \sin \omega t - V_B}{10 + 50} \end{aligned}$$

where

$$\hat{V}_S = \sqrt{2} \times 12 = 16.97 \text{ V}$$

Thus, for $V_B = 12 \text{ V}$,

$$i_D = \frac{16.97 \sin \omega t - 12}{60 \Omega}$$

which has a peak value of

$$\hat{i}_D = \frac{16.97 - 12}{60} = 82.8 \text{ mA}$$

The diode begins to conduct (and ceases to conduct) when $16.97 \sin \omega t = 12 \text{ V}$ or $\sin \omega t = 12/16.97 = 0.707$, which correspond to an angle $\theta = \frac{\pi}{4} = 45^\circ$. The average value of i_D can be computed as

$$\begin{aligned} i_{D|av} &= \frac{1}{2\pi} \int_{\pi/4}^{3\pi/4} (16.97 \sin \theta - 12) d\theta / 60 \\ &= \frac{1}{2\pi \times 60} [-16.97 \cos \theta - 12\theta]_{\pi/4}^{3\pi/4} \\ &= 13.7 \text{ mA} \end{aligned}$$

For $V_B = 14 \text{ V}$,

$$\text{Peak current} = \frac{16.97 - 14}{60 \Omega} = 49.5 \text{ mA}$$

Conduction begins when $16.97 \sin \omega t = 14$, or $\sin \omega t = \frac{14}{16.97} = 0.825$, or $\omega t = 55.6^\circ$. Thus,

$$\begin{aligned} \text{Average current} &= \frac{1}{2\pi} \int_{55.6^\circ}^{180^\circ - 55.6^\circ} (16.97 \sin \theta - 14) d\theta / 60 \\ &= \frac{1}{2\pi \times 60} [-16.97 \cos \theta - 14\theta]_{55.6^\circ}^{124.4^\circ} \\ &= 6.3 \text{ mA} \end{aligned}$$

4.4

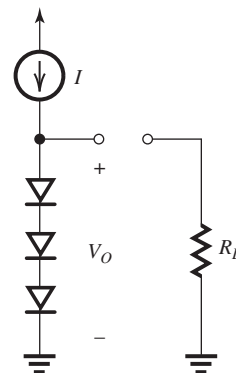


Figure 4.4.1

$$V_O = 3V_D$$

To obtain $V_O = 2.4 \text{ V}$, we need to establish

$$V_D = 0.8 \text{ V}$$

This is achieved when I is

$$\begin{aligned}
 I &= I_S e^{V_D/V_T} \\
 &= 10^{-16} e^{0.8/0.025} \\
 &\simeq 7.9 \text{ mA}
 \end{aligned}$$

If R_L is connected and it draws a current of 1 mA, the current in the diodes will be reduced by 1 mA, to 6.9 mA, thus V_D becomes

$$\begin{aligned}
 V_D &= V_T \ln(6.9 \times 10^{-3}/10^{-16}) \\
 &= 0.797 \text{ V}
 \end{aligned}$$

and V_O becomes

$$V_O = 3 \times 0.797 = 2.39 \text{ V}$$

Thus, V_O decreases by only 10 mV. Without R_L connected, since the diodes are fed with a constant current I , a change in temperature causes the voltage across each diode to change by $-2 \text{ mV}/^\circ\text{C}$. Thus, a temperature increase of 20°C causes V_D to decrease by $2 \times 20 = 40 \text{ mV}$ and causes V_O to decrease by 120 mV.

4.5

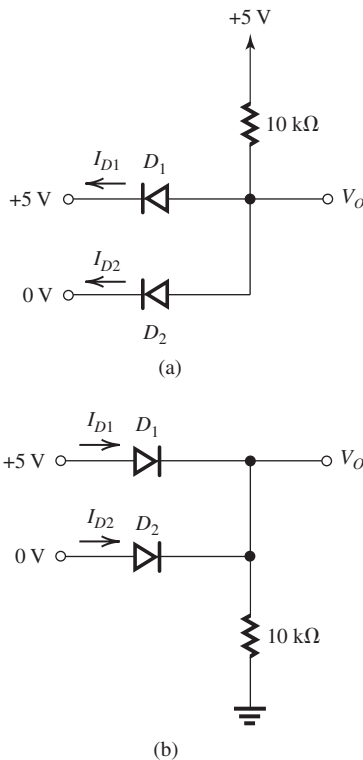


Figure 4.5.1

(a) For the circuit in Fig. 4.5.1(a), diode D_1 will be cut off while D_2 will conduct, causing the output voltage to become

$$V_O = 0 + V_{D2} = 0.7 \text{ V}$$

Thus, D_1 has a 4.3-V reverse bias, which keeps it cut off. Thus,

$$I_{D1} = 0$$

and

$$I_{D2} = \frac{5 - 0.7}{10} = 0.43 \text{ mA}$$

(b) For the circuit in Fig. 4.5.1(b), diode D_2 will be cut off while D_1 will conduct, causing V_O to become

$$V_O = 5 - V_{D1} = 5 - 0.7 = 4.3 \text{ V}$$

Thus, D_2 will have a reverse-bias voltage of 4.3 V, which keeps it in the cut-off mode,

$$I_{D2} = 0$$

The current in D_1 can be found as

$$I_{D1} = \frac{V_O}{10 \text{ k}\Omega} = \frac{4.3}{10} = 0.43 \text{ mA}$$

4.6

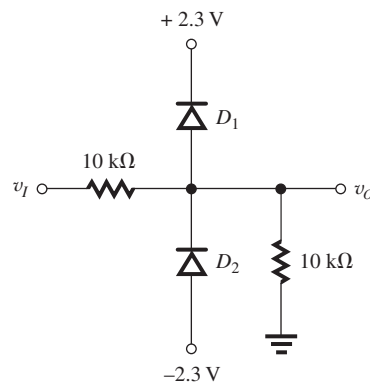


Figure 4.6.1

When v_O reaches +3 V, D_1 conducts and v_O remains at the +3-V level irrespective of the value of v_I . Thus, the upper limiting level is +3 V. v_O reaches +3 V when v_I is +6 V (because of the voltage divider comprised of the two 10-k Ω resistors), thus the upper input threshold voltage is +6 V.

A similar situation occurs in the negative direction: When v_O reaches -3 V , D_2 conducts and v_O remains at the -3-V level irrespective of the value of v_i . Thus, the lower limiting level is -3 V . v_O reaches -3 V when v_i reaches -6 V , thus the lower input threshold is -6 V .

In between the two threshold levels (i.e., for $-6\text{ V} \leq v_i \leq +6\text{ V}$), both D_1 and D_2 will be off and

$$v_O = \frac{10}{10 + 10} v_i = 0.5v_i$$

Thus, the limiter gain K is

$$K = 0.5\text{ V/V}$$

Figure 4.6.2 shows the transfer characteristic of the limiter.

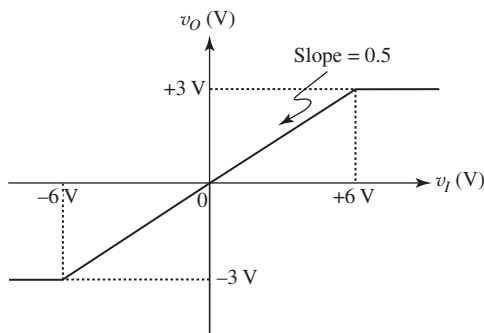


Figure 4.6.2

For $v_i = +12\text{ V}$, v_O will be $+3\text{ V}$, thus

$$i_I = \frac{12 - 3}{10\text{ k}\Omega} = 0.9\text{ mA}$$

4.7

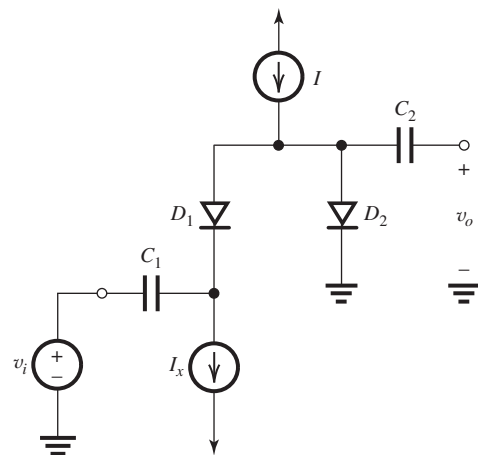


Figure 4.7.1

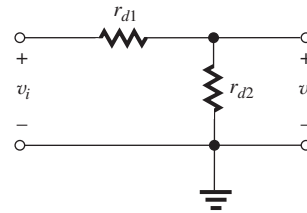


Figure 4.7.2

The dc currents in D_1 and D_2 are

$$I_{D1} = I_x$$

$$I_{D2} = I - I_{D1} = I - I_x$$

Thus, the small-signal resistances of D_1 and D_2 are

$$r_{d1} = \frac{V_T}{I_x}$$

$$r_{d2} = \frac{V_T}{I - I_x}$$

The small-signal equivalent circuit is shown in Fig. 4.7.2 from which we can find v_o/v_i as

$$\begin{aligned} \frac{v_o}{v_i} &= \frac{r_{d2}}{r_{d2} + r_{d1}} \\ &= \frac{V_T/(I - I_x)}{\frac{V_T}{I - I_x} + \frac{V_T}{I_x}} \end{aligned}$$

Thus,

$$\frac{v_o}{v_i} = \frac{I_x}{I}$$

For $I = 1\text{ mA}$,

$$\frac{v_o}{v_i} = I_x$$

where I_x is in mA.

To obtain the given values of v_o/v_i , we need the corresponding values of I_x as follows:

v_o/v_i	0	0.2	0.5	1.0
I_x (mA)	0	0.2	0.5	1.0

This circuit is a signal attenuator whose transfer ratio is linearly controlled by the current I_x .

4.8

Figure 4.8.1 shows the circuit.

$$\begin{aligned} V_O &= 4V_D \\ \Rightarrow V_D &= \frac{3.0}{4} = 0.75\text{ V} \end{aligned}$$

Now, for the available diode, we have

$$0.1\text{ mA} = I_S e^{0.7/0.025} \tag{1}$$

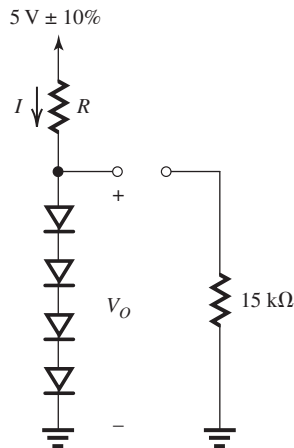


Figure 4.8.1

Thus, the required current I can be found from

$$I = I_S e^{0.75/0.025} \quad (2)$$

Dividing Eq. (2) by Eq. (1) yields

$$I = 0.1 \times e^{0.05/0.025} = 0.74 \text{ mA}$$

The required value of R can now be found from

$$I = \frac{5 - V_O}{R}$$

$$0.74 = \frac{5 - 3}{R}$$

$$\Rightarrow R = 2.7 \text{ k}\Omega$$

At a current $I_D = 0.74 \text{ mA}$, each diode has a small-signal resistance of

$$r_d = \frac{V_T}{I_D} = \frac{25 \text{ mV}}{0.74 \text{ mA}} = 33.8 \Omega$$

and the string of four diodes has an incremental (small-signal) resistance of

$$r = 4r_d = 4 \times 33.8 = 135 \Omega$$

With the supply voltage changing by $\pm 10\%$ —that is, by $\pm 0.5 \text{ V}$ —we can use the voltage divider comprised of the diode string (with a total resistance $r = 135 \Omega$) and the resistance R to determine the corresponding change in V_O as

$$\Delta V_O = \pm 0.5 \times \frac{0.135}{0.135 + 2.7}$$

$$= \pm 23.8 \text{ mV}$$

or $\pm 0.8\%$.

This implies a change of $\pm \frac{23.8}{4} \simeq \pm 6 \text{ mV}$ across each diode, which is small enough for the small-signal model to be applicable.

If a load resistance $R_L = 15 \text{ k}\Omega$ is connected to V_O , we can determine the approximate change ΔV_O in V_O as follows. First, assume that V_O does not change, then the current drawn by R_L can be found as

$$I_L = \frac{V_O}{R_L} = \frac{3}{15} = 0.2 \text{ mA}$$

This current will be subtracted from that supplied through R , thus the current in the diode string is reduced by 0.2 mA . Using the small signal model for the diodes, each diode voltage will decrease by $0.2 \text{ mA} \times r_d = 0.2 \times 33.8 = 6.76 \text{ mV}$, which is still small enough for the small signal model to be applicable. Thus, the change in V_O will be

$$\Delta V_O = -4 \times 6.76 = -27 \text{ mV}$$

or 0.9% .

Since the change in V_O is small, our original assumption used to find the current I_L is justified.

4.9

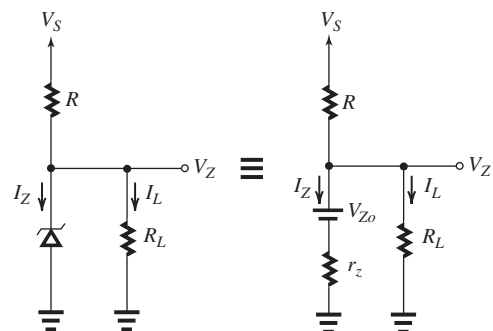


Figure 4.9.1

$$V_{ZK} \simeq V_{Z0}$$

where

$$V_{Z0} + r_z I_Z = V_Z$$

Thus,

$$V_{Z0} = V_Z - r_z I_Z$$

$$= 6.8 - 0.020 \times 5$$

$$= 6.7 \text{ V}$$

For no load, the lowest value of V_S to maintain breakdown operation is equal to the knee voltage, that is,

$$V_{S\text{min}} = 6.7 \text{ V}$$

For $V_S = 9\text{ V}$, the maximum load current $I_{L\text{max}}$ for which breakdown operation is maintained is found from

$$V_S = V_{Z0} + (I_{L\text{max}} + I_{ZK})R$$

where we have assumed the zener voltage to be at its knee value ($V_{ZK} \approx V_{Z0}$) and the zener current at $I_{ZK} = 0.2\text{ mA}$. Thus

$$9 = 6.7 + (I_{L\text{max}} + 0.2) \times 0.2$$

$$\Rightarrow I_{L\text{max}} = 11.3\text{ mA}$$

For $I_L = 0.5 I_{L\text{max}} = 5.65\text{ mA}$, the lowest value of V_S to maintain breakdown operation is found from

$$V_{S\text{min}} = V_{Z0} + (0.5 I_{L\text{max}} + I_{ZK})R$$

$$= 6.7 + (0.5 \times 11.3 + 0.2) \times 0.2$$

$$= 7.9\text{ V}$$

$$\text{Line regulation} = \frac{r_z}{r_z + R} = \frac{20}{20 + 200} \approx 91\text{ mV/V}$$

$$\text{Load regulation} = -(r_z \parallel R) = -(20 \parallel 200)$$

$$= -18.2\text{ mV/mA}$$

The circuit in Fig. 4.10.1 is a full-wave rectifier with a center-tapped secondary winding. The circuit can be analyzed by looking at v_O^+ and v_O^- separately. The circuits for doing so are shown in Fig. 4.10.2. Their analysis, of course, is identical. For each supply,

$$V_O = 10\text{ V}$$

$$V_r = 0.8\text{ V}$$

Thus,

$$v_O = 10 \pm 0.4\text{ V}$$

It follows that the peak value of v_S must be $10.4 + 0.7 = 11.1\text{ V}$ and the total rms voltage across the secondary will be

$$\frac{2 \times 11.1}{\sqrt{2}} = 15.7\text{ V (rms)}$$

Thus,

$$\text{Transformer turns ratio} = \frac{120}{15.7} = 7.64 : 1$$

To deliver a 50-mA dc current to each load,

$$R = \frac{10}{0.05} = 200\ \Omega$$

4.10 Refer to Figures 4.10.1 and 4.10.2 below.

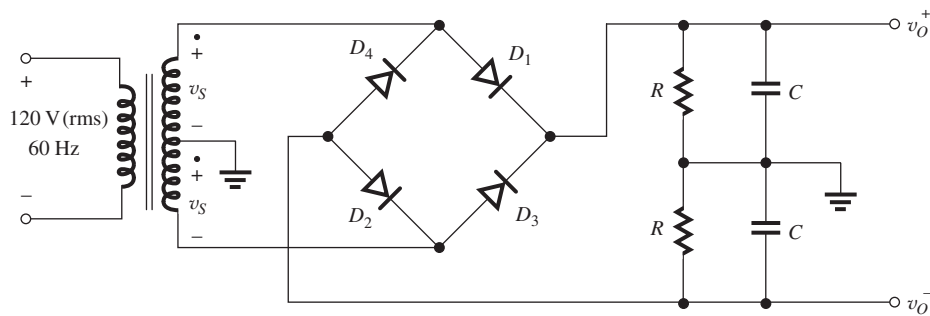


Figure 4.10.1

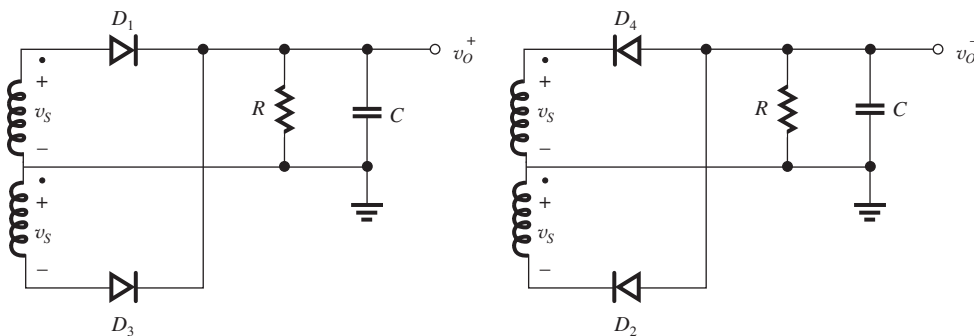


Figure 4.10.2

Now, the value of C can be found from

$$V_r = \frac{V_p - 0.7}{2fCR}$$

$$0.8 = \frac{11.1 - 0.7}{2 \times 60 \times C \times 200}$$

$$\Rightarrow C = 541.7 \mu\text{F}$$

To specify the diodes, we determine i_{Dav} and i_{Dmax} ,

$$i_{Dav} = I_L \left[1 + \pi \sqrt{(V_p - 0.7)/2V_r} \right]$$

$$= 50 \left[1 + \pi \sqrt{(11.1 - 0.7)/1.6} \right]$$

$$= 450.5 \text{ mA}$$

$$i_{Dmax} = I_L \left[1 + 2\pi \sqrt{(V_p - 0.7)/2V_r} \right]$$

$$= 50 \left[1 + 2\pi \sqrt{(11.1 - 0.7)/1.6} \right]$$

$$= 851 \text{ mA}$$

To determine the required PIV rating of each diode, we determine the maximum reverse voltage that appears across one of the diodes, say D_1 . This occurs when v_S is at its maximum negative value $-V_p$. Since the cathode of D_1 will be at $+10.4 \text{ V}$, the maximum reverse voltage across D_1 will be $10.4 + 11.1 = 21.5 \text{ V}$. Using a factor of safety of 1.5, then each of the four diodes must have

$$\text{PIV} = 1.5 \times 21.5 = 32.3 \text{ V}$$

4.11

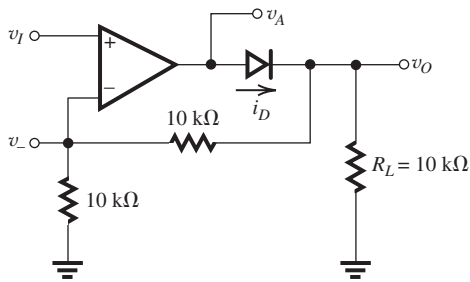


Figure 4.11.1

When v_I is positive, v_A goes positive, turning on the diode and closing the negative feedback loop around the op amp. The result is that $v_- = v_I$, $v_O = 2v_- = 2v_I$, $v_A = v_O + 0.7$, and $i_D = \frac{v_O}{20} + \frac{v_O}{10} = 0.15v_O$, mA. Thus,

(a) For $v_I = +0.1 \text{ V}$: $v_- = +0.1 \text{ V}$, $v_O = +0.2 \text{ V}$, $v_A = 0.9 \text{ V}$, $i_D = 0.03 \text{ mA} = 30 \mu\text{A}$.

(b) For $v_I = +1 \text{ V}$: $v_- = +1 \text{ V}$, $v_O = +2 \text{ V}$, $v_A = +2.7 \text{ V}$, $i_D = 0.15 \times 2 = 0.3 \text{ mA}$.

When v_I goes negative, v_A follows, the diode turns off, and the feedback loop is opened. The op amp saturates with $v_A = -5 \text{ V}$, $v_- = 0 \text{ V}$, and $v_O = 0 \text{ V}$. Thus,

(c) For $v_I = -0.1 \text{ V}$: $v_- = 0 \text{ V}$, $v_A = -5 \text{ V}$, $v_O = 0 \text{ V}$, and $i_D = 0$.

(d) For $v_I = -1 \text{ V}$: $v_- = 0 \text{ V}$, $v_A = -5 \text{ V}$, $v_O = 0 \text{ V}$, and $i_D = 0$.

Finally, if v_I is a symmetrical square wave of 2-V amplitude and zero average, the output will be zero during the negative half-cycles of the input and will equal twice the input (i.e., 4 V) during the positive half-cycles. See Fig. 4.11.2.

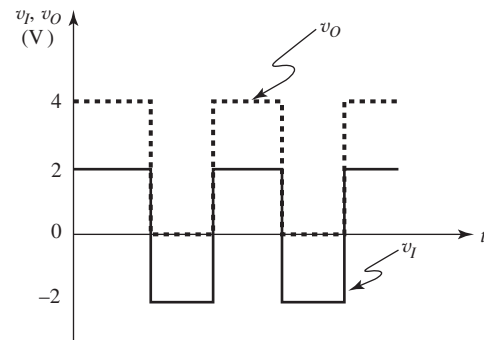


Figure 4.11.2

Thus, v_O is a square wave with 0-V and 4-V levels (i.e., 2-V average) and, of course, the same frequency (1 kHz) as the input.

4.12



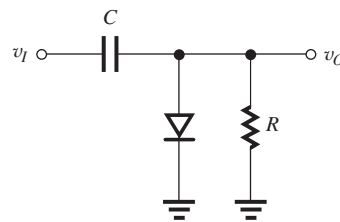


Figure 4.12.1

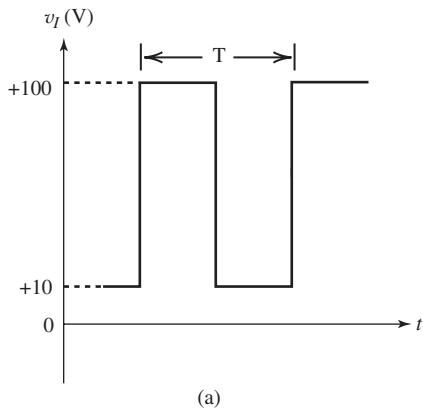

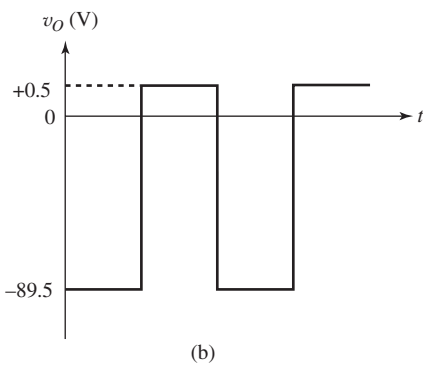(a) For light load (R very large), the output is a square wave of period T going from $+0.5$ V to $+0.5 - (100 - 10) = -89.5$ V. See Figure 4.12.2(b).




(b) If R is reduced so that $RC = 2T$, the output waveform will take the shape shown in Fig. 4.12.2(c). Consider first the negative portion of the waveform. As before, the largest negative value is -89.5 V. At this time, the diode is cut off and the capacitor discharges through the now smaller resistance R . Thus, v_O rises exponentially, heading towards 0 V, but of course is interrupted ($T/2$) second later, thus

$$v_O(t) = 0 - 89.5e^{-t/CR}$$

$$v_O\left(\frac{T}{2}\right) = -89.5e^{-T/2CR}$$

For $CR = 2T$,
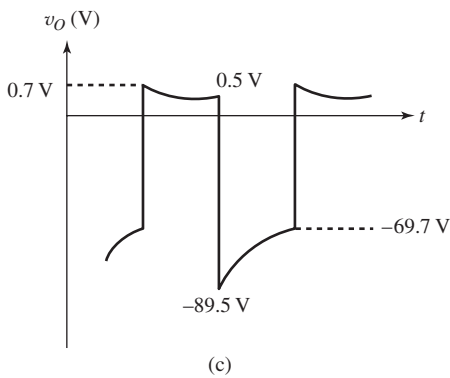
$$v_O\left(\frac{T}{2}\right) = -89.5 \times e^{-1/4} = -69.7 \text{ V}$$



Thus, at the end of the discharge interval, $v_O = -69.7$ V. At that time, the input rises by 90 V and the output attempts to follow. However, the diode clamps v_O to about 0.7 V or so and it conducts heavily to recharge the capacitor. The diode voltage then drops, reaching about 0.5 V at the end of the half-cycle. As the input falls by 90 V, the output follows, reaching -89.5 V, and the cycle repeats.

Figure 4.12.2