



UNIVERSITY OF RWANDA  
COLLEGE OF SCIENCE & TECHNOLOGY  
SCHOOL OF ENGEERING  
DEPARTMENT OF ELECTRICAL & ELECTRONICS ENGINEERING

KIZITO NKURIKIYEYEU, PHD


EPE 2165—ANALOG ELECTRONICS

**EXERCISE #—1: DIODE CIRCUITS**

July 26, 2022

**Section 4.1: The Ideal Diode**


**4.1**

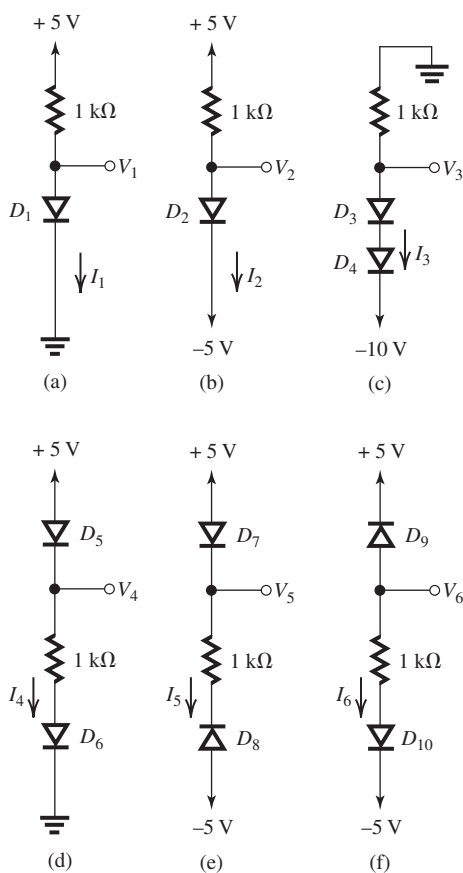

**Figure 4.1.1**

For the circuits in Fig. 4.1.1 employing ideal diodes, find the labeled currents  $I$  and voltages  $V$ , measured with respect to ground.


**4.2**

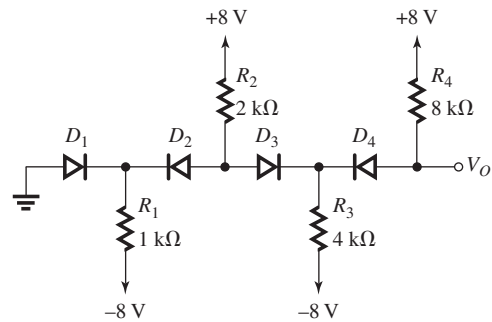

**Figure 4.2.1**

For the circuit shown in Fig. 4.2.1 employing ideal diodes, find the currents through all branches and determine the voltages at all nodes.

**4.3**

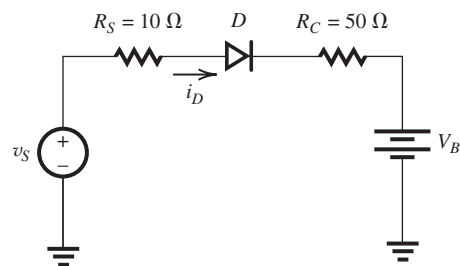

**Figure 4.3.1**


In the battery-charger circuit shown in Fig. 4.3.1, the sine-wave input  $v_S$  is 12 V (rms), while the battery voltage varies from 12 V to 14 V from the discharged to fully charged states.  $R_S = 10 \Omega$  is the charging-source resistance,  $D$  is an ideal diode,



and  $R_C = 50 \Omega$  is a current-controlling resistor established by the designer. Sketch and label the diode-current waveform for  $V_B = 12 \text{ V}$ . What are its peak and average values? What do the peak and average diode currents become when  $V_B$  reaches  $14 \text{ V}$ ?

**Section 4.2: Terminal Characteristics of Junction Diodes**

**D4.4**

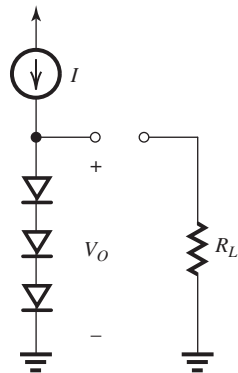


**Figure 4.4.1**


The diodes in the circuit in Fig. 4.4.1 have  $I_S = 10^{-16} \text{ A}$ . Find the value of the current  $I$  that results in  $V_O = +2.4 \text{ V}$ . If a resistance  $R_L$  is connected to  $V_O$  and it draws a current of  $1 \text{ mA}$ , find the change in  $V_O$ . Without  $R_L$  connected, find the change  $V_O$  that results when the temperature increases by  $20^\circ\text{C}$ .

**Section 4.3: Modeling the Diode**

**4.5**

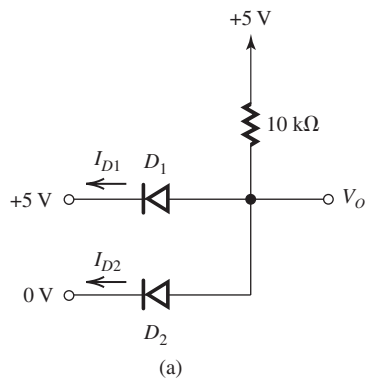

**Figure 4.5.1**

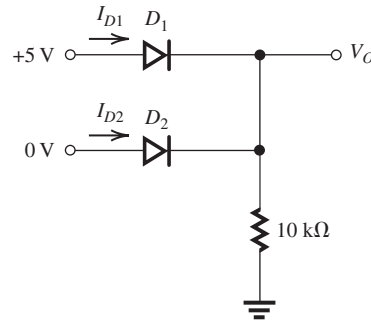


(b)

**Figure 4.5.1 continued**

For the diode logic circuits shown in Fig. 4.5.1, find the output voltage and the diode currents for the particular input values shown. Model a conducting diode as a constant voltage drop of  $0.7 \text{ V}$ .

**4.6**

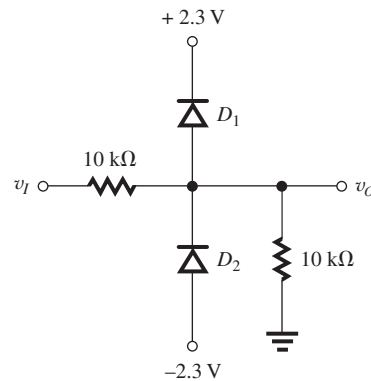

**Figure 4.6.1**

For the limiter circuit shown in Fig. 4.6.1, find the upper and lower limiting levels, the transmission  $v_o/v_i$  in the linear region, and the upper- and lower-input threshold levels. Sketch  $v_o$  vs  $v_i$ . What is the input current required from an input which is twice the upper threshold value? Assume that when a diode conducts it exhibits a voltage drop of  $0.7 \text{ V}$ .

**Section 4.4: The Small-Signal Model**

**4.7**

For the circuit in Fig. 4.7.1, assume that  $v_i$  is a small signal and that  $C_1$  and  $C_2$  are large coupling capacitors. Use the small-signal model for each of  $D_1$  and  $D_2$  to find  $v_o/v_i$ . For  $I = 1 \text{ mA}$ , what must  $I_x$  be to obtain  $v_o/v_i = 0, 0.2, 0.5, \text{ or } 1$ ?

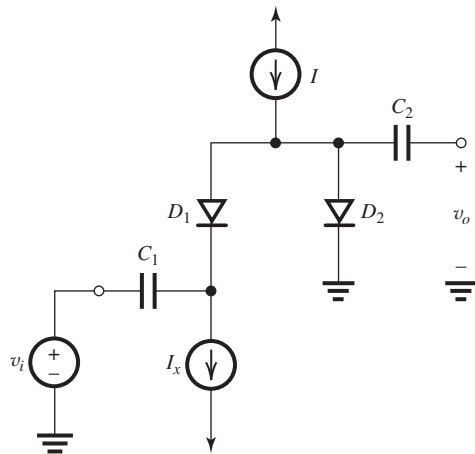


Figure 4.7.1

**Section 4.5: Voltage Regulation**

**D4.8**

Given the availability of diodes that exhibit a voltage drop of 0.7 V at a current of 0.1 mA, use four diodes connected in series and fed from a +5-V supply through a resistance  $R$  to obtain a voltage  $V_O = 3.0\text{ V}$  across the diode string. What value of  $R$  is required? If the supply voltage changes by  $\pm 10\%$ , use the small-signal diode model to find the corresponding absolute and percentage changes in  $V_O$ ? If a load resistance  $R_L = 15\text{ k}\Omega$  is connected across the diode string, what do you estimate the absolute and percentage changes of  $V_O$  to be? Whenever you use the small-signal diode model, verify that such use is justified.

**4.9**

A 6.8-V Zener diode specified at 5 mA to have  $V_Z = 6.8\text{ V}$  and  $r_z = 20\ \Omega$  with  $I_{ZK} = 0.2\text{ mA}$

is operated in a regulator circuit using a 200- $\Omega$  resistor and a 9-V supply. Estimate the knee voltage of the zener. For no load, what is the lowest supply voltage for which the zener remains in breakdown operation? For the nominal supply voltage, what is the maximum load current for which the zener remains in breakdown operation? For half this load current, what is the lowest supply voltage for breakdown operation? What are the line regulation and load regulation?

**Section 4.6: Rectifier Circuits**

**D4.10**

The circuit in Fig. 4.10.1 (refer Figure below) implements a complementary-output peak rectifier. Assume that the diodes available exhibit a 0.7-V drop when conducting. Design the circuit to provide a  $\pm 10\text{-V}$  dc output voltages with a peak-to-peak ripple no greater than 0.8 V. Each supply should be capable of providing 50-mA dc current to its load resistor  $R$ . Completely specify the capacitors, diodes, and the transformer.

**4.11**

The op amp in the precision rectifier circuit of Fig. 4.11.1 is ideal with output that saturates at  $\pm 5\text{ V}$ . Assume that when conducting the diode exhibits a constant voltage drop of 0.7 V. Find  $v_O$ ,  $v_A$ , and  $i_D$  for:

- (a)  $v_I = +0.1\text{ V}$
- (b)  $v_I = +1.0\text{ V}$
- (c)  $v_I = -0.1\text{ V}$
- (d)  $v_I = -1.0\text{ V}$

Also, find the average output voltage obtained when  $v_I$  is a symmetrical square wave of 1-kHz frequency, 2-V amplitude, and zero average.

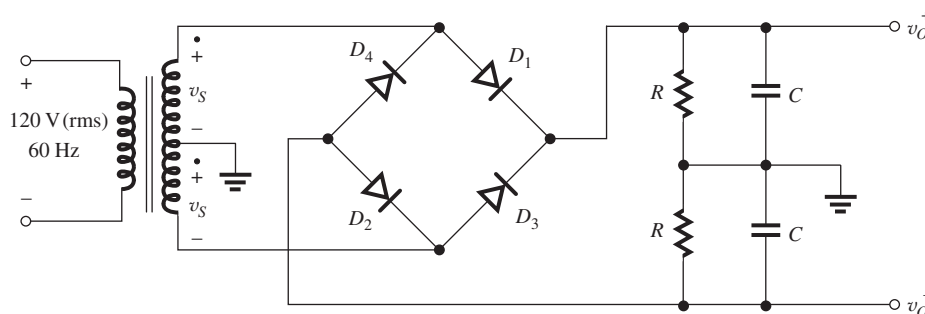


Figure 4.10.1

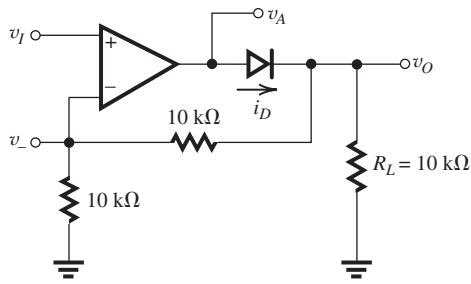


Figure 4.11.1

**Section 4.7: Diode Applications**

**4.12**

The clamped-capacitor circuit shown in Fig. 4.12.1 has a square-wave input of 10-V and 100-V levels.

(a) Describe the resulting output for a very high-resistance load  $R$  and a diode that has 0.5-V drop at very low currents.

(b) What happens when the load resistance  $R$  is reduced such that  $CR = 2T$ , where  $T$  is the period of the square-wave input.

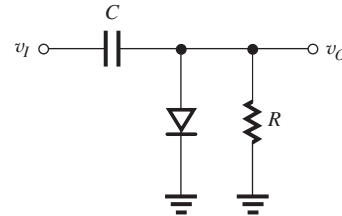


Figure 4.12.1