



UNIVERSITY OF RWANDA
COLLEGE OF SCIENCE & TECHNOLOGY
SCHOOL OF ENGEERING
DEPARTMENT OF ELECTRICAL & ELECTRONICS ENGINEERING

KIZITO NKURIKIYEYEU, PHD

EPE 2165—ANALOG ELECTRONICS

SOLUTION #—3: DIODE CIRCUITS

July 26, 2022



6.1

(a)

$$i_C = I_S e^{v_{BE}/V_T}$$

At $i_C = i_{C1}$,

$$i_{C1} = I_S e^{v_{BE1}/V_T} \tag{1}$$

and at $i_C = i_{C2}$,

$$i_{C2} = I_S e^{v_{BE2}/V_T} \tag{2}$$

Dividing Eq. (2) by Eq. (1), we obtain

$$\frac{i_{C2}}{i_{C1}} = e^{(v_{BE2} - v_{BE1})/V_T} \tag{3}$$

Which can be expressed alternately as

$$v_{BE2} - v_{BE1} = V_T \ln\left(\frac{i_{C2}}{i_{C1}}\right) \tag{4}$$

For $i_{C2}/i_{C1} = 2$,

$$\Delta v_{BE} \equiv v_{BE2} - v_{BE1} = 25 \ln 2 = 17.3 \text{ mV}$$

(b) Using Eq. (4) with $i_{C2}/i_{C1} = 10$, we find

$$\Delta v_{BE} \equiv v_{BE2} - v_{BE1} = 25 \ln(10) = 57.6 \text{ mV}$$

(c) The percentage change in i_C ,

$$\frac{i_{C2} - i_{C1}}{i_{C1}} \times 100$$

corresponding to a change $\Delta v_{BE} \equiv v_{BE2} - v_{BE1}$ can be calculated using Eq. (3). The results obtained for the given values of Δv_{BE} are as in the table below:

$\Delta v_{BE}, \text{mV}$	+0.5	-0.5	+1.0	-1.0	+2.0	-2.0	+5.0	-5.0	+10	-10
$\frac{\Delta i_C}{i_C}, \%$	+2	-2	-4	-4	+8.3	-7.7	+22	-18	+49	-33

We observe that for small Δv_{BE} , positive and negative increments yield nearly equal positive and negative changes in i_C . Also, for small Δv_{BE} , the changes in i_C are linearly related to Δv_{BE} with a proportionality factor of 4% per mV. This linear relationship breaks down when Δv_{BE} becomes large, for instance, $\pm 10 \text{ mV}$.

(d)

$$\beta = \frac{i_C}{i_B} = \frac{1 \text{ mA}}{12.5 \mu\text{A}} = \frac{1}{0.0125} = 80$$

$$\alpha = \frac{\beta}{\beta + 1} = \frac{80}{81} = 0.988$$

$$i_E = i_C + i_B = 1 + 0.0125 = 1.0125 \text{ mA}$$

(e)

$$1 \times 10^{-3} = I_S e^{675/25} \Rightarrow I_S = 1.88 \times 10^{-15} \text{ A}$$

(f) With two identical transistors connected in parallel with a combined collector current of 1 mA, each transistor has a collector current of 0.5 mA. Thus, Eq. (4) can be used to determine the change in v_{BE} as i_C decreases from 1 mA to 0.5 mA as

$$v_{BE2} - v_{BE1} = 25 \ln(0.5) = -17.3 \text{ mV}$$

From (e) above, $v_{BE1} = 675 \text{ mV}$, thus

$$v_{BE2} = 675 - 17.3 = 657.7 \text{ mV}$$

Alternatively, we can think of the combination of the two parallel devices as a transistor with twice the base-emitter area and correspondingly twice the value of I_S . When this equivalent transistor is conducting a 1-mA collector current, the base emitter voltage can be obtained from

$$1 \times 10^{-3} = 2 \times 1.88 \times 10^{-15} e^{v_{BE}/V_T}$$

$$\Rightarrow v_{BE} = 657.7 \text{ mV}$$

6.2

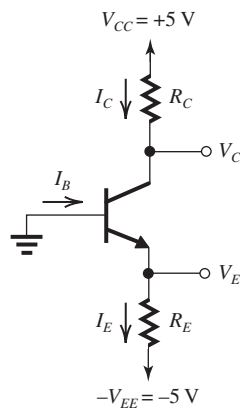


Figure 6.2.1

(a) $V_C = +1.58 \text{ V}$ and $V_B = 0 \text{ V}$; thus, $V_C > V_B$, indicating that the transistor must be operating in the active mode.

(b)

$$I_E = \frac{V_E - (-V_{EE})}{R_E} = \frac{-0.68 - (-5)}{5}$$

$$I_E = 0.864 \text{ mA}$$

$$I_B = \frac{I_E}{\beta + 1} = \frac{0.864}{100 + 1} = 0.0086 \text{ mA}$$

$$I_C = I_E - I_B = 0.855 \text{ mA}$$

(c)

$$I_C = \frac{V_{CC} - V_C}{R_C}$$

$$0.855 = \frac{5 - 1.58}{R_C}$$

$$\Rightarrow R_C = 4 \text{ k}\Omega$$

(d) To obtain $I_C = 2 \text{ mA}$, the emitter current I_E must be

$$I_E = \frac{I_C}{\alpha}$$

where

$$\alpha = \frac{\beta}{\beta + 1} = \frac{100}{101} = 0.99$$

Thus,

$$I_E = \frac{2}{0.99} = 2.02 \text{ mA}$$

Next, we determine V_E by first finding V_{BE} . The transistor has $I_C = 0.855 \text{ mA}$ at $V_{BE} = 0.68 \text{ V}$. To obtain $I_C = 2 \text{ mA}$, V_{BE} must be increased by

$$\Delta V_{BE} = V_T \ln \frac{2}{0.855} = 0.02 \text{ V}$$

resulting in

$$V_{BE} = 0.68 + 0.02 = 0.7 \text{ V}$$

and thus

$$V_E = 0 - V_{BE} = -0.7 \text{ V}$$

The required value of R_E can now be determined from

$$R_E = \frac{V_E - (-V_{EE})}{I_E} = \frac{-0.7 - (-5)}{2.02}$$

$$\Rightarrow R_E = 2.13 \text{ k}\Omega$$

The required value of R_C can be determined from

$$R_C = \frac{V_{CC} - V_C}{I_C} = \frac{5 - 1}{2}$$

$$\Rightarrow R_C = 2 \text{ k}\Omega$$

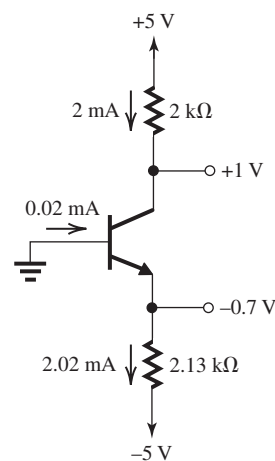


Figure 6.2.2

Figure 6.2.2 shows the redesigned circuit together with all voltages and currents.

6.3

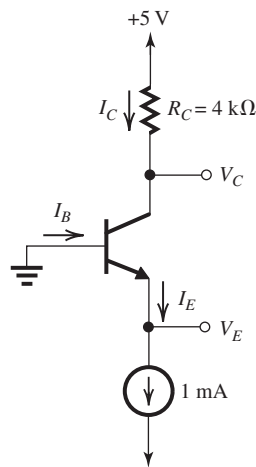


Figure 6.3.1

Since $I_E = 1 \text{ mA}$, it remains constant and independent of the value of β .

$$\alpha = \frac{\beta}{\beta + 1}$$

$$\beta = 50, \quad \alpha = \frac{50}{50 + 1} = 0.980$$

$$\beta = 200, \quad \alpha = \frac{200}{200 + 1} = 0.995$$

Thus, α lies in the range 0.980 to 0.995. Assuming the transistor is operating in the active mode over this range, we find I_C from

$$I_C = \alpha I_E$$

For $I_E = 1 \text{ mA}$, I_C lies in the range 0.980 mA to 0.995 mA.

$$V_C = V_{CC} - I_C R_C = 5 - I_C \times 4$$

Substituting for $I_C = 0.980$ to 0.995 results in the range of V_C as 1.08 V to 1.02 V. Note that over this range of V_C , the BJT is indeed in the active region, as assumed.

$$I_B = \frac{I_E}{\beta + 1} = \frac{1}{\beta + 1} \text{ mA}$$

For β in the range 50 to 200, I_B will be in the range 0.02 mA to 0.005 mA. Utilizing the relationship

$$I_C = I_S e^{V_{BE}/V_T}$$

which can be rewritten as

$$V_{BE} = V_T \ln(I_C/I_S)$$

we can determine the range of V_{BE} by substituting $I_C = 0.980 \text{ mA}$ to 0.995 mA . We obtain the range of V_{BE} as from 0.690 V to 0.691 V. Since $V_E = -V_{BE}$, the range of V_E will be -0.690 V to -0.691 V .

Comment:

Although β ranges over a 4:1 range or a 300% change relative to its low value, the corresponding changes in α and all voltages and currents (except for I_B) are much lower. For instance, α , I_C , and V_C change by only 1.5% relative to their low values. V_{BE} and V_E change by only 1 mV (in 700 mV or so; a negligible change). The only quantity that tracks the change in β is I_B . Nevertheless, as we will learn later on, I_B in this circuit is not an important parameter. The insensitivity of this circuit to β variation makes it an excellent design!

6.4

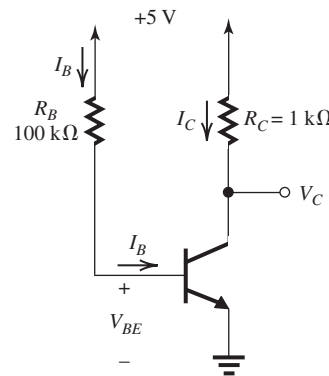


Figure 6.4.1

The current I_B can be determined from

$$I_B = \frac{5 - V_{BE}}{R_B} = \frac{5 - 0.7}{100}$$

Thus,

$$I_B = 0.043 \text{ mA}$$

and is independent of β .

Assuming active-mode operation, the collector current can be found from

$$I_C = \beta I_B$$

and the collector voltage can then be determined using

$$V_C = 5 - R_C I_C = 5 - 1 \times I_C$$

For $\beta = 50$,

$$I_C = 50 \times 0.043 = 2.15 \text{ mA}$$

and

$$V_C = 5 - 1 \times 2.15 = 2.85 \text{ V}$$

which is greater than the voltage at the base, thus the transistor is in the active region, as assumed.

For $\beta = 200$,

$$I_C = 200 \times 0.043 = 8.6 \text{ mA}$$

and

$$V_C = 5 - 1 \times 8.6 = -3.6 \text{ V}$$

which is impossible as the base voltage is $+0.7 \text{ V}$. Thus, the transistor cannot be operating in the active mode. Rather, it must be in the saturation mode, for which

$$V_C = V_{CE\text{sat}} = 0.2 \text{ V}$$

$$I_C = \frac{5 - V_C}{R_C} = \frac{5 - 0.2}{1} = 4.8 \text{ mA}$$

The ratio I_C/I_B , which is the forced β , is thus

$$\beta_{\text{forced}} = \frac{I_C}{I_B} = \frac{4.8}{0.043} = 111.6$$

which is lower than the normal value of β (200), confirming that the transistor is in saturation.

Comment:

The operation of this circuit is highly sensitive to the value of β . Indeed, over the specified range of β , the transistor goes from active mode to saturation. This is not a desirable situation and the circuit is not a good design.

6.5

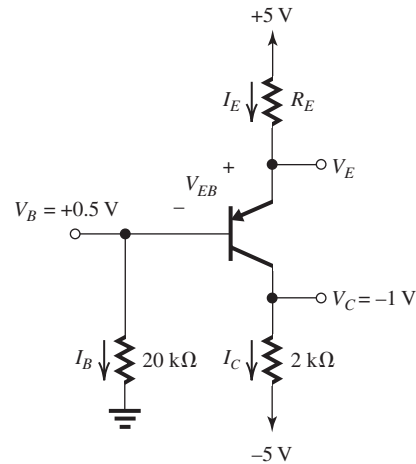


Figure 6.5.2

From Fig. 6.5.2, we see that V_C is lower than V_B , thus the *pn*p transistor is operating in the active mode. By reference to the figure, we can write

$$I_B = \frac{V_B}{20 \text{ k}\Omega} = \frac{+0.5 \text{ V}}{20 \text{ k}\Omega} = 0.025 \text{ mA}$$

and

$$I_C = \frac{V_C - (-5)}{2 \text{ k}\Omega} = \frac{-1 + 5}{2} = 2 \text{ mA}$$

Thus,

$$\beta \equiv \frac{I_C}{I_B} = \frac{2 \text{ mA}}{0.025 \text{ mA}} = 80$$

To obtain V_{EB} , we utilize the given information that $V_{BE} = 0.7 \text{ V}$ at $I_C = 1 \text{ mA}$. Here $I_C = 2 \text{ mA}$, thus

$$V_{BE} = 0.7 + V_T \ln\left(\frac{2}{1}\right) = 0.717 \text{ V}$$

We now can find V_E as

$$\begin{aligned} V_E &= V_B + V_{EB} \\ &= 0.5 + 0.717 = 1.217 \text{ V} \end{aligned}$$

The current I_E can be found as

$$I_E = I_C + I_B = 2 + 0.025 = 2.025 \text{ mA}$$

The value of R_E can be determined from

$$\begin{aligned} I_E &= \frac{5 - V_E}{R_E} \\ \Rightarrow R_E &= \frac{5 - 1.217}{2.025} = 1.868 \text{ k}\Omega \end{aligned}$$

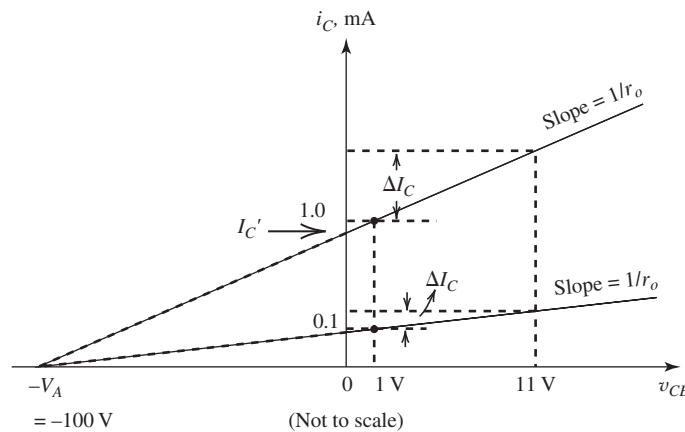


Figure 6.6.1

6.6

(a) Refer to Figure 6.6.1 above.

$$r_o = \frac{V_A}{I_C} \approx \frac{100 \text{ V}}{1 \text{ mA}} = 100 \text{ k}\Omega$$

Note that the approximation involved is that we used I_C at $V_{CE} = 1 \text{ V}$ rather than I_C' , which would be the value at the intersection of the $i_C - v_{CE}$ line with the vertical axis (Fig. 6.6.1). Alternatively, we can use

$$r_o = \frac{V_A + V_{CE}}{I_C} = \frac{100 + 1}{1} = 101 \text{ k}\Omega$$

which is very close to the approximate value obtained above and which we will usually use.

(b) For $\Delta V_{CE} = 10 \text{ V}$, the current I_C changes by

$$\Delta I_C = \frac{\Delta V_{CE}}{r_o} = \frac{10}{100} = 0.1 \text{ mA}$$

Thus, I_C becomes

$$I_C = 1 + 0.1 = 1.1 \text{ mA}$$

(c)

$$r_o = \frac{V_A}{I_C} \approx \frac{100 \text{ V}}{0.1 \text{ mA}} = 1000 \text{ k}\Omega = 1 \text{ M}\Omega$$

$$\Delta I_C = \frac{\Delta V_{CE}}{r_o} = \frac{10 \text{ V}}{1000 \text{ k}\Omega} = 0.01 \text{ mA}$$

$$I_C = 0.1 + 0.01 = 0.11 \text{ mA}$$

6.7

(a)

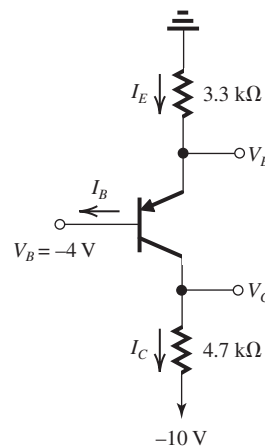


Figure 6.7.1(a)

Assume operation in the active mode.

$$V_E = V_B + V_{EB} = -4 + 0.7 = -3.3 \text{ V}$$

$$I_E = \frac{0 - V_E}{3.3 \text{ k}\Omega} = \frac{0 - (-3.3)}{3.3} = 1 \text{ mA}$$

$$I_C = \alpha I_E = \frac{\beta}{\beta + 1} I_E = \frac{50}{50 + 1} \times 1 = 0.98 \text{ mA}$$

$$I_B = \frac{I_C}{\beta} = \frac{0.98}{50} = 0.0196 \text{ mA} = 19.6 \mu\text{A}$$

$$V_C = -10 + I_C \times 4.7 = -10 + 0.98 \times 4.7 = -5.39 \text{ V}$$

Since $V_C < V_B$, the CBJ is reverse biased and the pnp transistor is operating in the active mode, as assumed.

(b)

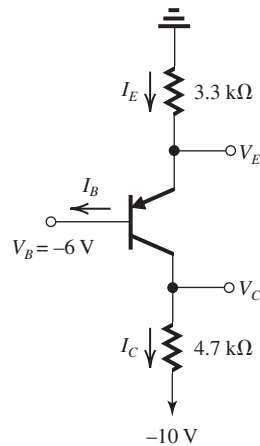


Figure 6.7.1(b)

Assume active-mode operation.

$$V_E = V_B + V_{EB} = -6 + 0.7 = -5.3 \text{ V}$$

$$I_E = \frac{0 - V_E}{3.3 \text{ k}\Omega} = \frac{0 - (-5.3)}{3.3} = 1.606 \text{ mA}$$

$$I_C = \alpha I_E = \frac{\beta}{\beta + 1} I_E = \frac{50}{50 + 1} \times 1.606 \\ = 1.57 \text{ mA}$$

$$V_C = -10 + 4.7 \times I_C = -10 + 4.7 \times 1.57 \\ = -2.62 \text{ V}$$

Since V_C at -2.62 V is higher than V_B at -6 V , it follows that the transistor is not in the active mode as we assumed. Rather, the *pnp* transistor must be operating in saturation. In this case, V_E and I_E remain unchanged at

$$V_E = -5.3 \text{ V}, \quad I_E = 1.606 \text{ mA}$$

but V_{EC} now is

$$V_{EC\text{sat}} = 0.2 \text{ V}$$

Thus,

$$V_C = V_E - V_{EC\text{sat}} = -5.3 - 0.2 = -5.5 \text{ V}$$

and

$$I_C = \frac{V_C - (-10)}{4.7 \text{ k}\Omega} = \frac{-5.5 + 10}{4.7} = 0.957 \text{ mA}$$

and

$$I_B = I_E - I_C = 1.606 - 0.957 = 0.649 \text{ mA}$$

As another check that the transistor is operating in saturation, we find the forced β as

$$\beta_{\text{forced}} \equiv \frac{I_C}{I_B} = \frac{0.957 \text{ mA}}{0.649 \text{ mA}} = 1.47$$

which is much lower than the normal β of 50, verifying that the transistor is operating in saturation.

(c)

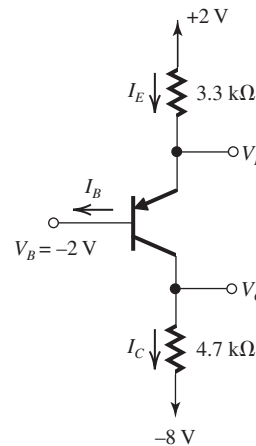


Figure 6.7.1(c)

Assume active-mode operation.

$$V_E = V_B + V_{EB} = -2 + 0.7 = -1.3 \text{ V}$$

$$I_E = \frac{+2 - V_E}{3.3 \text{ k}\Omega} = \frac{2 - (-1.3)}{3.3} = 1 \text{ mA}$$

$$I_C = \alpha I_E = \frac{\beta}{\beta + 1} I_E = \frac{50}{50 + 1} \times 1 = 0.98 \text{ mA}$$

$$I_B = \frac{I_C}{\beta} = \frac{0.98 \text{ mA}}{50} = 0.0196 \text{ mA} = 19.6 \mu\text{A}$$

$$V_C = -8 + I_C \times 4.7 = -8 + 0.98 \times 4.7 = -3.39 \text{ V}$$

Since V_C at -3.39 V is lower than V_B at -2 V , the CBJ is reverse biased and the transistor is operating in the active mode, as assumed.



(d)

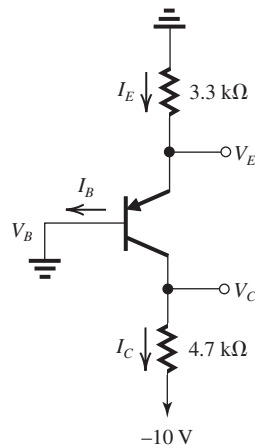


Figure 6.7.1(d)

Since the base is at 0 V and the emitter is connected to ground (0 V) through the 3.3-kΩ resistance, the emitter-base junction cannot conduct. Thus,

$$V_E = 0 \text{ V}$$

$$I_E = 0 \text{ mA}$$

Since the collector is connected to -10 V through the 4.7-kΩ resistance, the CBJ will be reverse biased. Thus,

$$I_C = 0 \text{ mA}$$

$$I_B = 0$$

and

$$V_C = -10 + I_C \times 4.7 = -10 \text{ V}$$

Thus, the transistor is cut off.

(e)

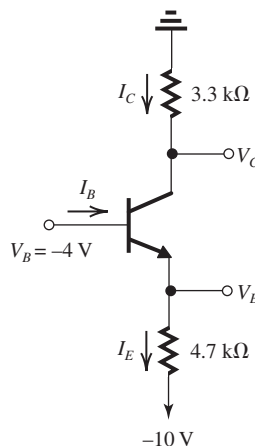


Figure 6.7.1(e)

Assume active-mode operation.

$$V_E = V_B - V_{BE} = -4 - 0.7 = -4.7 \text{ V}$$

$$I_E = \frac{V_E - (-10)}{4.7 \text{ k}\Omega} = \frac{-4.7 + 10}{4.7} = 1.128 \text{ mA}$$

$$I_C = \alpha I_E = \frac{\beta}{\beta + 1} I_E = \frac{50}{50 + 1} \times 1.13 = 1.105 \text{ mA}$$

$$I_B = \frac{I_C}{\beta} = \frac{1.105}{50} = 0.022 \text{ mA} = 22 \mu\text{A}$$

$$V_C = 0 - I_C \times 3.3 = -1.105 \times 3.3 = -3.65 \text{ V}$$

Since V_C at -3.65 V is higher than V_B at -4 V, the CBJ is reverse biased and the npn transistor is operating in the active mode, as assumed.

(f)

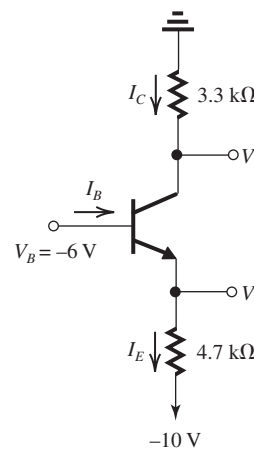


Figure 6.7.1(f)

Assume active-mode operation.

$$V_E = V_B - V_{BE} = -6 - 0.7 = -6.7 \text{ V}$$

$$I_E = \frac{V_E - (-10)}{4.7 \text{ k}\Omega} = \frac{-6.7 + 10}{4.7} = 0.702 \text{ mA}$$

$$I_C = \alpha I_E = \frac{\beta}{\beta + 1} I_E = \frac{50}{50 + 1} \times 0.702 = 0.688 \text{ mA}$$

$$I_B = \frac{I_C}{\beta} = \frac{0.688}{50} = 0.0138 \text{ mA} = 13.8 \mu\text{A}$$

$$V_C = 0 - I_C \times 3.3 = 0 - 0.688 \times 3.3 = -2.27 \text{ V}$$

Since V_C at -2.27 V is higher than V_B at -6 V, the CBJ is reverse biased and the npn transistor is operating in the active mode, as assumed.



6.8
(a)

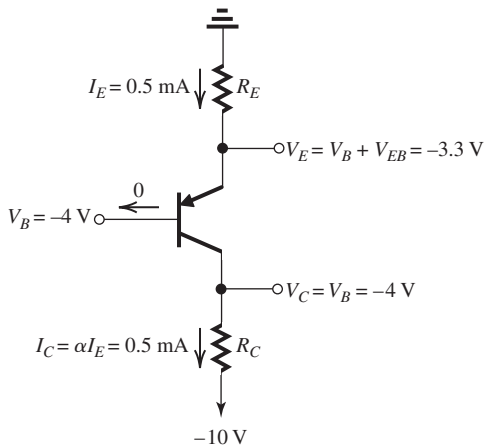


Figure 6.8.1

We note that $V_{BC} = 0$ means the transistor is operating in the active mode. The circuit is shown in Fig. 6.8.1 with some of the analysis already done on the diagram. We can now write

$$R_E = \frac{0 - V_E}{I_E} = \frac{0 - (-3.3)}{0.5 \text{ mA}} = 6.6 \text{ k}\Omega$$

$$R_C = \frac{V_C - (-10)}{I_C} = \frac{-4 + 10}{0.5 \text{ mA}} = 12 \text{ k}\Omega$$

(b)

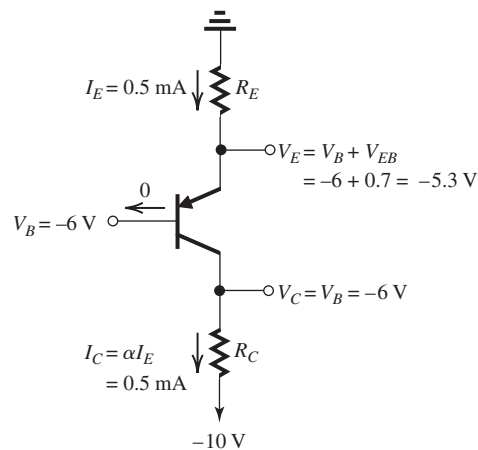


Figure 6.8.2

The circuit with some of the analysis already performed directly on the diagram is shown in

Fig. 6.8.2. We can now write

$$R_E = \frac{0 - V_E}{I_E} = \frac{0 - (-5.3)}{0.5} = 10.6 \text{ k}\Omega$$

$$R_C = \frac{V_C - (-10)}{I_C} = \frac{-6 + 10}{0.5} = 8 \text{ k}\Omega$$

6.9

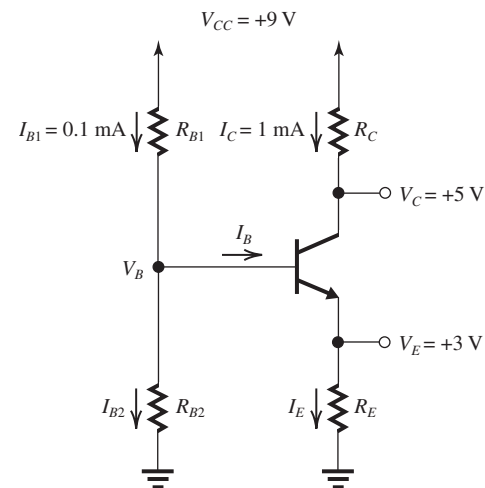


Figure 6.9.2

The circuit is shown in Fig. 6.9.2 with the required current and voltage values indicated. Observe that since V_C is higher than V_E by more than 0.3 V, the BJT will be operating in the active mode. The required value of R_C can be found from

$$R_C = \frac{V_{CC} - V_C}{I_C} = \frac{9 - 5}{1 \text{ mA}} = 4 \text{ k}\Omega$$

We can determine I_B from

$$I_B = \frac{I_C}{\beta} = \frac{1 \text{ mA}}{100} = 0.01 \text{ mA}$$

and thus

$$I_E = I_C + I_B = 1 + 0.01 = 1.01 \text{ mA}$$

Now, the value of R_E can be found from

$$R_E = \frac{V_E}{I_E} = \frac{3 \text{ V}}{1.01 \text{ mA}} = 2.97 \text{ k}\Omega$$

The base voltage V_B can be found as

$$V_B = V_E + V_{BE} = 3 + 0.7 = 3.7 \text{ V}$$



The value of R_{B1} can be then found from

$$R_{B1} = \frac{V_{CC} - V_B}{I_{B1}} = \frac{9 - 3.7}{0.1 \text{ mA}} = 53 \text{ k}\Omega$$

A node equation at the base yields the value of the current I_{B2} as

$$\begin{aligned} I_{B2} &= I_{B1} - I_B \\ &= 0.1 - 0.01 = 0.09 \text{ mA} \end{aligned}$$

The required value of R_{B2} can now be found as

$$R_{B2} = \frac{V_B}{I_{B2}} = \frac{3.7}{0.09} = 41.1 \text{ k}\Omega$$

6.10

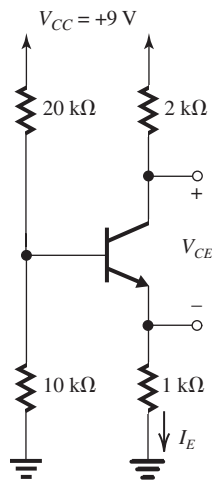


Figure 6.10.1

Using Thevenin's theorem, we can replace the voltage divider across V_{CC} with

$$V_{BB} = V_{CC} \times \frac{10}{10 + 20} = 9 \times \frac{10}{10 + 20} = +3 \text{ V}$$

and

$$R_{BB} = 10 || 20 = 6.67 \text{ k}\Omega$$

The resulting circuit with this simplification is shown in Fig. 6.10.2. Noting that the current in the base is

$$I_B = \frac{I_E}{\beta + 1}$$

we can write a loop equation for the loop containing V_{BB} , R_{BB} , and the emitter circuit as

$$V_{BB} = \frac{I_E}{\beta + 1} R_{BB} + V_{BE} + I_E R_E$$

from which I_E can be found as

$$I_E = \frac{V_{BB} - V_{BE}}{R_E + \frac{R_{BB}}{\beta + 1}}$$

Substituting $V_{BB} = 3 \text{ V}$, $V_{BE} = 0.7 \text{ V}$, and $R_E = 1 \text{ k}\Omega$, we obtain

$$I_E = \frac{3 - 0.7}{1 + \frac{6.67}{\beta + 1}} = \frac{2.3}{1 + \frac{6.67}{\beta + 1}} \quad (1)$$

The voltage V_E can then be found as

$$V_E = I_E R_E = I_E \times 1 = I_E \quad (2)$$

The collector current I_C is obtained as

$$I_C = \alpha I_E = \frac{\beta}{\beta + 1} I_E \quad (3)$$

and the collector voltage is found as

$$V_C = V_{CC} - I_C R_C = 9 - 2I_C \quad (4)$$

Finally, V_{CE} can be calculated from

$$V_{CE} = V_C - V_E \quad (5)$$

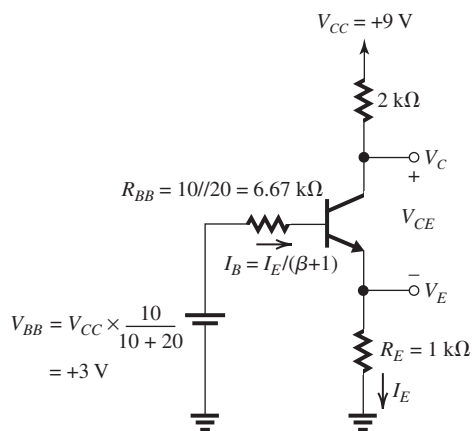


Figure 6.10.2

Using Eqs. (1)–(5), we can obtain the following results for the three β values specified:

Case	β	I_E (mA)	V_E (V)	I_C (mA)	V_C (V)	V_{CE} (V)
a	∞	2.3	+2.3	2.3	+4.4	+2.1
b	100	2.16	+2.16	2.14	+4.72	+2.56
c	10	1.43	+1.43	1.30	+6.40	+4.97

Observe that in all cases V_{CE} is greater than 0.3 V, confirming that the transistor is operating in the active mode, as implicitly assumed.

(a) $\beta = \infty$. Assume active-mode operation for both transistors. The sequence of analysis steps is as follows:

6.11

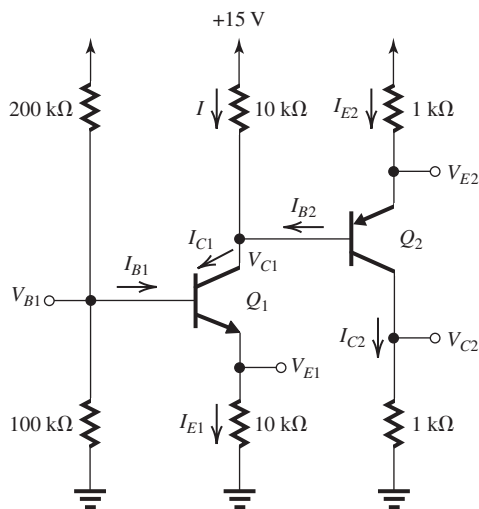


Figure 6.11.1

- (1) $I_{B1} = 0$
- (2) $V_{B1} = 15 \times \frac{100}{100+200} = +5 \text{ V}$.
- (3) $V_{E1} = V_{B1} - V_{BE1} = 5 - 0.7 = +4.3 \text{ V}$
- (4) $I_{E1} = \frac{V_{E1}}{10 \text{ k}\Omega} = \frac{4.3}{10} = 0.43 \text{ mA}$
- (5) $I_{C1} = \alpha_1 I_{E1} = 1 \times 0.43 = 0.43 \text{ mA}$
- (6) $I_{B2} = 0$
- (7) $I = I_{C1} = 0.43 \text{ mA}$
- (8) $V_{C1} = 15 - 0.43 \times 10 = +10.7 \text{ V}$
- (9) $V_{E2} = V_{C1} + V_{EB2} = 10.7 + 0.7 = +11.4 \text{ V}$
- (10) $I_{E2} = \frac{15 - V_{E2}}{1 \text{ k}\Omega} = \frac{15 - 11.4}{1} = 3.6 \text{ mA}$
- (11) $I_{C2} = \alpha_2 \times I_{E2} = 1 \times 3.6 = 3.6 \text{ mA}$
- (12) $V_{C2} = I_{C2} \times 1 = 3.6 \times 1 = +3.6 \text{ V}$

Check: (1) $V_{C1} = +10.7 \text{ V}$ is higher than $V_{B1} = +5 \text{ V}$, verifying that Q_1 is in the active mode.
 (2) $V_{C2} = +3.6 \text{ V}$ is lower than $V_{B2} = V_{C1} = +10.7 \text{ V}$, verifying that Q_2 is in the active mode.

(b) Refer to Figure 6.11.2 below.

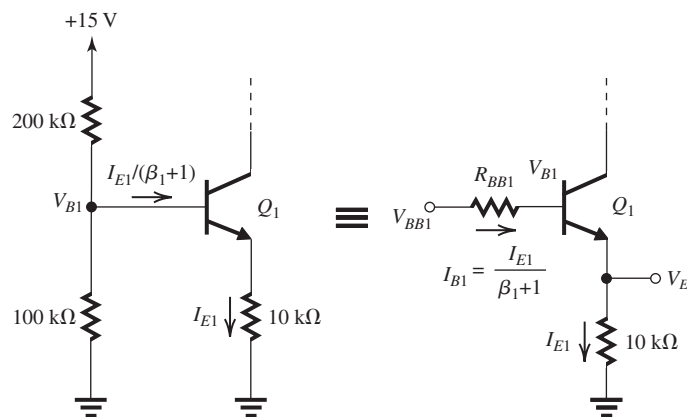


Figure 6.11.2



$\beta = 100$. Assume both transistors are operating in the active mode. To simplify the analysis, we replace the voltage divider that is connected to the base of Q_1 with its Thevenin equivalent, as shown in Fig. 6.11.2, where

$$V_{BB1} = 15 \times \frac{100}{100 + 200} = +5 \text{ V}$$

and

$$R_{BB1} = 100 \text{ k}\Omega \parallel 200 \text{ k}\Omega = 66.7 \text{ k}\Omega$$

Writing a loop equation for the base-emitter circuit of Q_1 enables us to find I_{E1} as

$$I_{E1} = \frac{V_{BB1} - V_{BE1}}{10 + \frac{R_{BB1}}{\beta_1 + 1}} = \frac{5 - 0.7}{10 + \frac{66.7}{100 + 1}} = 0.403 \text{ mA}$$

Continuing with the analysis:

$$I_{B1} = \frac{I_{E1}}{\beta_1 + 1} = \frac{0.403}{101} = 4 \mu\text{A}$$

$$V_{E1} = I_{E1} \times 10 = +4.03 \text{ V}$$

$$I_{C1} = \alpha_1 I_{E1} = \frac{\beta_1}{\beta_1 + 1} I_{E1} = 0.99 \times 0.403 = 0.4 \text{ mA}$$

The remainder of the analysis can be simplified by replacing the circuit that is connected to the base of Q_2 by its Thevenin equivalent, as shown in Fig. 6.11.3 (refer Figure below).

Here, we have considered the collector of Q_1 as a constant-current source I_{C1} . Thus,

$$V_{BB2} = 15 - I_{C1} \times 10 = 15 - 0.4 \times 10 = 11 \text{ V}$$

$$R_{BB2} = 10 \text{ k}\Omega$$

Writing a loop equation for the base-emitter circuit of Q_2 , we can obtain I_{E2} as

$$I_{E2} = \frac{15 - V_{EB2} - V_{BB2}}{1 + \frac{R_{BB2}}{\beta_2 + 1}} = \frac{15 - 0.7 - 11}{1 + \frac{10}{101}} = 3 \text{ mA}$$

Continuing with the analysis:

$$V_{E2} = 15 - I_{E2} \times 1 = +12 \text{ V}$$

$$V_{C1} = V_{E2} - V_{EB2} = 12 - 0.7 = +11.3 \text{ V}$$

$$I_{B2} = \frac{I_{E2}}{\beta_2 + 1} = \frac{3}{101} = 0.03 \text{ mA}$$

$$I = I_{C1} - I_{B2} = 0.4 - 0.03 = 0.37 \text{ mA}$$

$$I_{C2} = \alpha_2 I_{E2} = 0.99 \times 3 = 2.97 \text{ mA}$$

$$V_{C2} = I_{C2} \times 1 = 2.97 \text{ V}$$

Check: $V_{C1} (+11.3 \text{ V}) > V_{B1} (+4.73 \text{ V})$, thus Q_1 is in active mode; and $V_{C2} (+2.97 \text{ V}) < V_{B2} (+11.3 \text{ V})$, thus Q_2 is in active mode.

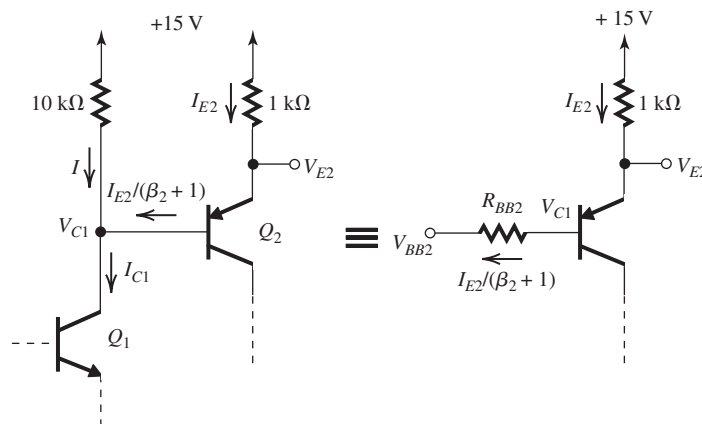


Figure 6.11.3

As a summary, Fig. 6.11.4 shows the results for the case $\beta = \infty$, and Fig. 6.11.5 shows the results for the case $\beta = 100$.

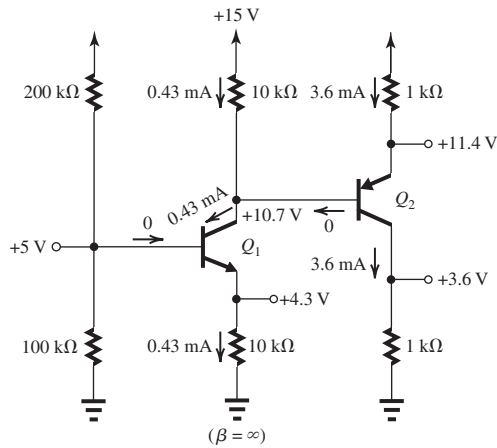


Figure 6.11.4

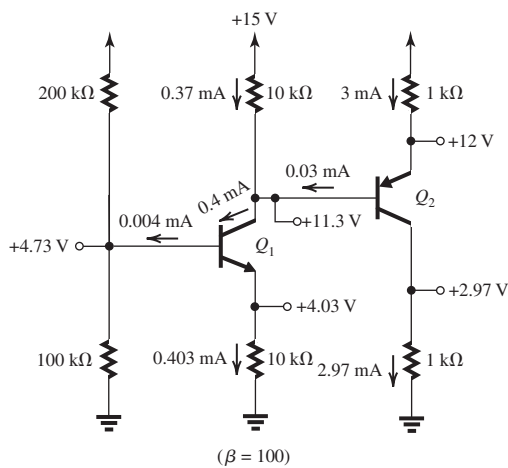


Figure 6.11.5

6.12

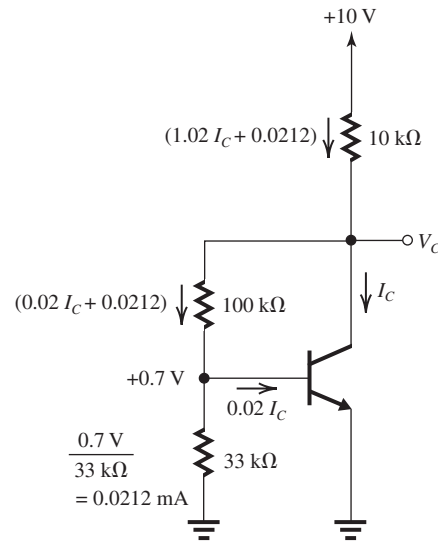


Figure 6.12.2

Figure 6.12.2 shows the circuit with most of the analysis. Here, since V_C is greater than V_B by the voltage drop across the 100-k Ω resistor, the transistor will be operating in the active mode. Our analysis assumed a collector current I_C and determined the base current as $I_C/\beta = I_C/50 = 0.02I_C$. The 33-k Ω resistor has a voltage across it equal to V_{BE} , that is, 0.7 V; thus, its current is $0.7/3.3 = 0.0212$ mA. A node equation at the base yields the current through the 100-k Ω resistor, and a node equation at the collector provides the current through the 10-k Ω resistor.

Now, writing an equation for the voltage between the supply (+10 V) to ground, we obtain

$$10 = 10(1.02I_C + 0.0212) + 100(0.02I_C + 0.0212) + 0.7$$

This equation can be solved to obtain

$$I_C = 0.571 \text{ mA}$$

Finally, the voltage V_C can be found from

$$\begin{aligned} V_C &= 10 - (1.02I_C + 0.0212) \times 10 \\ &= 10 - 10.2 \times 0.571 - 0.212 \\ V_C &= 3.96 \text{ V} \end{aligned}$$