



UNIVERSITY OF RWANDA  
COLLEGE OF SCIENCE & TECHNOLOGY  
SCHOOL OF ENGINEERING  
DEPARTMENT OF ELECTRICAL & ELECTRONICS ENGINEERING

DR. KIZITO NKURIKIYEYEU

EPE 2165—ANALOG ELECTRONICS

## **HOMEWORK #2—diode circuits**

Question:	1	2	3	4	5	Total
Points:	20	10	10	20	40	100
Score:						

*Issued on:*

*June 23, 2022*

*Due on:*

*June 30, 2022*

1. **Figure 1** represents a portion of battery-charger circuit for a battery with a voltage  $V_B$ . The sine-wave input  $v_S = 12\text{ V}(rms)$ , while the battery voltage varies from 12 V to 14 V from the discharged to fully charged states. The charging-source resistance  $R_S = 10\ \Omega$ . Assuming that  $D$  is an ideal diode, and  $R_C = 50\ \Omega$  is a current-controlling resistor established by the designer:

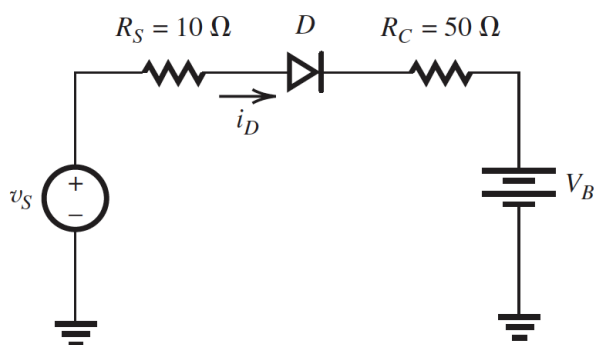


FIGURE 1. Battery-charger circuit

- (a) (10 points) Sketch and label the voltage waveforms of the voltage across the diode and the current through the diode for  $V_B = 12\text{ V}$ .
  - (b) (10 points) What is the peak diode current?
2. (10 points) For the circuits shown in **Figure 2**, using ideal diodes, find the values the output voltage  $V_O$  and the currents  $I_{D1}$  and  $I_{D2}$ .
  3. (10 points) The diode in the circuit shown in **Figure 3** has a reverse-saturation current of  $I_s = 5 \times 10^{-11}\text{ A}$ . Determine the diode voltage  $V_D$  and current  $I_D$ .

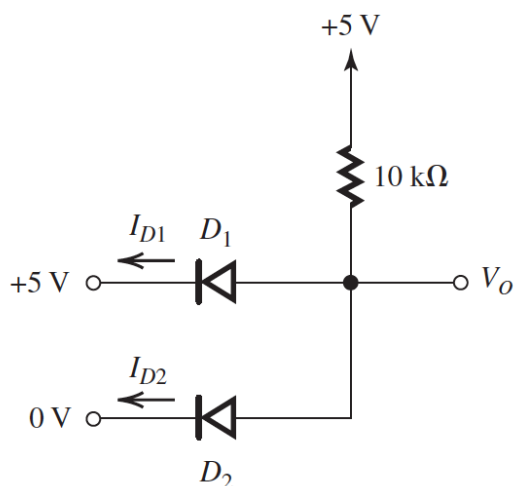


FIGURE 2



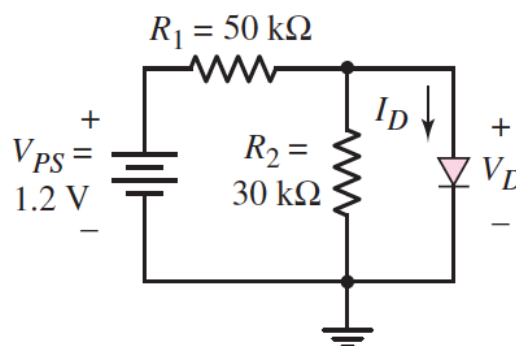


FIGURE 3

4. (20 points) **Figure 4** shows a 4 diode circuit. The 4 diodes are identical and each diode exhibits a voltage drop of  $V_D = 0.7V$  at a 1 mA current. For small input signals (e.g., 10-mV peak), find the small-signal equivalent circuit and use it to determine values of the small-signal transmission  $v_o/v_i$  for a current  $I = 1 \mu A$
5. Consider a half-wave rectifier circuit shown in **Figure 5**.

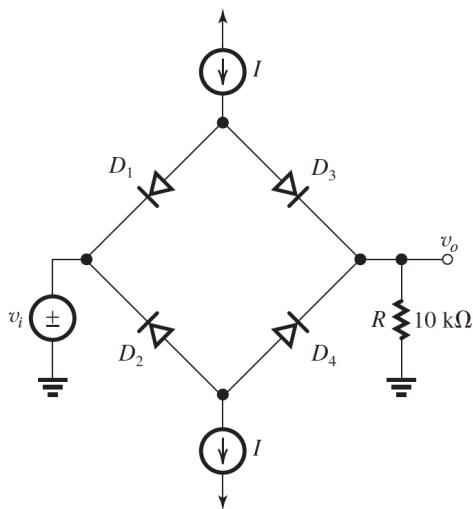

**FIGURE 4**

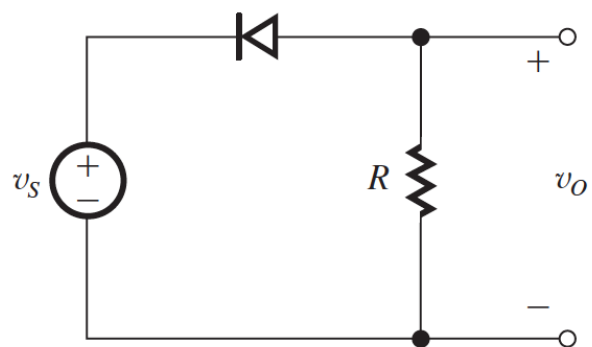

**FIGURE 5**

Let  $v_s$  be a sinusoid with 10V peak amplitude, and let  $R = 1k$  . Use the constant-voltage-drop diode model with  $V_D = 0.7V$  .

- (10 points) Sketch the transfer characteristic.
- (10 points) Sketch the waveform of  $v_o$ .
- (10 points) Find the peak current in the diode.
- (10 points) Find the PIV of the diode