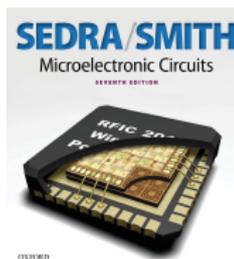


## Readings

- Section 4.3 on pages 193- 195



## Diode models

Kizito NKURIKIYEYEU,  
Ph.D.

- Readings are based on Sedra & Smith (2014), Microelectronic Circuits 7th edition.
- Bold reading sections are mandatory. Other sections are suggested but not required readings

Kizito NKURIKIYEYEU, Ph.D.

Diode models

June 1, 2022 1 / 11

## Background

How would you find  $I_D$  and  $V_D$  for the circuit in Fig. 2

- The current through the diode is the same as the current through the resistor

$$I = \frac{V_{DD} - V_D}{R} \quad (1)$$

- Similarly, from our previous lecture

$$I = I_s \left( e^{v/V_T} - 1 \right) \quad (2)$$

- Combining Equation (1) and Equation (2) allows to solve for the unknowns

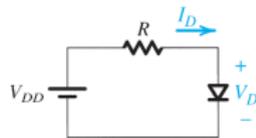


FIG 1. Illustrative diode circuit

## Background

- model** —a mathematical description or electrical equivalent circuit that represents the behavior of a device or system
- In this lecture, we shall learn simplified diode models that are suited for circuit analysis:

- Exponential model
- Constant voltage-drop model
- ideal diode model
- small-signal model


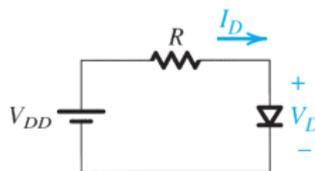


FIG 2. Illustrative diode circuit

# The exponential diode model

## Graphical analysis

- Plot the relationships of Equation (3) and Equation (4) on an  $i$ - $v$  plane.
- The solution is the **Q-point**—which is the coordinates of the point of intersection of the two graphs
- The Q point is also known as the operating point, the bias point, or quiescent point<sup>1</sup>
- The Q-point is the steady-state voltage or current at a specified terminal of an active diode with no input signal applied<sup>2</sup>

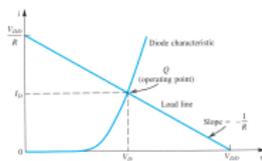

**FIG 3.** Illustration of the graphical analysis method using the exponential diode model

# The exponential diode model


- Most accurate model
- However, also most difficult to use:
  - For  $V_{DD} > 0.5V$ , Equation (3) holds true

$$I = I_s \left( e^{v_0/v_T} - 1 \right) \approx I_s \cdot e^{v_0/v_T} \quad (3)$$

- Since  $I_D = I_R$ , then

$$I_s \cdot e^{v_0/v_T} = \frac{V_{DD} - V_D}{R} \quad (4)$$

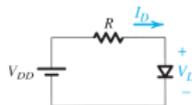- Combining Equation (3) and Equation (4) allows to solve for  $V_D$  and  $I_D$
- The value of  $V_D$  and  $I_D$  can also be obtained by graphical analysis and



## Iterative analysis<sup>1</sup>

**EXAMPLE**—Find  $I_D$  and  $V_D$  for the circuit in Section 1 when  $V_{DD} = 5V$  and  $R = 1k$ . Assume that the diode has a current of  $I_D = 1mA$  at a voltage of  $V_D = 0.7V$ .

- $I_D$  is found by KVL


$$I_D = \frac{V_{DD} - V_D}{R} = \frac{5V - 0.5V}{1k} = 4.5 \quad (5)$$

- $V_D$  is deduced from

$$V_2 - V_1 = 2.3V_T \cdot \log(I_2/I_1) \quad (6)$$

Since  $2.3V_T = 60mV$ , then
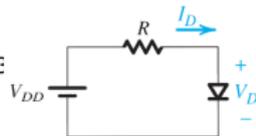
$$V_2 = V_1 + 0.06 \cdot \log(I_2/I_1) \quad (7)$$



<sup>1</sup>The graphical analysis is only used for visualization of simple circuit but it is

<sup>2</sup>See detailed electronic solution at

# Iterative analysis<sup>1</sup>

- The first iteration assumes  $V_1 = 0.7V$ ,  $I_1 = 1mA$  and  $I_2 = 4.3mA$  that we calculated earlier. Thus,  $V_D = 0.738V$
- The second iteration goes through the same process

$$I_D = \frac{V_{DD} - V_D}{R} = \frac{5V - 0.738V}{1k} = 4.262mA \quad (8)$$

$$\begin{aligned} V_2 &= V_1 + 0.06 \cdot \log(I_2/I_1) \\ &= 0.738V + 0.06 \cdot \log(4.262/4.3) \\ &= 0.738V \end{aligned} \quad (9)$$

- The iteration can continue but the second iteration yielded values close to the first iteration, there is no reason to continue any further.

■ Thus,  $I_D \approx 4.262mA$  and  $V_D \approx 0.738V$

<sup>1</sup>See detailed algebraic solution at

[https://en.wikipedia.org/wiki/Diode\\_modelling#Iterative\\_solution](https://en.wikipedia.org/wiki/Diode_modelling#Iterative_solution)


# The Constant-Voltage-Drop Model

# Iterative analysis—Practicality


- This method is simple and very accurate
- However, it is very slow and not practical. Circuit design requires evaluating various possibility before making a suitable design
- In practice, analog circuit design is something of an art. Although it is possible to predict the behavior of a very simple circuit mathematically, there are so many factors to consider in a more complicated circuit that the calculations become impossibly convoluted
- It is best to use less accurate methods and verify the design with computer analysis tools such as SPICE
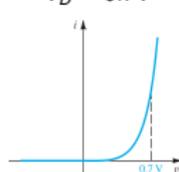
# The Constant-Voltage-Drop Model


- The simplest and most widely used diode model in the initial phases of analysis and design
- Since the forward-conducting diode has a voltage drop that varies in a relatively narrow range (usually between 0.6 to 0.8 V), assumes that that the slope of the i-v curve is vertical at  $V_D = 0.7V$



(a) The exponential characteristic

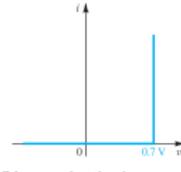

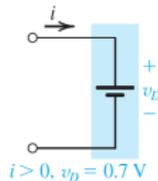(b) approximating by a constant voltage (usually  $V_D = 0.7V$ )



(c) the resulting model of the forward-conducting diodes  
 $i > 0, v_D = 0.7V$

FIG 4. Development of the diode constant-voltage-drop model:

# The Ideal-Diode Model

- Useful for applications that involve voltages much greater than the diode voltage drop
- In this case, we may neglect the diode voltage drop altogether while calculating the diode current.
- In summary, the ideal diode model assumes that the slope of i-v curve is vertical at  $V_D = 0V$

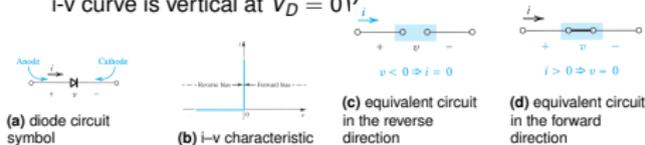


FIG 5. The ideal diode model

# Summary —When to use these models

- exponential model
  - low voltages
  - less complex circuits
  - emphasis on accuracy over practicality
- constant voltage-drop mode
  - medium voltages = 0.7V
  - more complex circuits
  - emphasis on practicality over accuracy
- ideal diode model
  - high voltages » 0.7V
  - very complex circuits
  - cases where a difference in voltage by 0.7V is negligible
- small-signal model
  - Coming soon!