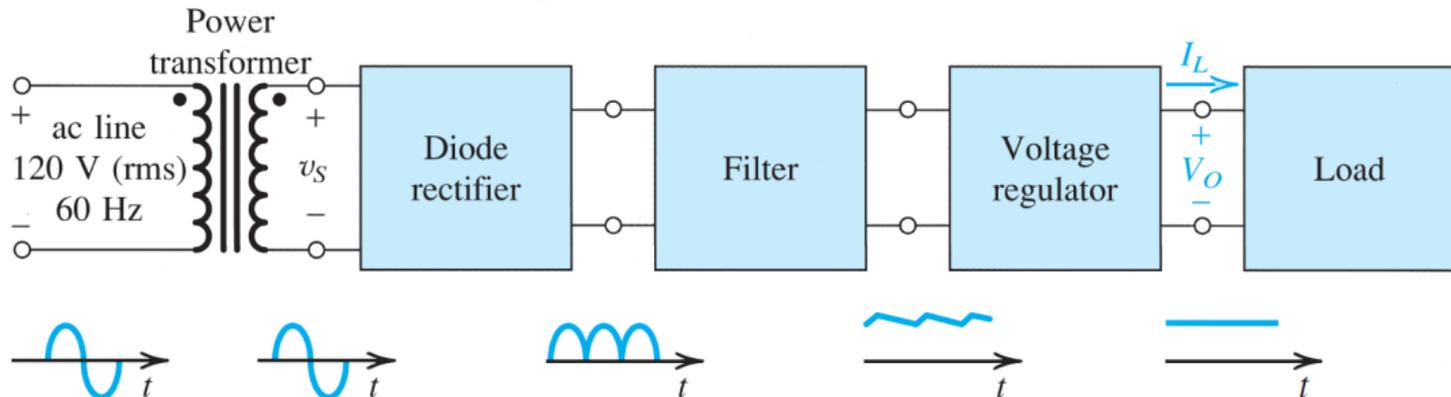


# Rectifier Circuits

Kizito NKURIKIYEYEU, Ph.D.

# Rectifier Circuits

- The most important applications of diodes is in the design of rectifier circuits
- Rectifiers converts alternating current (AC) to DC current<sup>1</sup>




**FIG 1. Block diagram of a dc power supply**

The power supply is fed from the 120-V (rms) 60-Hz ac line, and it delivers a dc voltage  $V_O$  (usually in the range of 4 V to 20 V) to an electronic circuit represented by the load block. The dc voltage  $V_O$  is required to be as constant as possible in spite of variations in the ac line voltage and in the current drawn by the load.

<sup>1</sup><https://en.wikipedia.org/wiki/Rectifier>

# Rectifier Circuits

- The most important applications of diodes is in the design of rectifier circuits
- Rectifiers converts alternating current (AC) to DC current<sup>1</sup>

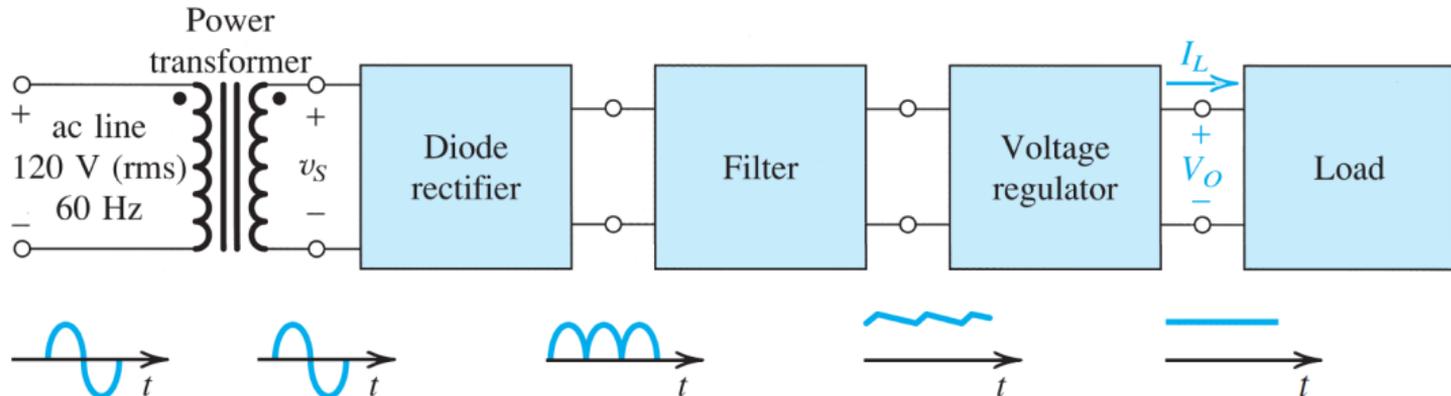

**FIG 1. Block diagram of a dc power supply**


The power supply is fed from the 120-V (rms) 60-Hz ac line, and it delivers a dc voltage  $V_O$  (usually in the range of 4 V to 20 V) to an electronic circuit represented by the load block. The dc voltage  $V_O$  is required to be as constant as possible in spite of variations in the ac line voltage and in the current drawn by the load.

<sup>1</sup><https://en.wikipedia.org/wiki/Rectifier>

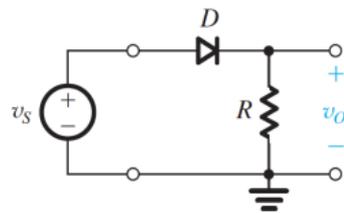
# Half-wave rectifier

- A half-wave rectifier utilizes alternate half-cycles of the input sinusoid
- If we use the constant voltage drop diode model in Fig. 2:


$$v_O = \begin{cases} 0, & \text{if } v_S < V_D \\ v_S - V_D & \text{otherwise} \end{cases} \quad (1)$$



(a) Half-wave rectifier.

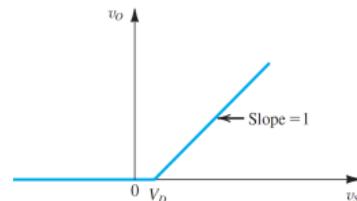

(b) Transfer characteristic

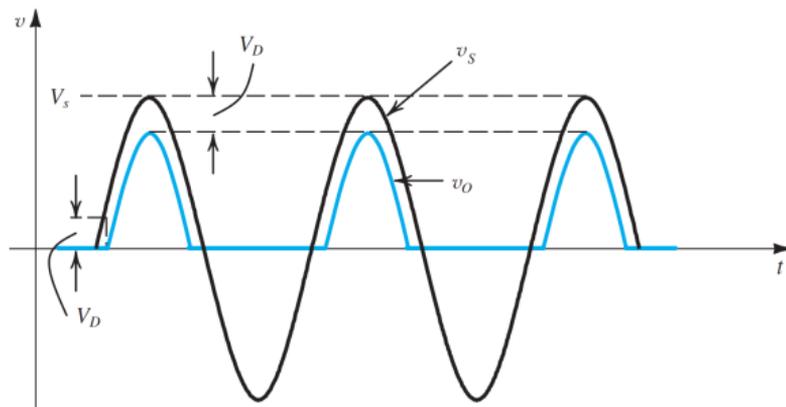

(c) Input and output waveforms


**FIG 2.** Characteristics of a half-wave rectifier

<sup>1</sup> <https://www.physics-and-radio-electronics.com/electronic-devices-and-circuits/rectifier/>

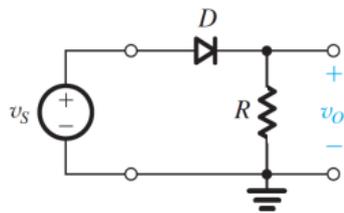
# Half-wave rectifier

- A half-wave rectifier utilizes alternate half-cycles of the input sinusoid
- If we use the constant voltage drop diode model in Fig. 2:


$$v_O = \begin{cases} 0, & \text{if } v_S < V_D \\ v_S - V_D & \text{otherwise} \end{cases} \quad (1)$$



(a) Half-wave rectifier.

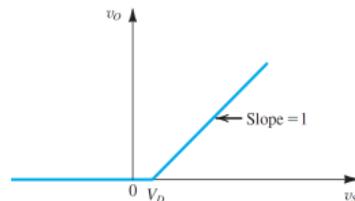

(b) Transfer characteristic

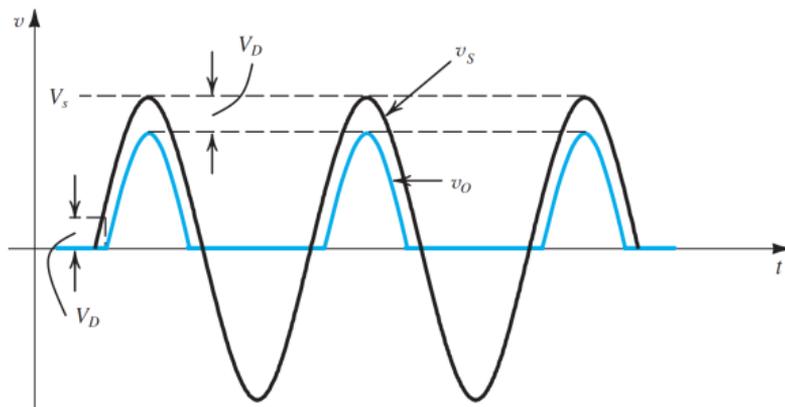

(c) Input and output waveforms

**FIG 2.** Characteristics of a half-wave rectifier

<sup>1</sup><https://www.physics-and-radio-electronics.com/electronic-devices-and-circuits/rectifier/>

# Half-wave rectifier

In selecting diodes for rectifier design, two important parameters must be specified

- **current-handling capability**—what is maximum forward current diode is expected to conduct?
- **peak inverse voltage (PIV)**—what is maximum reverse voltage it is expected to block without breakdown?

- When  $v_s < 0$ , the diode will be cut off and  $v_o$  will be zero and  $PIV$  is equal to the peak of  $v_s$  (Equation (2))

$$PIV = V_s \quad (2)$$

- It is usually prudent, however, to select a diode that has a reverse breakdown voltage at least 50% greater than the expected  $PIV$ .

## ■ Note:

- It is possible to use the diode exponential model in describing rectifier operation; however, this requires too much work
- The rectifier does not work well for small input voltage (e.g.,  $v_s < 100mV$ ). In this case, a precision rectifier (circuit with diode and op-amps) should be used.

# Half-wave rectifier

In selecting diodes for rectifier design, two important parameters must be specified

- **current-handling capability**—what is maximum forward current diode is expected to conduct?
- **peak inverse voltage (PIV)**—what is maximum reverse voltage it is expected to block without breakdown?

- When  $v_s < 0$ , the diode will be cut off and  $v_o$  will be zero and  $PIV$  is equal to the peak of  $v_s$  (Equation (2))

$$PIV = V_s \quad (2)$$

- It is usually prudent, however, to select a diode that has a reverse breakdown voltage at least 50% greater than the expected  $PIV$ .

## ■ Note:

- It is possible to use the diode exponential model in describing rectifier operation; however, this requires too much work
- The rectifier does not work well for small input voltage (e.g.,  $v_s < 100mV$ ). In this case, a precision rectifier (circuit with diode and op-amps) should be used.

# Half-wave rectifier

In selecting diodes for rectifier design, two important parameters must be specified

- **current-handling capability**—what is maximum forward current diode is expected to conduct?
- **peak inverse voltage (PIV)**—what is maximum reverse voltage it is expected to block without breakdown?
  - When  $v_s < 0$ , the diode will be cut off and  $v_o$  will be zero and  $PIV$  is equal to the peak of  $v_s$  (**Equation (2)**)

$$PIV = V_s \quad (2)$$

- It is usually prudent, however, to select a diode that has a reverse breakdown voltage at least 50% greater than the expected  $PIV$ .
- **Note:**
  - It is possible to use the diode exponential model in describing rectifier operation; however, this requires too much work
  - The rectifier does not work well for small input voltage (e.g.,  $v_s < 100mV$ ). In this case, a precision rectifier (circuit with diode and op-amps) should be used.

# Half-wave rectifier

In selecting diodes for rectifier design, two important parameters must be specified

- **current-handling capability**—what is maximum forward current diode is expected to conduct?
- **peak inverse voltage (PIV)**—what is maximum reverse voltage it is expected to block without breakdown?
  - When  $v_s < 0$ , the diode will be cut off and  $v_o$  will be zero and  $PIV$  is equal to the peak of  $v_s$  (**Equation (2)**)

$$PIV = V_s \quad (2)$$

- It is usually prudent, however, to select a diode that has a reverse breakdown voltage at least 50% greater than the expected  $PIV$ .
- **Note:**
  - It is possible to use the diode exponential model in describing rectifier operation; however, this requires too much work
  - The rectifier does not work well for small input voltage (e.g.,  $v_s < 100mV$ ). In this case, a precision rectifier (circuit with diode and op-amps) should be used.

# Half-wave rectifier

In selecting diodes for rectifier design, two important parameters must be specified

- **current-handling capability**—what is maximum forward current diode is expected to conduct?
- **peak inverse voltage (PIV)**—what is maximum reverse voltage it is expected to block without breakdown?
  - When  $v_s < 0$ , the diode will be cut off and  $v_o$  will be zero and  $PIV$  is equal to the peak of  $v_s$  (**Equation (2)**)

$$PIV = V_s \quad (2)$$

- It is usually prudent, however, to select a diode that has a reverse breakdown voltage at least 50% greater than the expected  $PIV$ .
- **Note:**
  - It is possible to use the diode exponential model in describing rectifier operation; however, this requires too much work
  - The rectifier does not work well for small input voltage (e.g.,  $v_s < 100mV$ ). In this case, a precision rectifier (circuit with diode and op-amps) should be used.

# Half-wave rectifier

In selecting diodes for rectifier design, two important parameters must be specified

- **current-handling capability**—what is maximum forward current diode is expected to conduct?
- **peak inverse voltage (PIV)**—what is maximum reverse voltage it is expected to block without breakdown?
  - When  $v_s < 0$ , the diode will be cut off and  $v_o$  will be zero and  $PIV$  is equal to the peak of  $v_s$  (**Equation (2)**)


$$PIV = V_s \quad (2)$$

- It is usually prudent, however, to select a diode that has a reverse breakdown voltage at least 50% greater than the expected  $PIV$ .
- **Note:**
  - It is possible to use the diode exponential model in describing rectifier operation; however, this requires too much work
  - The rectifier does not work well for small input voltage (e.g.,  $v_s < 100mV$ ). In this case, a precision rectifier (circuit with diode and op-amps) should be used.


# Full-wave rectifier
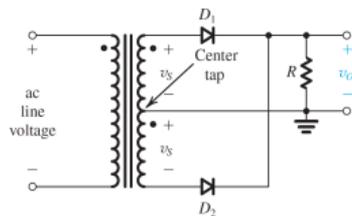
# Full-wave rectifier


- The full-wave rectifier utilizes both halves of the input sinusoid.
- The center-tapping of the transformer, allowing “reversal” of certain currents



(a) Full-wave rectifier circuit

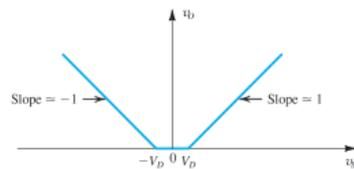

(b) Transfer characteristic

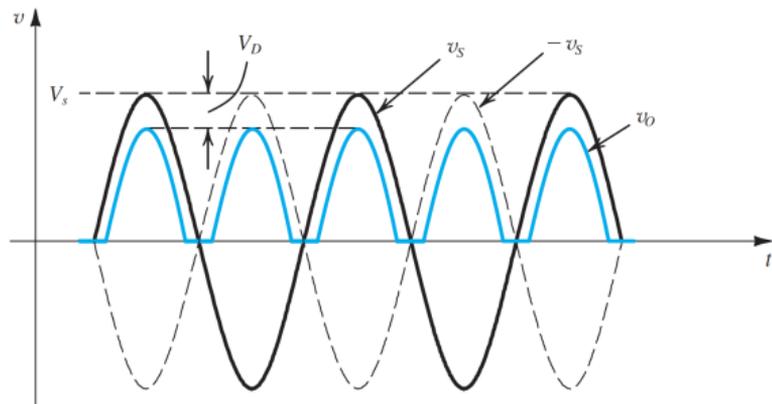


(c) Input and output waveforms


**FIG 3.** Full-wave rectifier utilizing a transformer with a center-tapped secondary winding
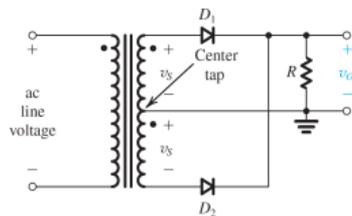
# Full-wave rectifier


- The full-wave rectifier utilizes both halves of the input sinusoid.
- The center-tapping of the transformer, allowing “reversal” of certain currents



(a) Full-wave rectifier circuit

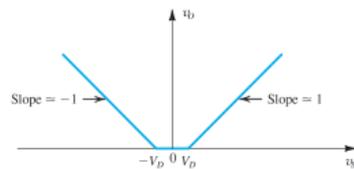

(b) Transfer characteristic

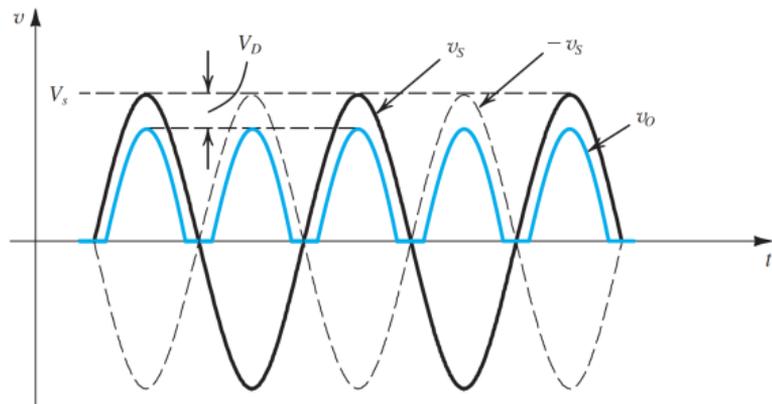


(c) Input and output waveforms

**FIG 3.** Full-wave rectifier utilizing a transformer with a center-tapped secondary winding
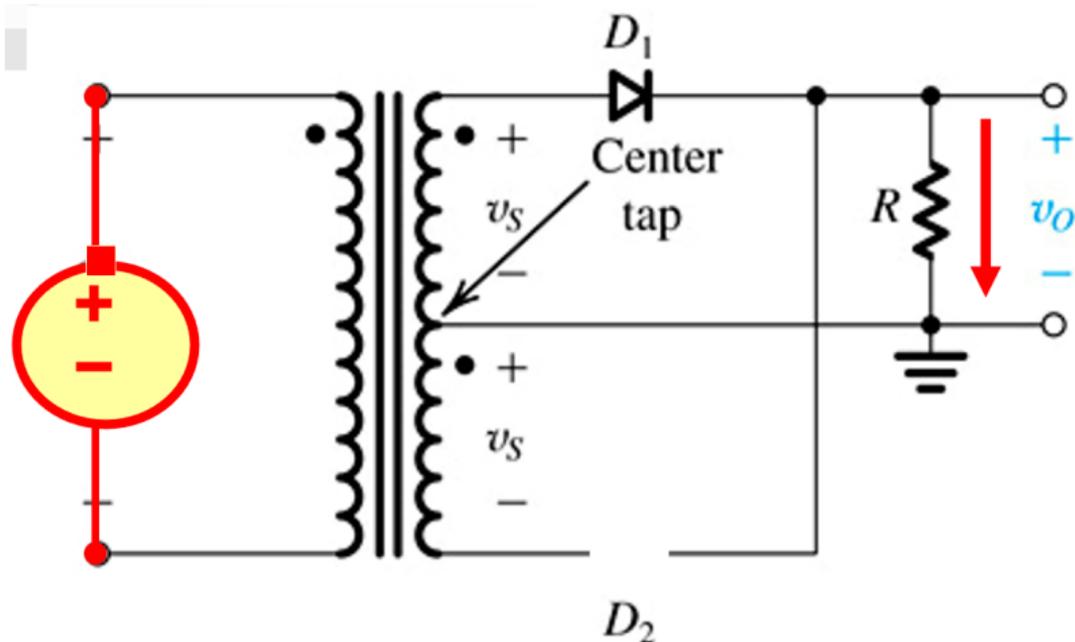
# Working principle


When  $v_s > 0$ ,  $D_1$  conducts while  $D_2$  will be reverse biased. The current through  $D_1$  will flow through  $R$  and back to the center tap of the secondary.




<sup>1</sup> <https://www.physics-and-radio-electronics.com/electronic-devices-and-circuits/rectifier/fullwaverectifier.html>
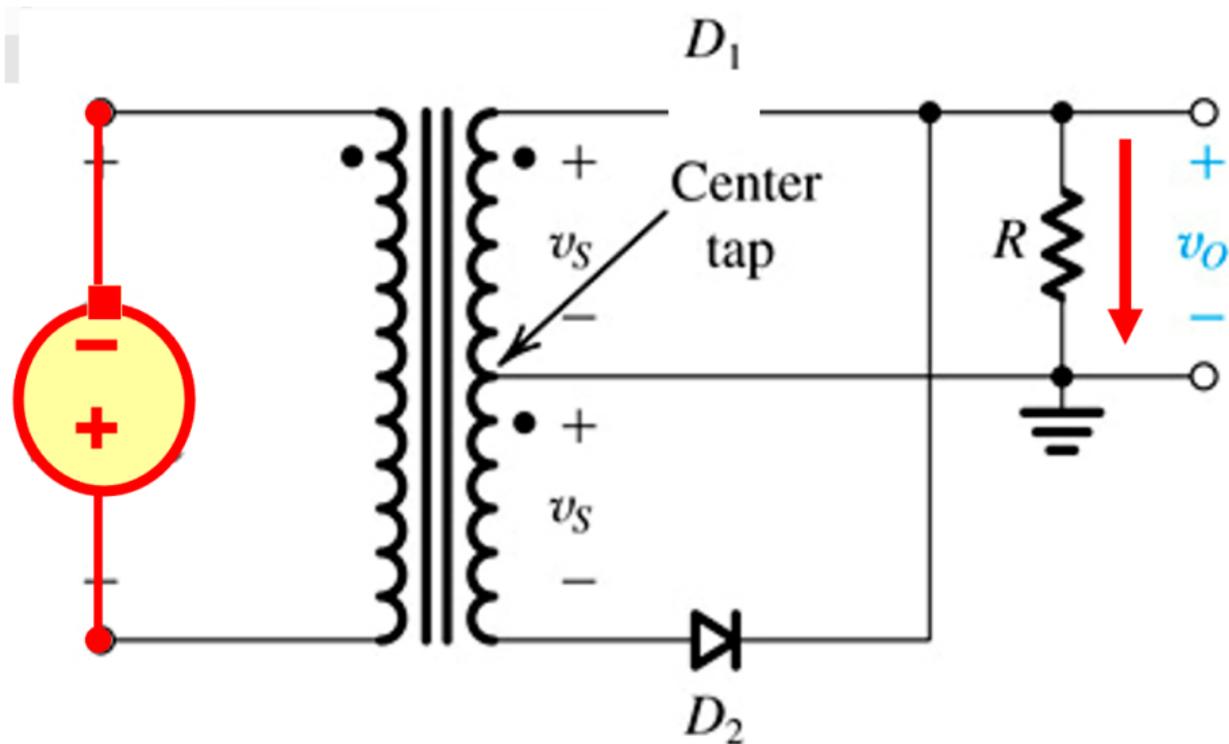
# Working principle

When  $v_s < 0$ , the situation reverses:  $D_2$  conducts while  $D_1$  blocks



# Working principle

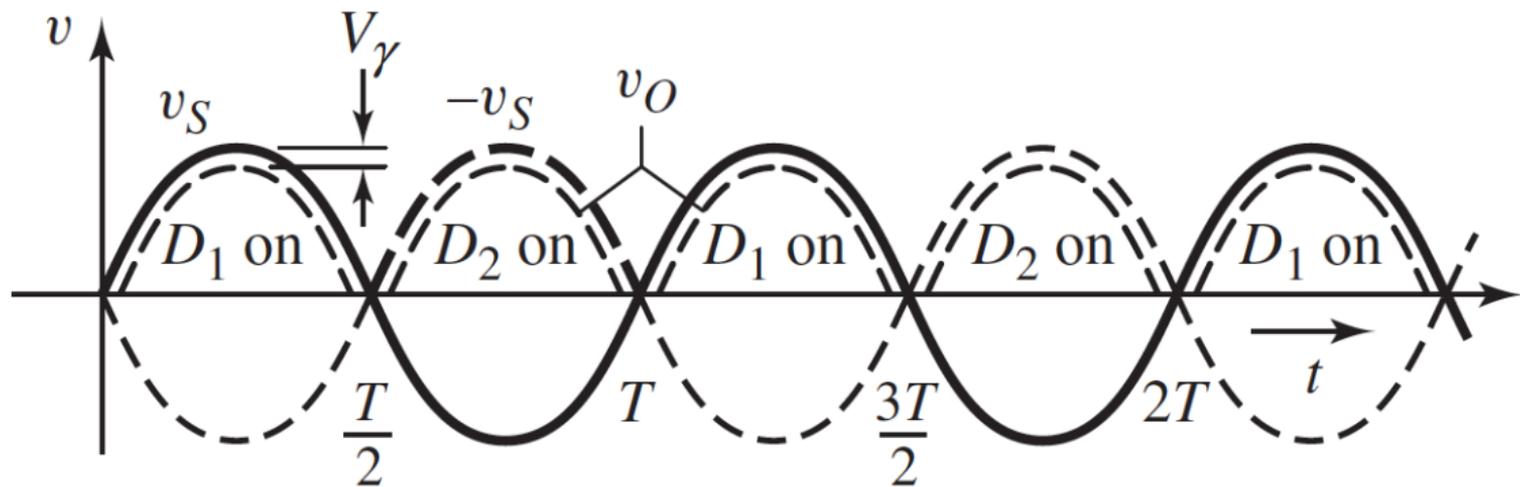

**FIG 4. Full-wave rectifier working principle**

When  $v_s > V_D$ ,  $D_1$  is on and  $D_2$  is off. The output voltage is then  $v_o = v_s - V_D$ . When  $v_s < V_D$ , then for  $v_s < -V_D$  or  $-v_s > V_D$ ,  $D_1$  is off and  $D_2$  is on. The output voltage is  $v_o = -v_s - V_D$ <sup>1</sup>

<sup>1</sup> Adapted from Neamen, D. (2009). Microelectronics Circuit Analysis and Design (4th ed.)

# Peak inverse voltage


- The direction of current flowing across load never changes (both halves of AC wave are rectified). The full-wave rectifier produces a more “energetic” waveform than half-wave
- During the positive half-cycle:
  - diode  $D_1$  is conducting, and  $D_2$  is cut off. The voltage at the cathode of  $D_2$  is  $v_o$ , and that at its anode is  $-v_s$ .
  - The reverse voltage across  $D_2$  is  $v_o + v_s$ , and reaches the maximum when  $v_o$  is at its peak value of  $V_p = V_s - V_D$
  - The peak inverse voltage is approximately twice that for the case of the half-wave rectifier as shown in Equation (3)

$$PIV = 2V_s - V_D \quad (3)$$


# Bridge rectifier
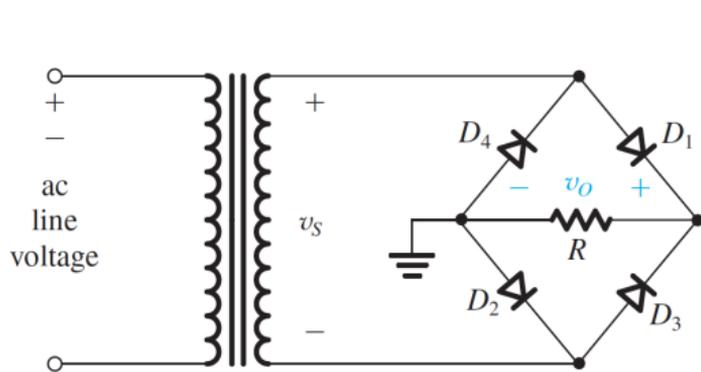
# Bridge rectifier

- Provides electrical isolation between the input ac powerline and the rectifier output, but does not require a center-tapped secondary winding.
- Uses four diodes, compared to only two in the previous circuit.
- Its Peak inverse voltage  $V_{IP} = V_s - 2V_D - V_D = V_s - V_D$  and is about half the value for the full-wave rectifier with a center-tapped transformer.



(a) Bridge rectifier circuit

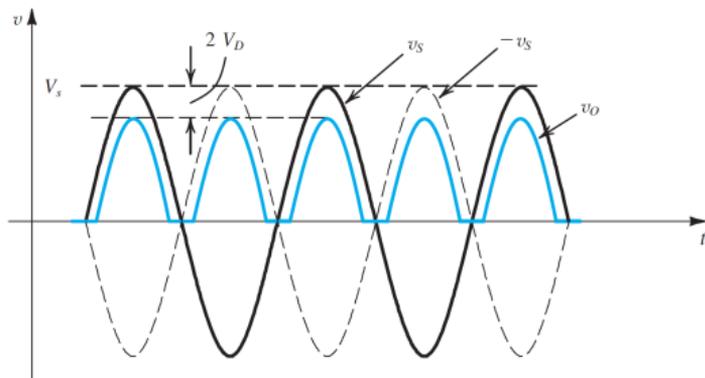


(b) input and output waveforms


FIG 5. A bridge rectifier
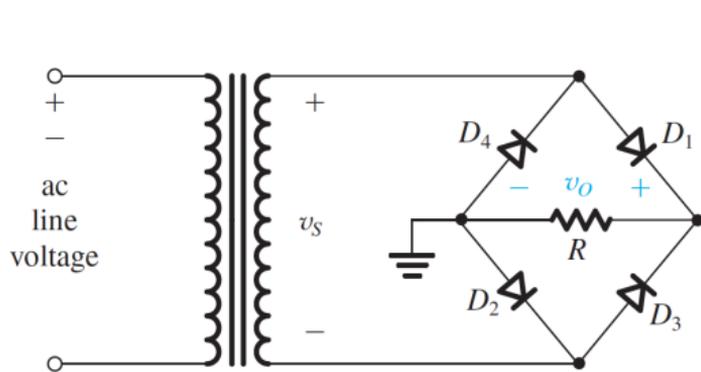
# Bridge rectifier

- Provides electrical isolation between the input ac powerline and the rectifier output, but does not require a center-tapped secondary winding.
- Uses four diodes, compared to only two in the previous circuit.
- Its Peak inverse voltage  $V_{IP} = V_s - 2V_D - V_D = V_s - V_D$  and is about half the value for the full-wave rectifier with a center-tapped transformer.



(a) Bridge rectifier circuit

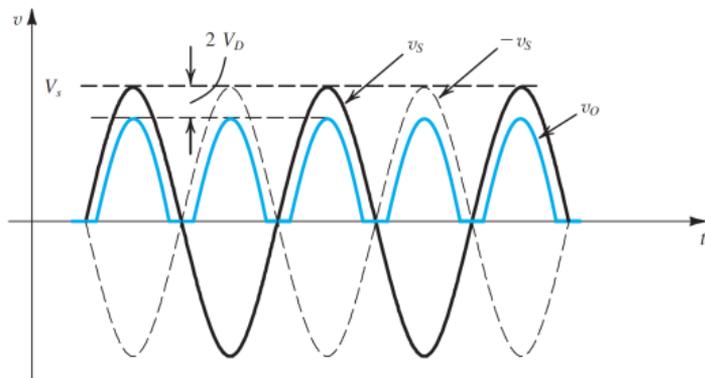


(b) input and output waveforms


FIG 5. A bridge rectifier
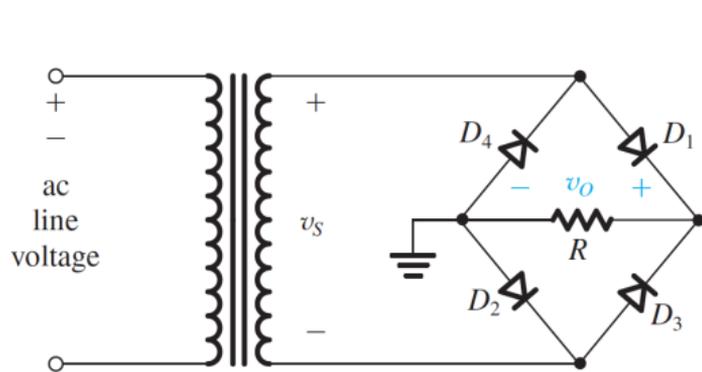
# Bridge rectifier

- Provides electrical isolation between the input ac powerline and the rectifier output, but does not require a center-tapped secondary winding.
- Uses four diodes, compared to only two in the previous circuit.
- Its Peak inverse voltage  $V_{IP} = V_s - 2V_D - V_D = V_s - V_D$  and is about half the value for the full-wave rectifier with a center-tapped transformer.



(a) Bridge rectifier circuit

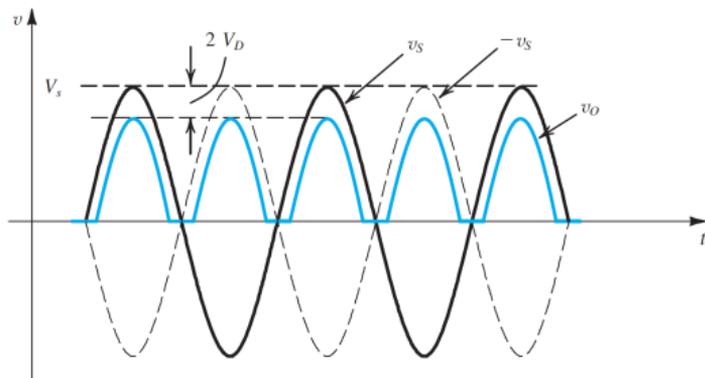


(b) input and output waveforms

FIG 5. A bridge rectifier

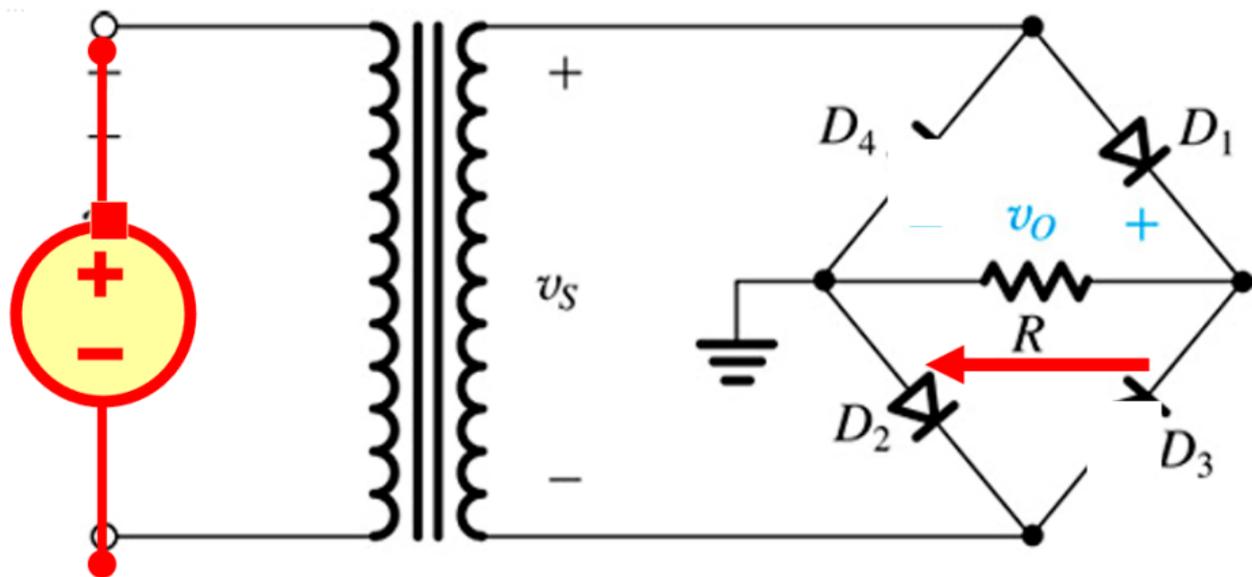
# Working principles


- When the instantaneous source voltage  $v_s > 0$ ,  $D_1$  and  $D_2$  conduct while  $D_3$  and  $D_4$  block
- In this case, the current passes from the source, then to  $D_1$ , then to  $D_2$  and return back to the source.



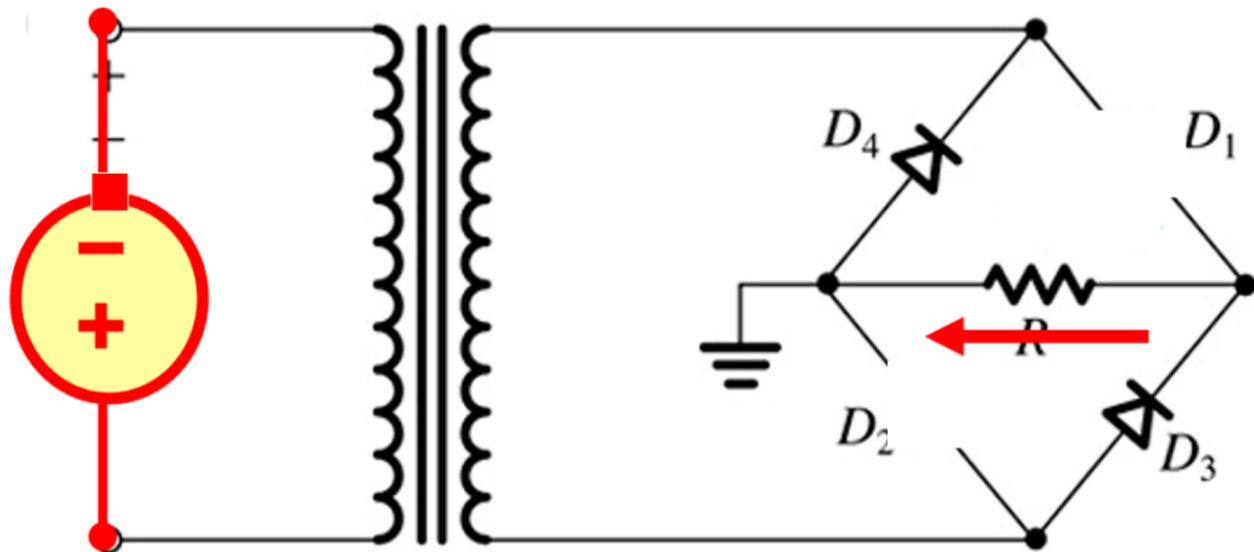
# Working principles

- When instantaneous source voltage is negative  $D_1$  and  $D_2$  block while  $D_3$  and  $D_4$  conduct
- In this case, the current passes from the source, then to  $D_3$ , then to  $D_4$  and return back to the source.




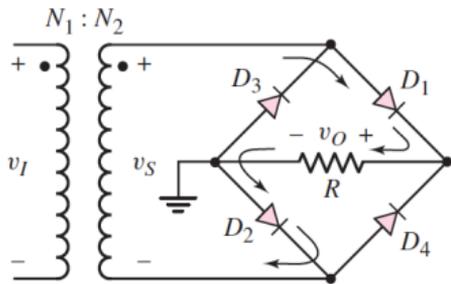

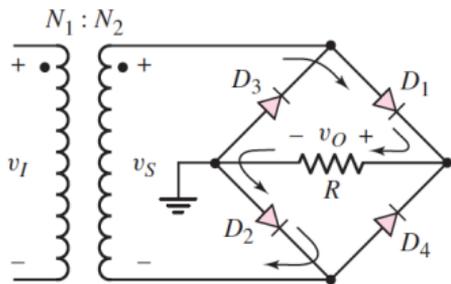
(a) Current direction for a positive input cycle



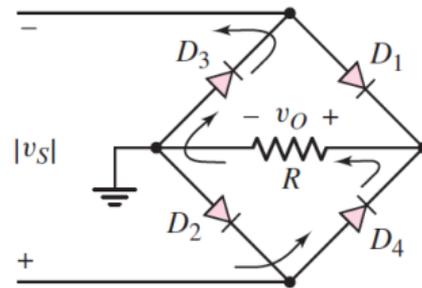
(a) Current direction for a positive input cycle



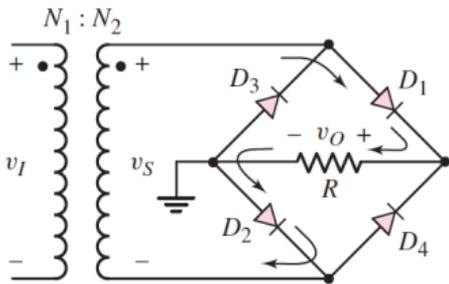
(b) Current direction for a negative input cycle



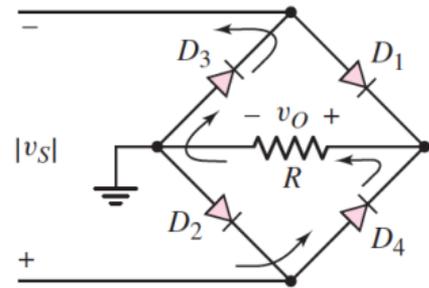(a) Current direction for a positive input cycle



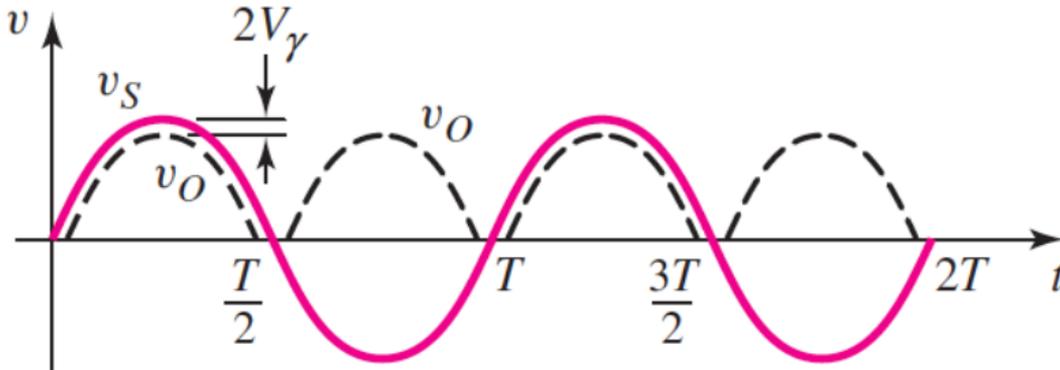(b) Current direction for a negative input cycle




(c) Input and output waveforms

**FIG 6.** A full-wave bridge rectifier
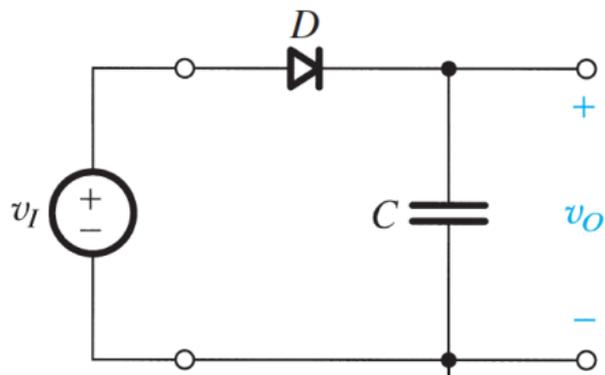
# The Peak Rectifier


- Pulsating nature of rectifier output makes unreliable dc supply.
- As such, a filter capacitor is employed to remove ripple.




(a) diode with a capacitor
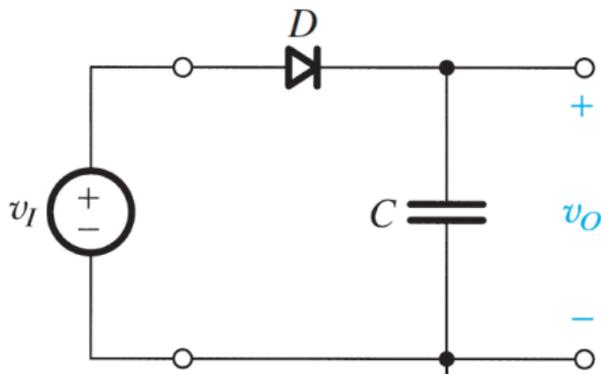
# The Peak Rectifier

- Pulsating nature of rectifier output makes unreliable dc supply.
- As such, a filter capacitor is employed to remove ripple.



(a) diode with a capacitor

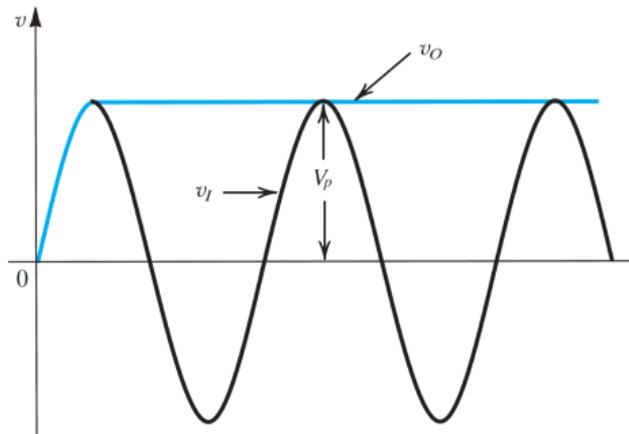


(b) Input and output assuming an ideal diode

**FIG 7.** A simple circuit used to illustrate the effect of a filter capacitor. Note that the circuit provides a dc voltage equal to the peak of the input sine wave. The circuit is therefore known as a *peak rectifier* or a *peak detector*


# The Peak Rectifier

The peak rectifier works in three steps:

- Step 1: The source voltage is positive, diode is ON—then **capacitor charges**.
- Step 2: The source voltage is reverse, diode is OFF—then **capacitor cannot discharge**
- Step 3: The source voltage is positive, diode is ON—then **capacitor charges**—thus, the capacitor maintains the existing voltage.
- This example is, of course, unrealistic because for any practical application, the converter would supply a load—which in turn provides a path for capacitor discharging.

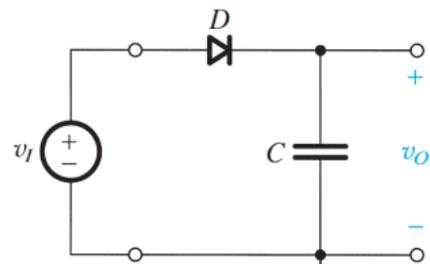

**FIG 8.** this is figure 1

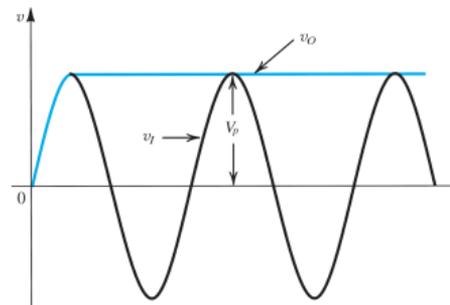

**FIG 9.** this is figure 2

# The Peak Rectifier

The peak rectifier works in three steps:

- Step 1: The source voltage is positive, diode is ON—then **capacitor charges**.
- Step 2: The source voltage is reverse, diode is OFF—then **capacitor cannot discharge**.
- Step 3: The source voltage is positive, diode is ON—then **capacitor charges**—thus, the capacitor maintains the existing voltage.
- This example is, of course, unrealistic because for any practical application, the converter would supply a load—which in turn provides a path for capacitor discharging.

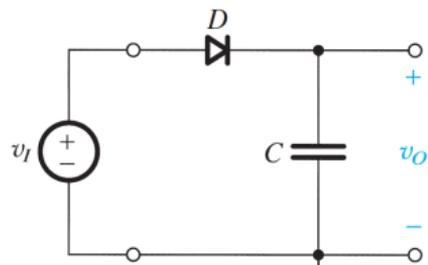


FIG 8. this is figure 1

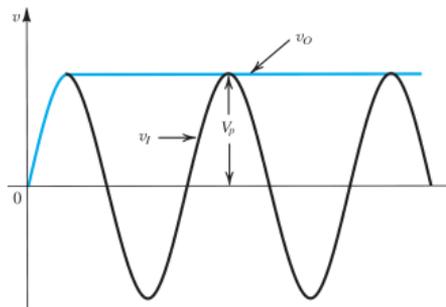


FIG 9. this is figure 2

# The Peak Rectifier

The peak rectifier works in three steps:

- Step 1: The source voltage is positive, diode is ON—then **capacitor charges**.
- Step 2: The source voltage is reverse, diode is OFF—then **capacitor cannot discharge**
- Step 3: The source voltage is positive, diode is ON—then **capacitor charges**—thus, the capacitor maintains the existing voltage.
- This example is, of course, unrealistic because for any practical application, the converter would supply a load—which in turn provides a path for capacitor discharging.

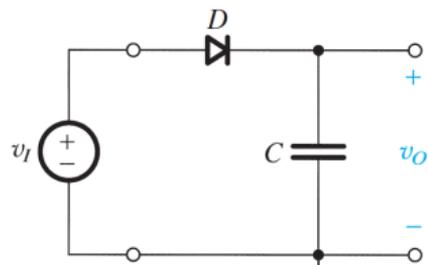


FIG 8. this is figure 1

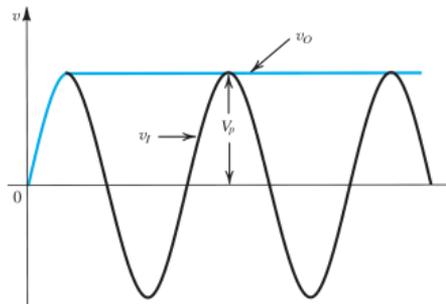


FIG 9. this is figure 2

# The Peak Rectifier

The peak rectifier works in three steps:

- Step 1: The source voltage is positive, diode is ON—then **capacitor charges**.
- Step 2: The source voltage is reverse, diode is OFF—then **capacitor cannot discharge**
- Step 3: The source voltage is positive, diode is ON—then **capacitor charges**—thus, the capacitor maintains the existing voltage.
- This example is, of course, unrealistic because for any practical application, the converter would supply a load—which in turn provides a path for capacitor discharging.

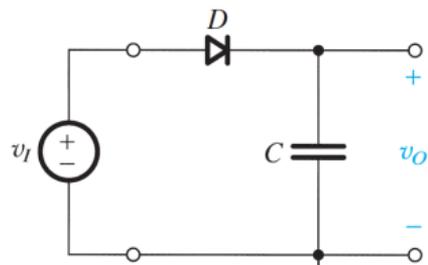


FIG 8. this is figure 1

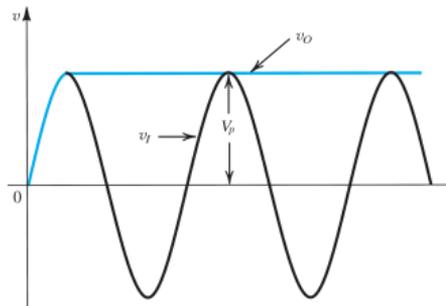


FIG 9. this is figure 2


# Peak Rectifier with a load

- Practical situation where a load resistance  $R$  is connected across the capacitor  $C$
- In this case, one must consider the **discharging** of capacitor across load.
- When diode is forward biased and conducting.

$$v_o(t) = v_I(t) - v_D \quad (4)$$

- When diode is reversed biased.

$$v_o(t) = V_{peak} e^{-\frac{t}{RC}} \quad (5)$$

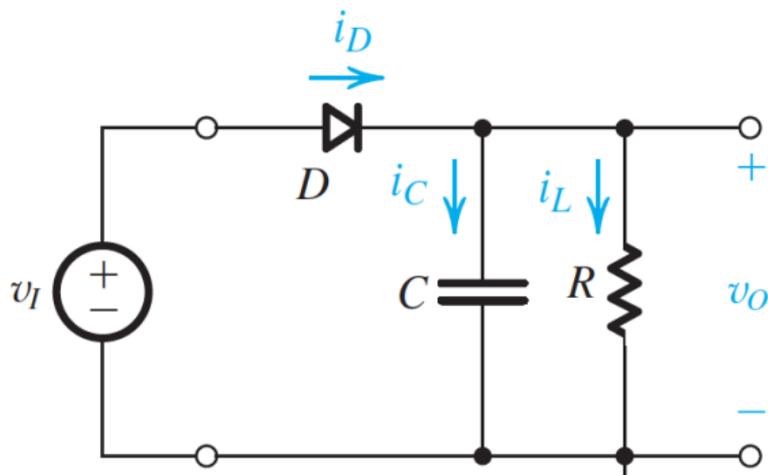

**FIG 10.** Rectifier with a filter capacitor and a load


# Peak Rectifier with a load

- Practical situation where a load resistance  $R$  is connected across the capacitor  $C$
- In this case, one must consider the **discharging** of capacitor across load.
- When diode is forward biased and conducting.

$$v_o(t) = v_I(t) - v_D \quad (4)$$

- When diode is reversed biased.

$$v_o(t) = V_{peak} e^{-\frac{t}{RC}} \quad (5)$$

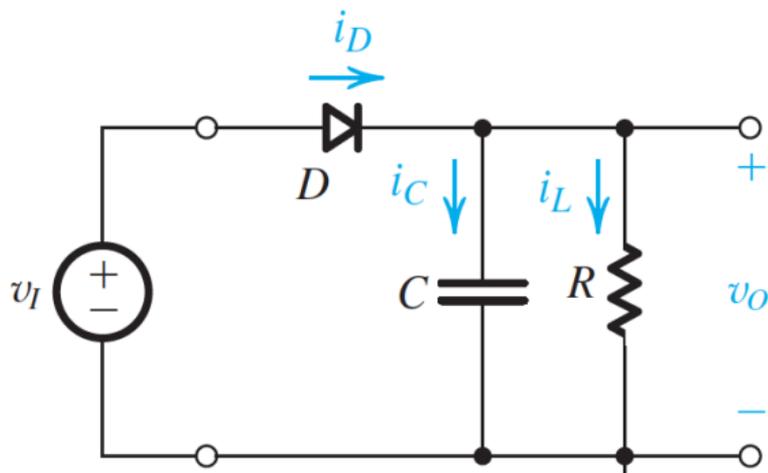

**FIG 10.** Rectifier with a filter capacitor and a load

# Peak Rectifier with a load

- Practical situation where a load resistance  $R$  is connected across the capacitor  $C$
- In this case, one must consider the **discharging** of capacitor across load.
- When diode is forward biased and conducting.

$$v_o(t) = v_I(t) - v_D \quad (4)$$

- When diode is reversed biased.

$$v_o(t) = V_{peak} e^{-\frac{t}{RC}} \quad (5)$$

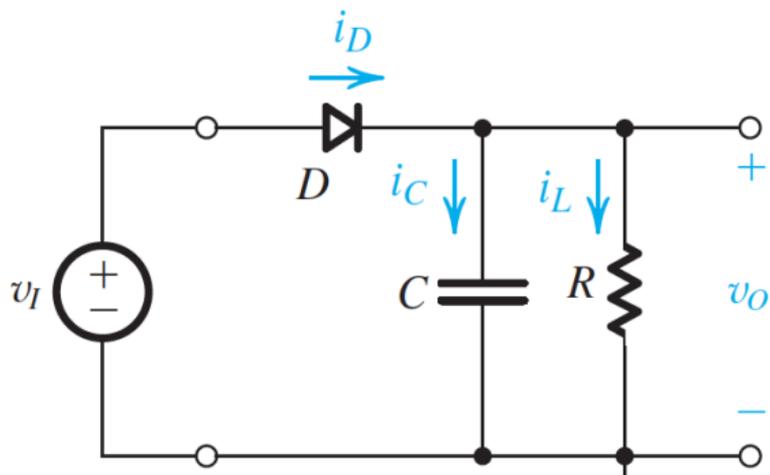


FIG 10. Rectifier with a filter capacitor and a load

# Peak Rectifier with a load

- Practical situation where a load resistance  $R$  is connected across the capacitor  $C$
- In this case, one must consider the **discharging** of capacitor across load.
- When diode is forward biased and conducting.

$$v_o(t) = v_I(t) - v_D \quad (4)$$

- When diode is reversed biased.

$$v_o(t) = V_{peak} e^{-\frac{t}{RC}} \quad (5)$$


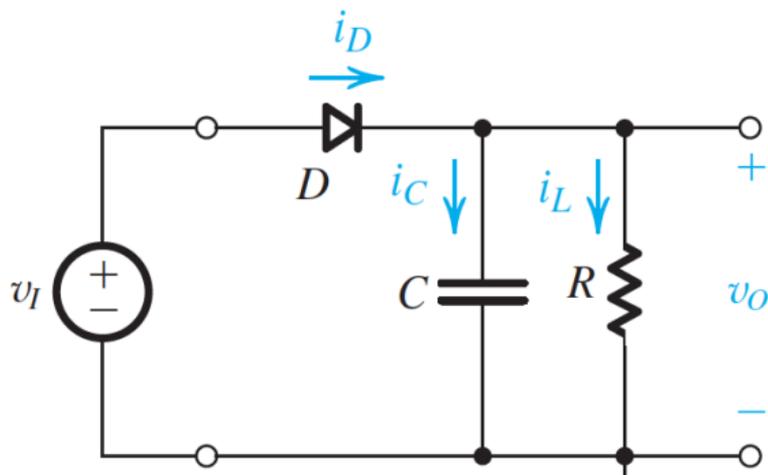
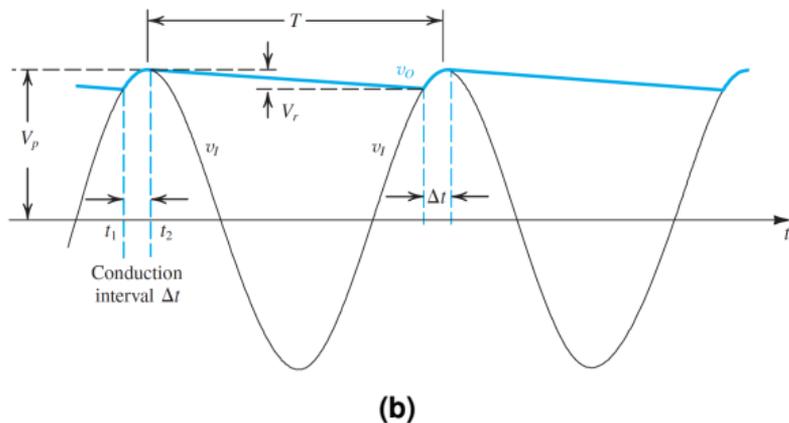


FIG 10. Rectifier with a filter capacitor and a load

# Case 1: —when the diode is forward biased

- The load current  $i_L$  is given  $i_L = v_o/R$
- The diode current is (Equation (6))

$$i_D = i_C + i_L = C \frac{dv_L}{dt} + i_L \quad (6)$$

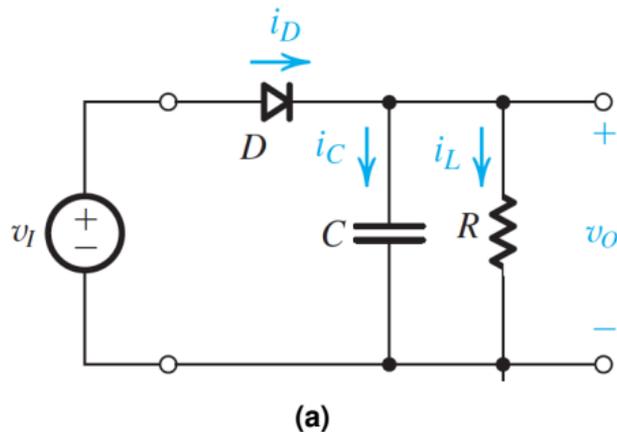

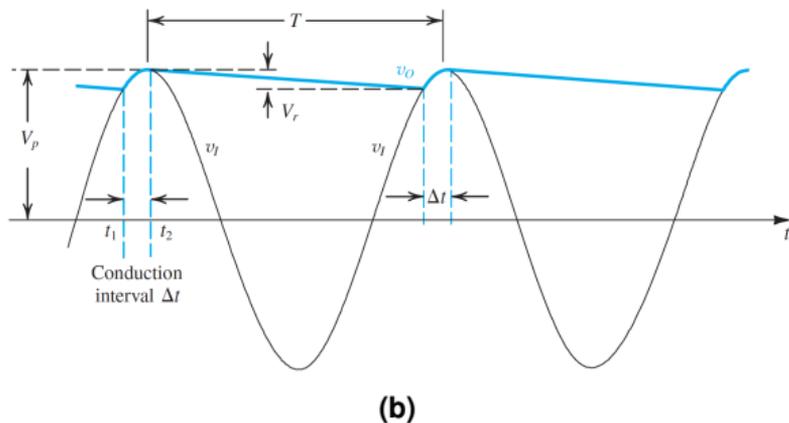
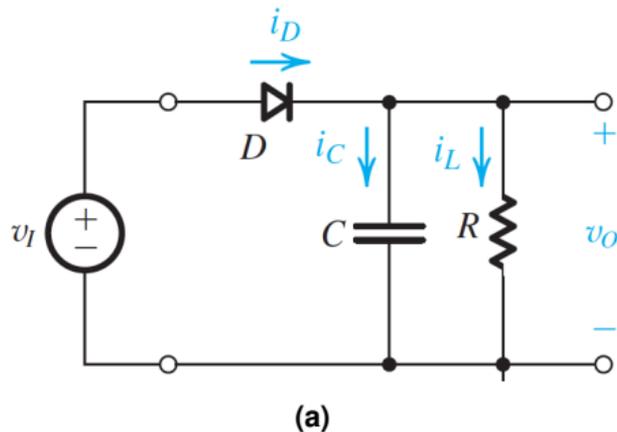
**FIG 11. Peak rectifier with  $v_L > 0$  for an ideal diode**

Fig. 11b shows the steady-state input and output voltage under the assumption that  $CR \gg T$

# Case 1: —when the diode is forward biased

- The load current  $i_L$  is given  $i_L = v_o/R$
- The diode current is (Equation (6))

$$i_D = i_C + i_L = C \frac{dv_I}{dt} + i_L \quad (6)$$

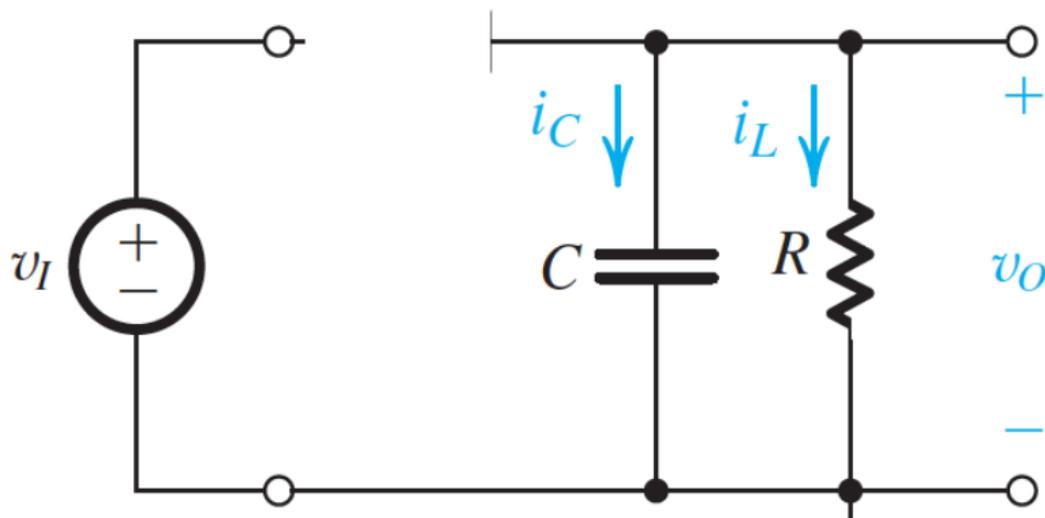


**FIG 11. Peak rectifier with  $v_I > 0$  for an ideal diode**

Fig. 11b shows the steady-state input and output voltage under the assumption that  $CR \gg T$


## Case 2: —when the diode is reverse biased

- The diode current is  $i_D = 0$
- The output voltage  $v_o$  is  $v_o = Ri_L$
- The load current is  $i_L = -i_C$



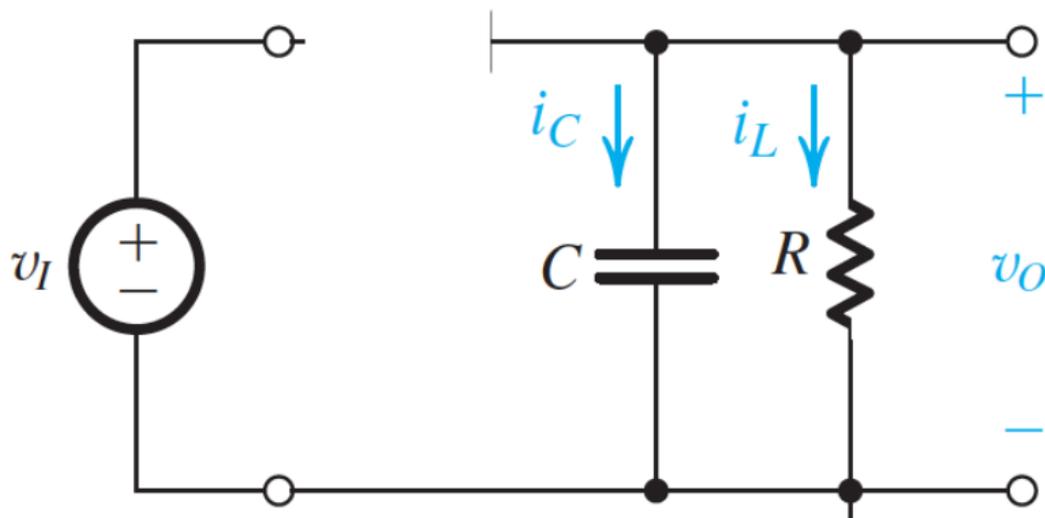
## Case 2: —when the diode is reverse biased

- The diode current is  $i_D = 0$
- The output voltage  $v_o$  is  $v_o = Ri_L$
- The load current is  $i_L = -i_C$


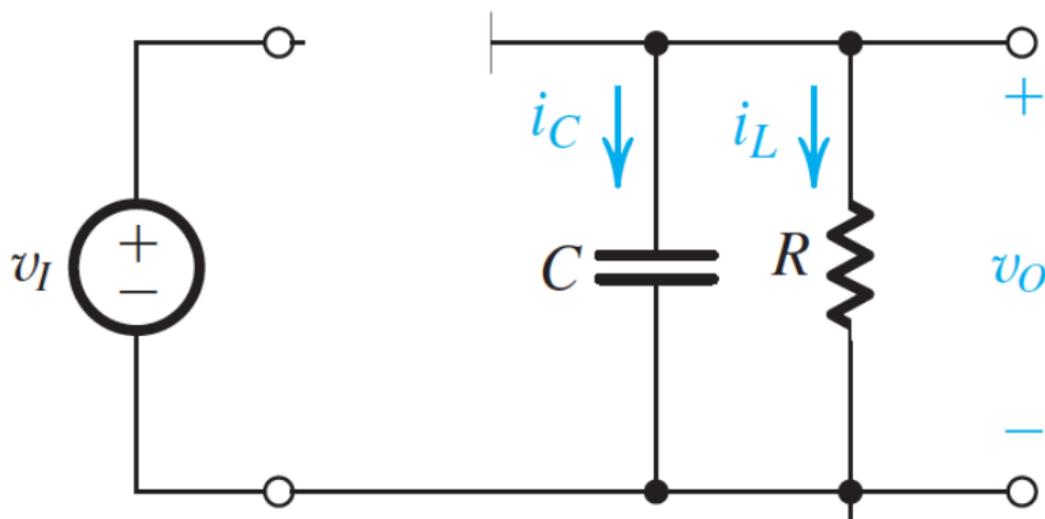
## Case 2: —when the diode is reverse biased

- The diode current is  $i_D = 0$
- The output voltage  $v_o$  is  $v_o = Ri_L$
- The load current is  $i_L = -i_C$



# Full-wave peak rectifier.

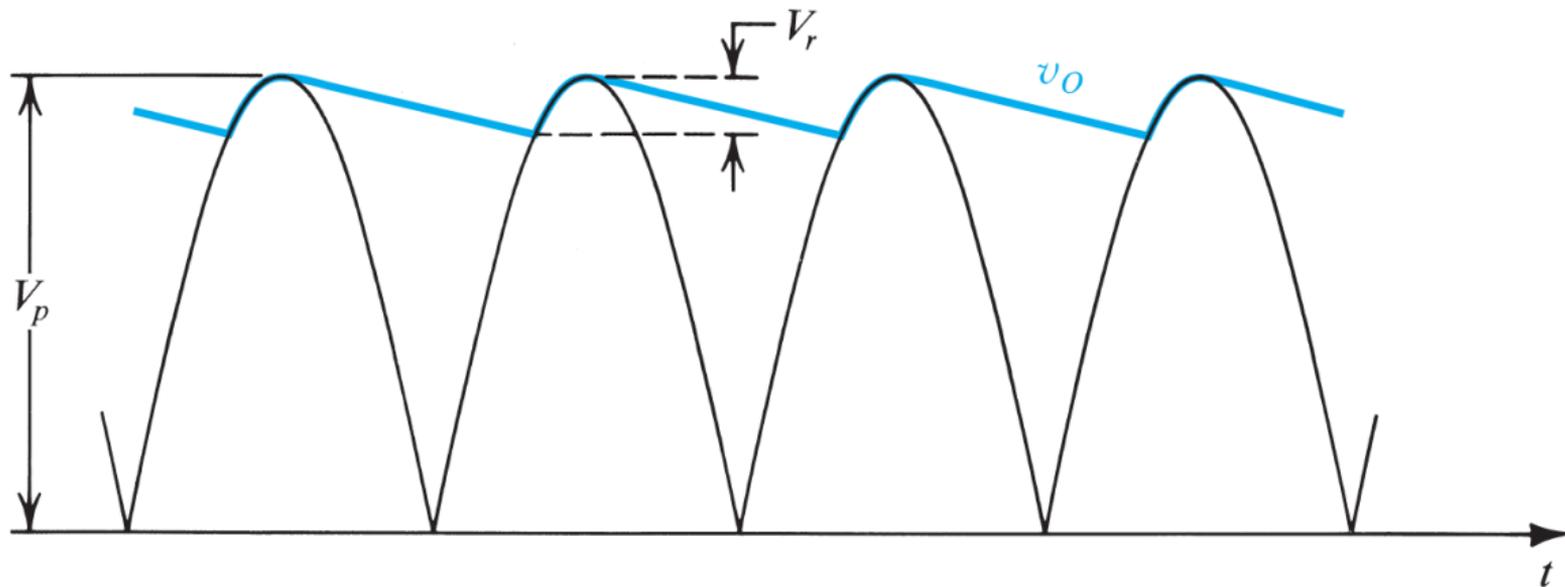


FIG 12. Waveforms in the full-wave peak rectifier.

**The end**